

TUTORIAL-6

EE 101: Basic Electronics

DEPARTMENT OF ELECTRONICS & ELECTRICAL ENGINEERING

INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI



(First question is the **Pre-Tutorial Assignment problem** to be solved in the space provided.)

Name:


Roll No.

Tutorial Group:

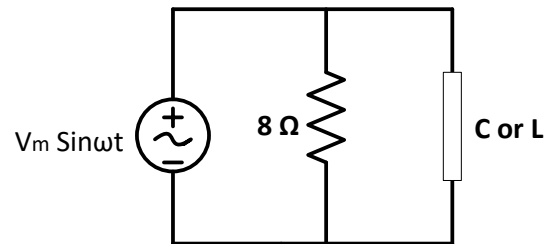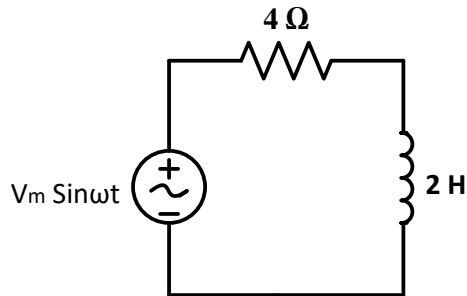
1. Under what conditions the following ac circuits will be equivalent to each other?



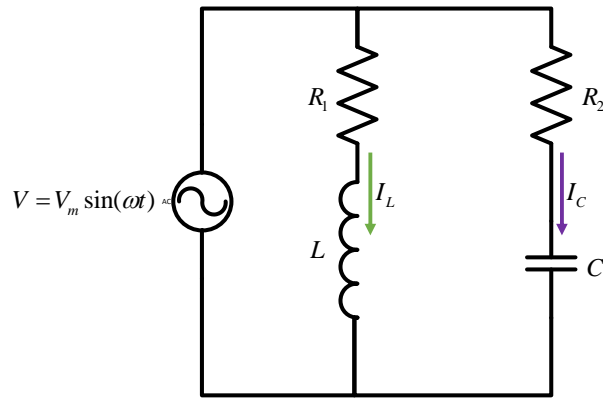
2. Draw an approximate phasor diagram for the following circuit and derive the condition for the two branch currents I_L and I_C to be in quadrature.



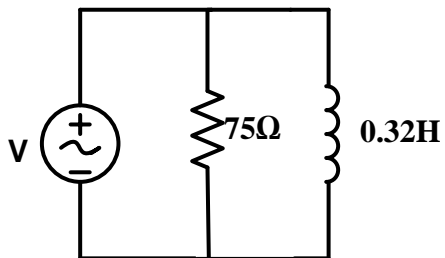3. Consider the following circuit which has a voltage source of $240\sqrt{2} \cos(100\pi t)$ V. Find its real power, reactive power and power factor. If a capacitor of $C = 11.3 \mu\text{F}$ is connected in parallel with the voltage source, then find its power factor.



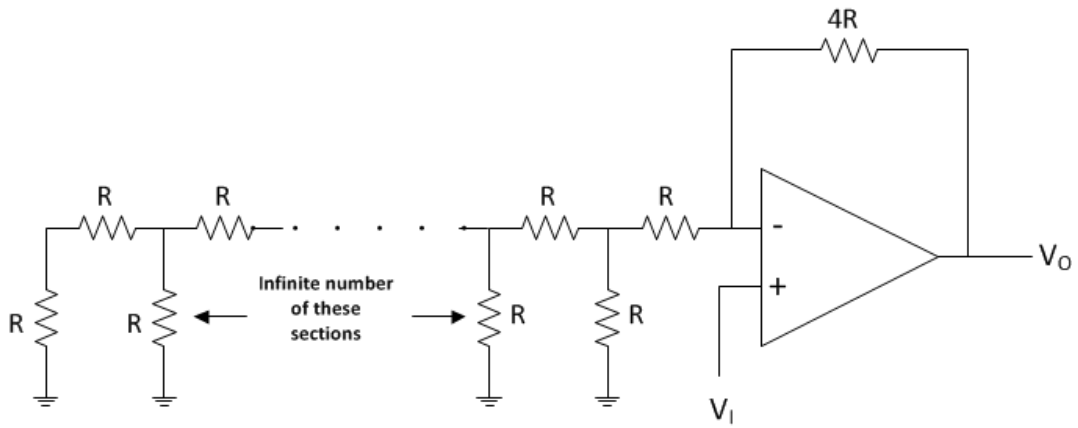4. Find the gain $A_v = \frac{V_o}{V_i}$ of the circuit shown.



5. Find the output voltage v_o of the circuit given below.

