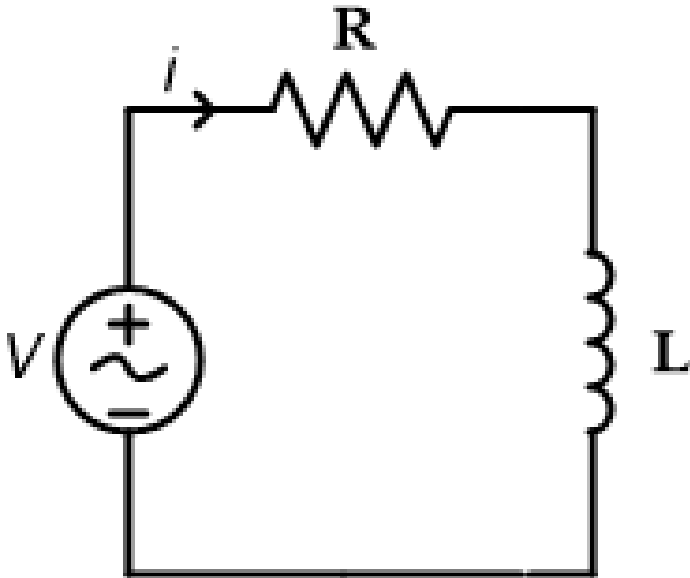


Lecture 9

Instantaneous Power, Average and Complex Power, Apparent Power and Power Factor

Instantaneous Power



Let $v = V_m \sin(\omega t + \theta)$

Then $i = I_m \sin(\omega t + \phi)$


$$p(t) = v(t)i(t)$$

$$p(t) = V_m \sin(\omega t + \theta) I_m \sin(\omega t + \phi)$$

$$p(t) = \frac{V_m I_m}{2} (\cos(\theta - \phi) - \cos(2\omega t + \theta + \phi))$$

$$p(t) = \frac{V_m I_m}{2} \cos(\theta - \phi) - \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)$$

Average Power

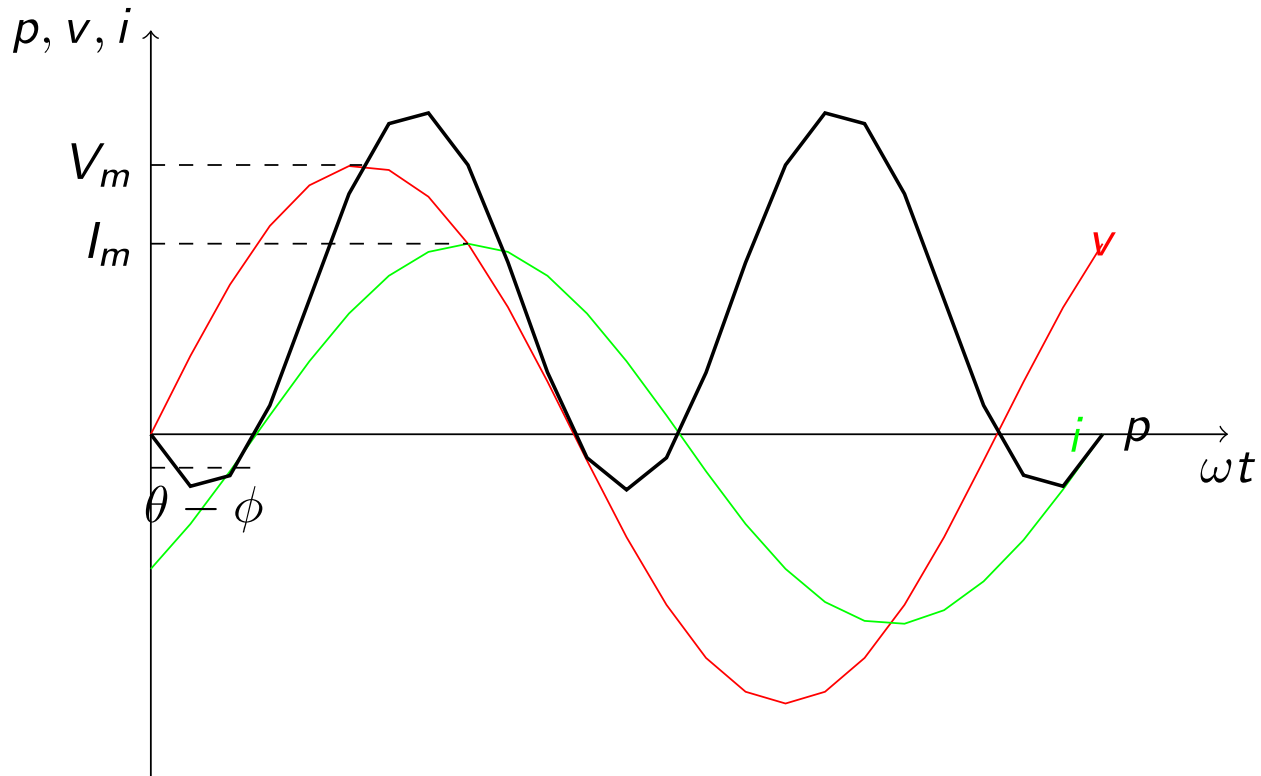

$$P = \frac{1}{T} \int_0^T p(t) dt$$

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

Average Power


Resistor: V_m and I_m are in phase.

$$P = \frac{1}{2} V_m I_m \cos(0) = \frac{1}{2} V_m I_m$$

Ideal Inductor : V_m leads I_m by 90° .

$$P = \frac{1}{2} V_m I_m \cos(90^\circ) = 0$$

RMS current and voltage

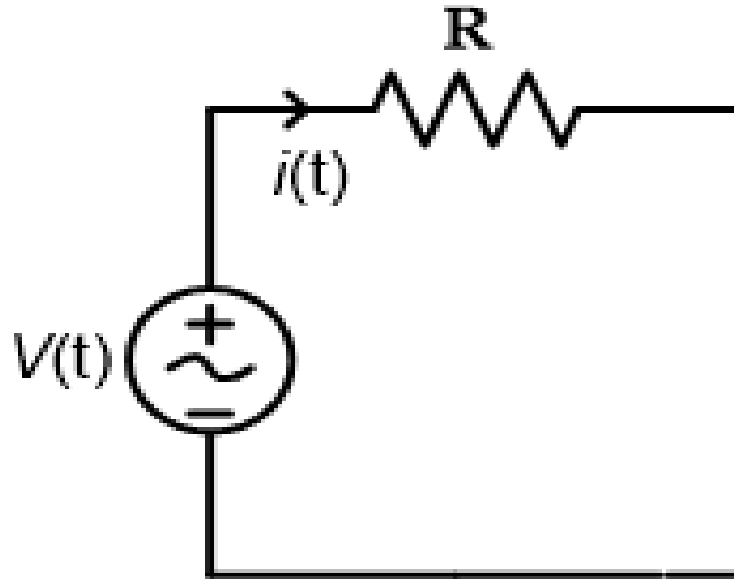

$$V = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$I = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$


Average or Real Power

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi) = VI \cos(\theta - \phi)$$

where

$$V = \frac{V_m}{\sqrt{2}}, \quad I = \frac{I_m}{\sqrt{2}}$$

Power Triangle

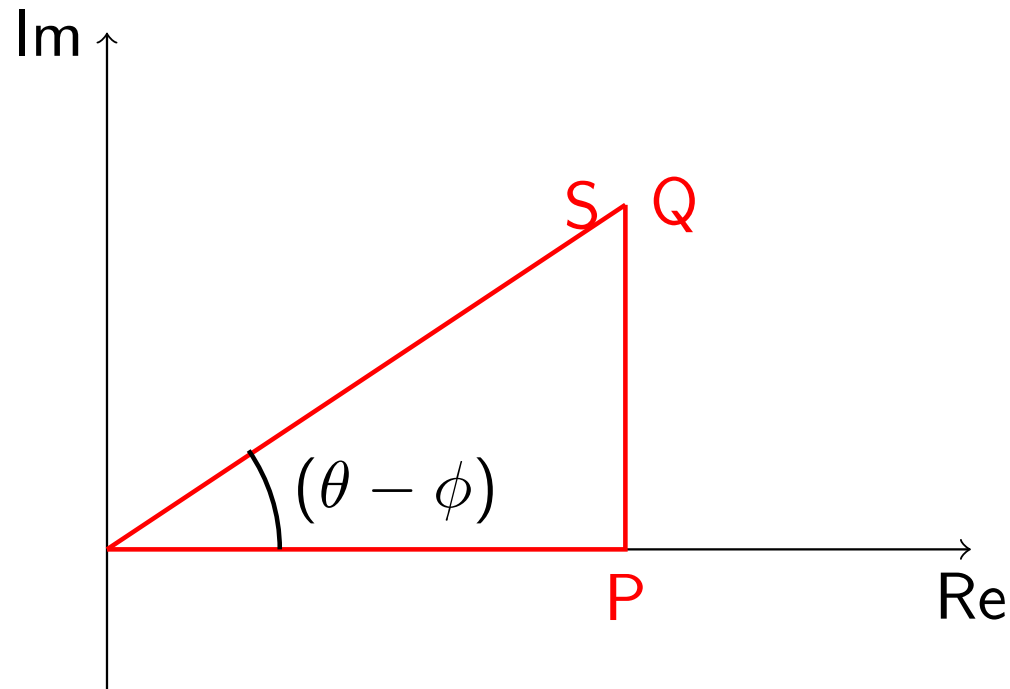

$$\mathbf{S} = VI \cos(\theta - \phi) + jVI \sin(\theta - \phi)$$

P = Real power in W, Q=Reactive power in VAR

Complex Power

$$\begin{aligned}\mathbf{S} &= VI \cos(\theta - \phi) + jVI \sin(\theta - \phi) \\ &= VI \angle(\theta - \phi) = V \angle \theta \ I \angle -\phi\end{aligned}$$

Phasor voltage and current are

$$\mathbf{V} = V \angle \theta, \quad \mathbf{I} = I \angle \phi$$

Then the complex power is

$$\mathbf{S} = \mathbf{V} \mathbf{I}^*$$

Apparent Power

Magnitude of complex power is called the apparent power

$$|S| = VI$$

Power factor

pf is the ratio of real power to the apparent power


$$\text{pf} = \frac{VI \cos(\theta - \phi)}{VI} = \cos(\theta - \phi)$$

Maximum value of pf is 1


$(\theta - \phi) < 0$ power factor is LEADING

Test

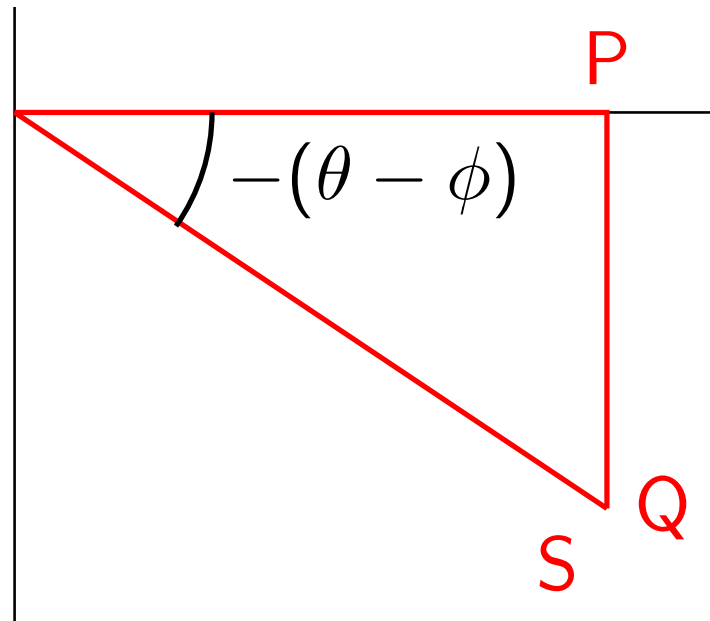- Draw the power triangle of a RC load connected to a sinusoidal source



Estimate average, reactive powers and pf

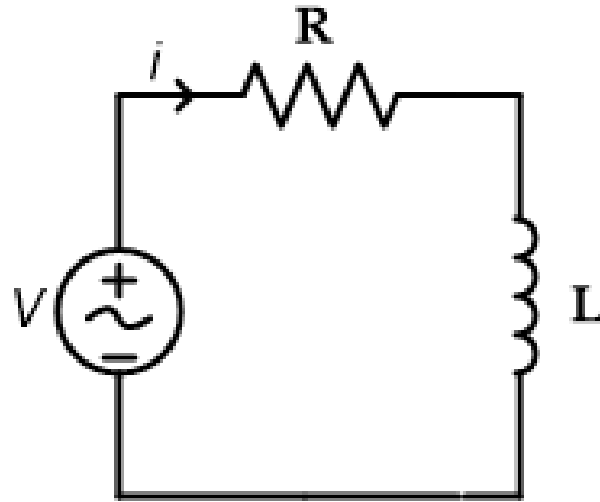

Given, $v=230\sqrt{2} \sin(1000t)$, $R = 4\Omega$ and $L = 3\text{mH}$

Answers: **8.5 kW**, **6.3 kVAR**, **0.8 lagging**