
TUTORIAL-9

EE 101: Basic Electronics DEPARTMENT OF ELECTRONICS & ELECTRICAL ENGINEERING INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI

(First question is the Pre-Tutorial Assignment problem to be solved in the space provided.)

1. Two wattmeter method is employed to measure the 3-phase power. A 3-phase line supplies to a balanced inductive delta connected load. The current coil of Wattmeter W1 is in line A and its voltage coil is connected across the line voltage V_{AC}. The current coil of Wattmeter W₂ is in line B and its voltage coil is connected across the line voltage V_{BC}. Derive the expressions for the readings of W₁ and W₂ in terms of the line voltage (V_L) and the line current (I_L) and the phase angle θ (angle between the phase voltage and phase current). Assume the line voltage V_{AB} as the reference. Draw the phasor diagram to explain your derivations.

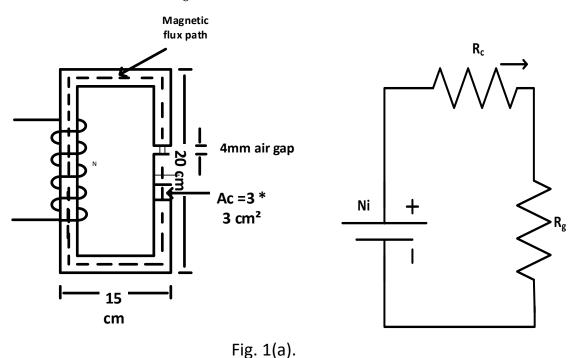- 2. Three identical coils, each having a reactance of 20 Ω and a resistance of 20 Ω are connected (a) in star, (b) in delta, across 440 V, 3-phase line. Calculate for each method of connection, the line current and the readings on each of the two watt-meters connected to measure the power.
- 3. Fig. 1(a) shows a rectangular magnetic core with an air gap. Find the exciting current needed to cause a flux density of $B_g = 1.2T$ in the air gap. Given $N = 400 \ turns$ and $\mu_r(iron) = 4000$



- 4. Given the function $f(A,B,C,D)=\sum m(1,2,3,5,13)+\sum d(6,7,8,9,11,15)$.
 - (a) Find a minimal sum-of-products expression.
 - (b) Find a minimal products -of-sums expression.
 - (c) Compare the expression obtained in (a) and (b). If they do not represent identical function. Explain why?
- 5. $f(A,B,C,D) = (A+B+D)(B+C)(\overline{A}+\overline{D})(\overline{A}+C)$ is the minimal product-of-sums expression obtained by simplifying $f(A,B,C,D) = (A+B+D)(\overline{A}+B+C)(\overline{A}+\overline{B}+C)(\overline{A}+\overline{B}+\overline{C}+\overline{D})$ through kmap. Is there any don't care terms in the k-map? If so, determine the don't care terms.