

# Lecture 5


Revision for Quiz

and


RL Circuit

# Revision for Quiz

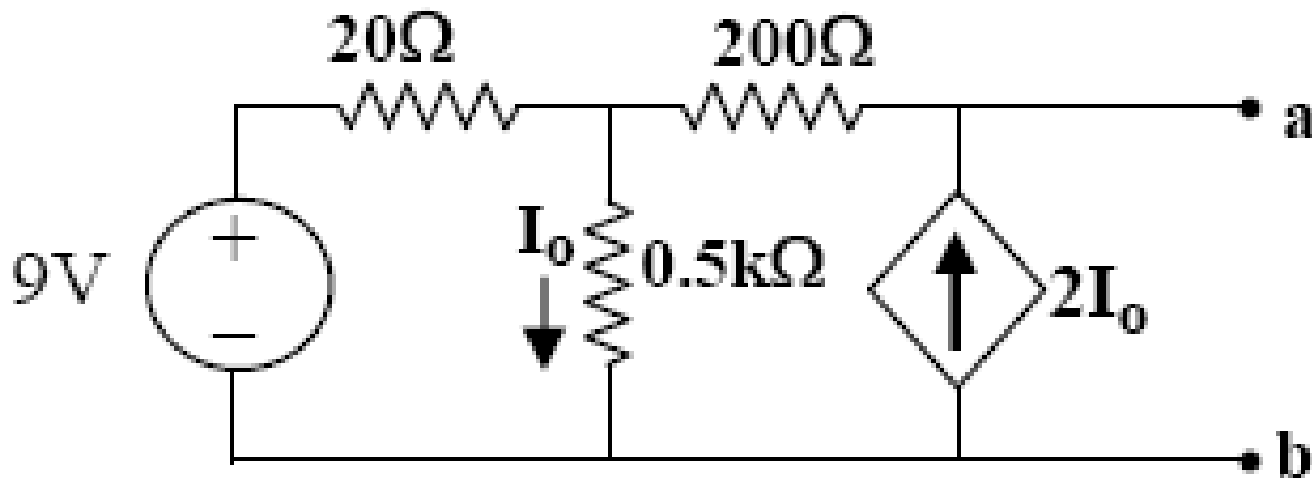Q.1 Find the Norton's equivalent current ( $I_{sc}$ ) of the circuit between the terminals **a-b**.



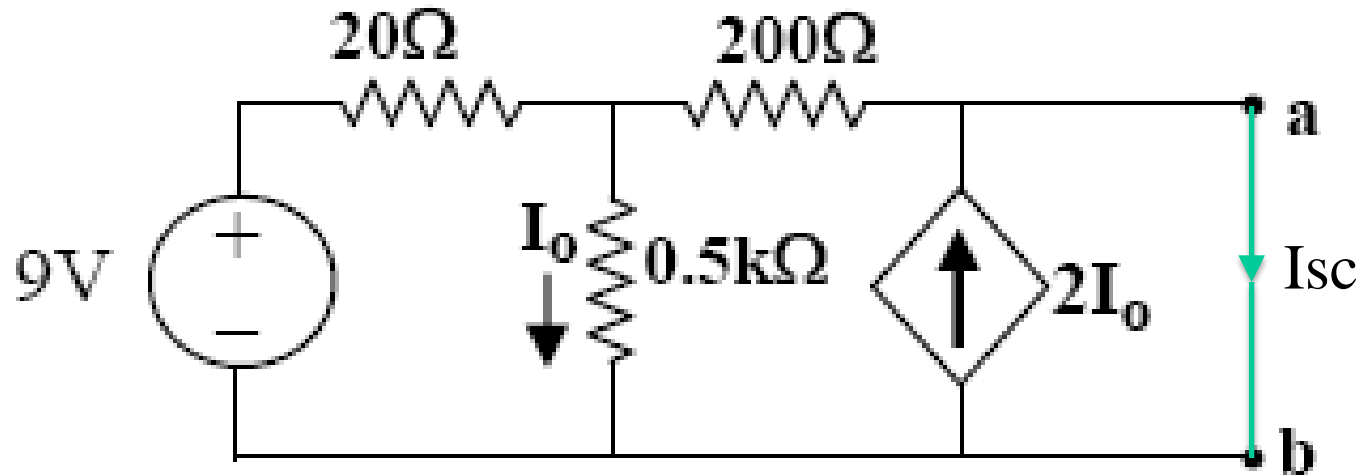To find Norton's current  $I_{sc}$ , terminals **a** and **b** are short-circuited




Apply Nodal/Mesh analysis and find  $I_{sc}$ .


Answer :  $I_{sc} = 0.07104 \text{ A}$  (approx)

# Revision for Quiz

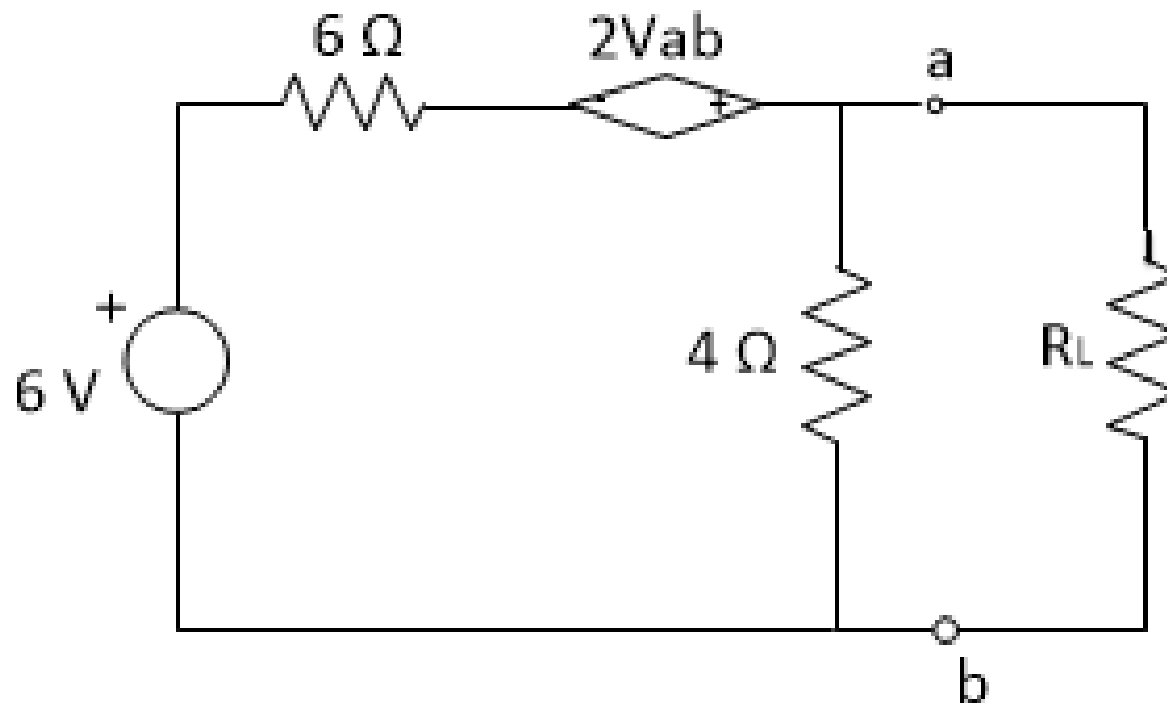Q.2 Find maximum power delivered to the load  $\mathbf{R_L}$ .



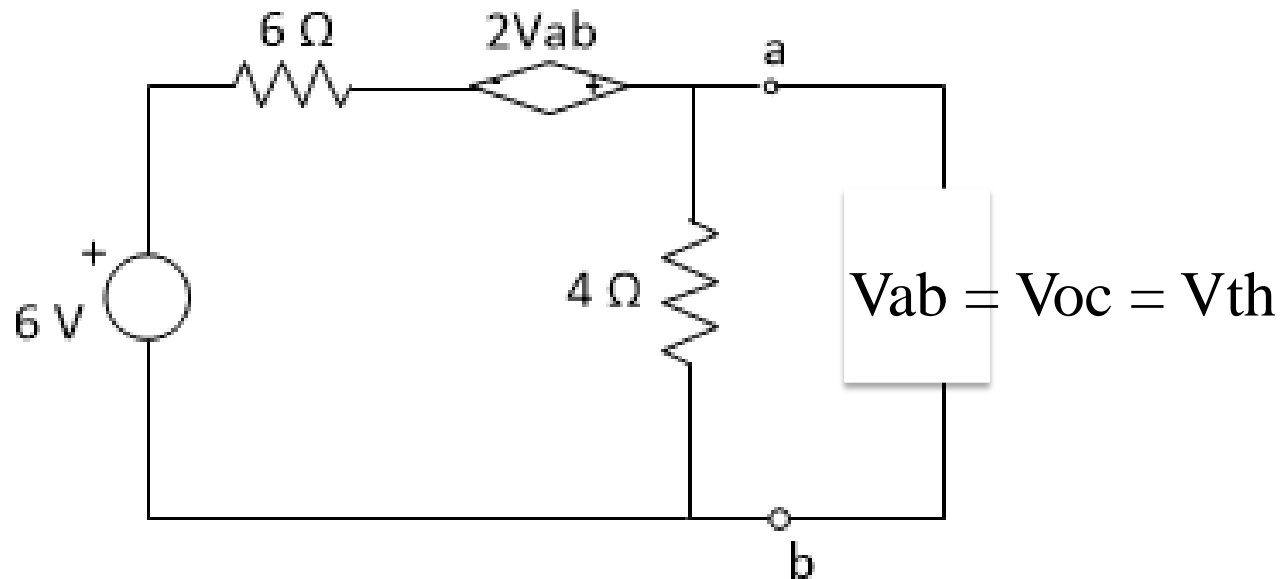
Thevenin's voltage and equivalence resistance are to be estimated first. Remove  $R_L$  to find  $V_{ab} = V_{th}$



Answer :  $P_{max} = 3 \text{ W}$

# Revision for Quiz

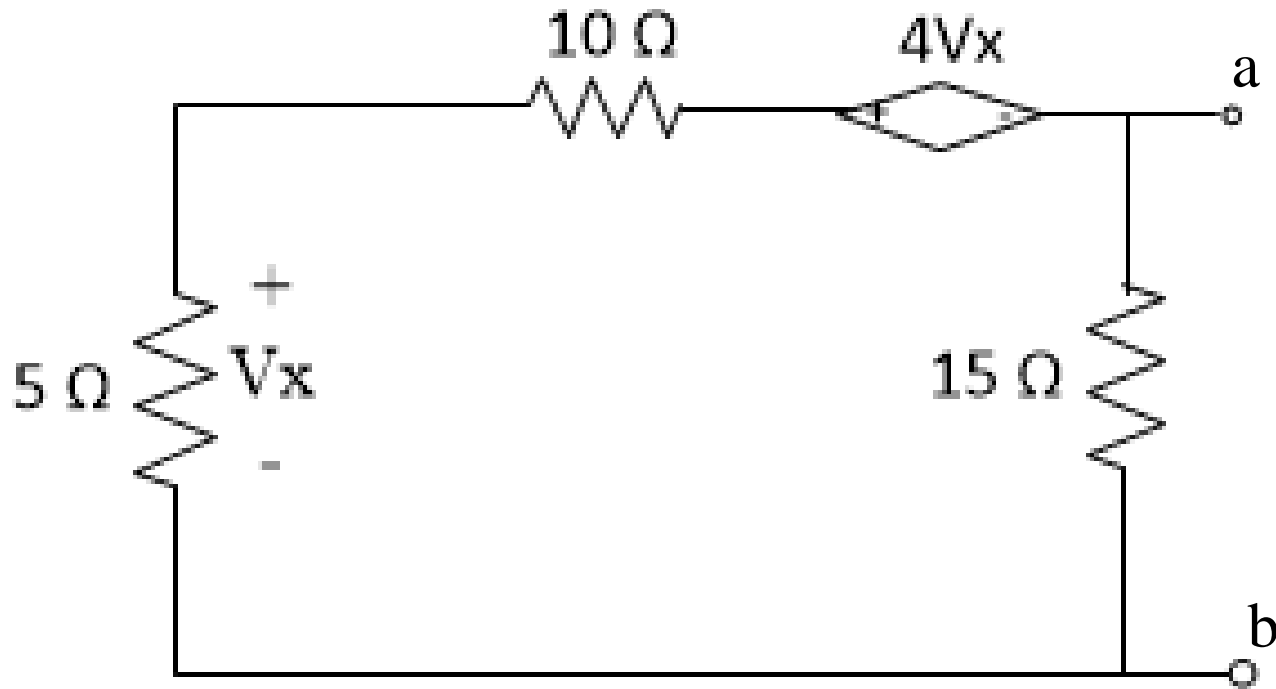
Q.3 Find Thevenin's equivalent of the following circuit.



Answer :  $V_{th} = 0\text{ V}$  and  $R_{th} = -7.5\ \Omega$

# RL and RC Circuits


## The Inductor

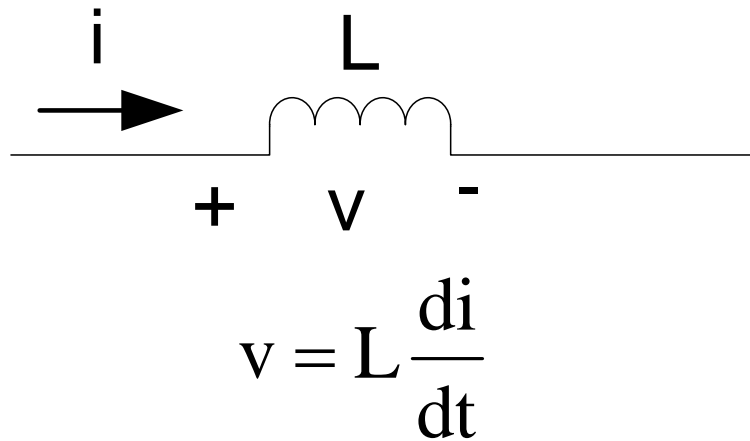

If current  $i$  is constant, voltage  $v$  is 0

So, inductor behaves as a short circuit to dc input current

# The Capacitor

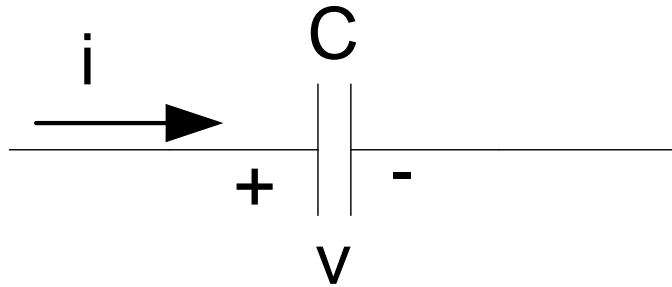


$$i = C \frac{dv}{dt}$$

If voltage  $v$  is constant, then  $i$  is 0

So, capacitor behaves as an open circuit to dc input voltage




# Response of RL Series Circuit

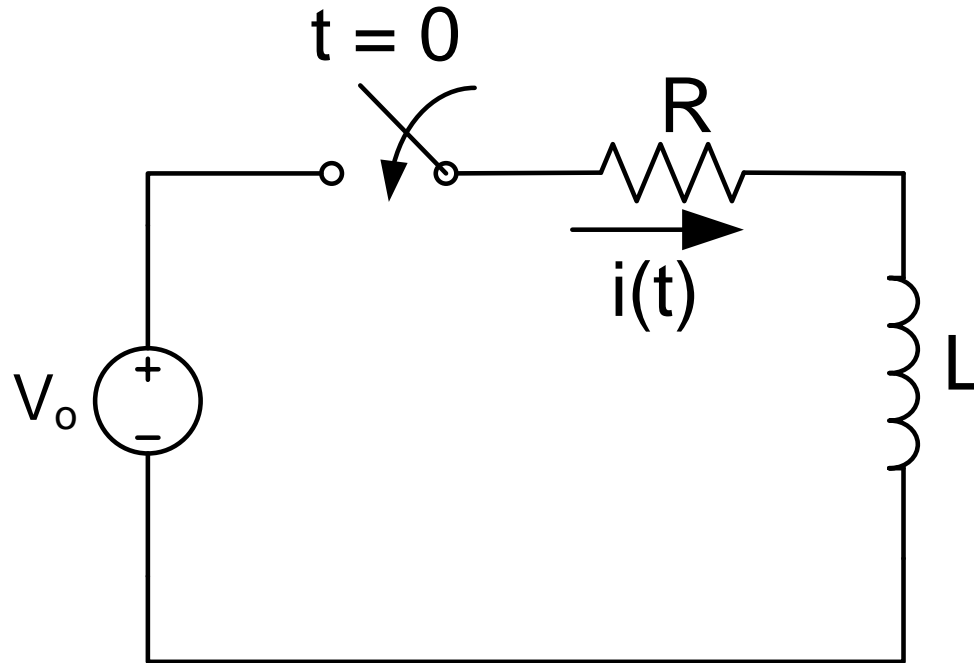

Find  $i(t)$

Why RL load?

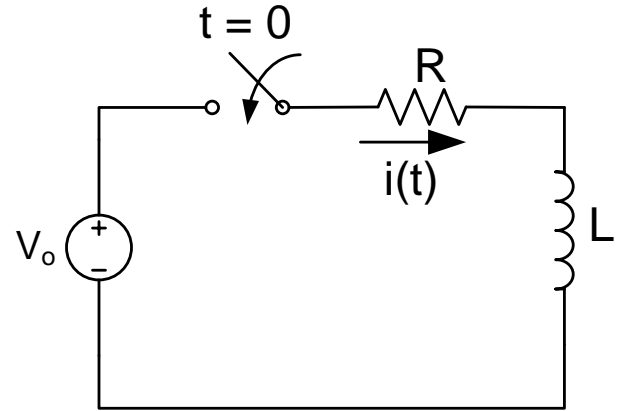

*For  $t < 0$ ,  $i(t) = 0$*

$$Ri + L \frac{di}{dt} = V_0 \quad \text{for } t > 0 \quad \text{and using KVL}$$

$$\text{or, } L \frac{di}{dt} = V_0 - Ri$$

$$\text{or, } \frac{L di}{V_0 - Ri} = dt$$

Integrating, we get

$$\int \frac{L di}{V_0 - Ri} = \int dt$$

$$-\frac{L}{R} \ln(V_0 - Ri) = t + K$$

Integrating, we get

$$\int \frac{L di}{V_0 - Ri} = \int dt$$

$$-\frac{L}{R} \ln(V_0 - Ri) = t + K$$

Setting  $i = 0$  at  $t = 0$ , we have

$$-\frac{L}{R} \ln V_0 = K$$

Hence, we have

$$-\frac{L}{R} \ln(V_0 - Ri) = -\frac{L}{R} \ln V_0 + t$$

$$\text{or, } -\frac{L}{R} \ln\left(\frac{V_0 - Ri}{V_0}\right) = t$$

$$\text{or, } \ln\left(\frac{V_0 - Ri}{V_0}\right) = -\frac{Rt}{L}$$

$$\text{or, } \frac{V_0 - Ri}{V_0} = e^{-\frac{Rt}{L}}$$

$$V_0 - Ri = V_0 e^{-\frac{R}{L}t}$$

$$\text{or, } Ri = V_0 - V_0 e^{-\frac{R}{L}t}$$

$$\text{or, } i = \frac{V_0}{R} - \frac{V_0}{R} e^{-\frac{R}{L}t}$$

The expression for the response for all t is

$$i(t) = \left( \frac{V_0}{R} - \frac{V_0}{R} e^{-\frac{R}{L}t} \right)$$

$$\frac{L}{R} = \tau = \text{Time Constant}$$

$$i(t) = \left( \frac{V_0}{R} - \frac{V_0}{R} e^{-\frac{t}{\tau}} \right)$$

*Another way to solve*

$$Ri + L \frac{di}{dt} = V_0 \quad \text{for } t > 0$$

*Solution -*

*Complimentary Function + Particular Integral*

*Solution -*

*Natural Response ( $i_n$ ) from*

$$Ri + L \frac{di}{dt} = 0$$

*Forced Response ( $i_f$ ) from*

$$Ri + L \frac{di}{dt} = V_0$$

*Complete Solution is*

$$i = i_n + i_f$$



*For Natural Response*

$$Ri + L \frac{di}{dt} = 0$$

$$\text{or, } \frac{di}{dt} + \frac{R}{L}i = 0$$

$$\text{or, } i_n = Ae^{-\frac{R}{L}t}$$

*For Forced Response*

$$Ri + L \frac{di}{dt} = V_0$$

$$\text{But } L \frac{di}{dt} = 0$$

$$\text{So, } i_f = \frac{V_0}{R}$$

$$i(t) = Ae^{-\left(\frac{R}{L}\right)t} + \frac{V_0}{R} \quad t > 0$$

*For Finding A :      Apply the condition*


$$i(t = 0) = i(t = 0^-) = i(t = 0^+)$$

$$0 = A + \frac{V_0}{R}$$

$$A = -\frac{V_0}{R}$$

$$i(t) = \left( \frac{V_0}{R} - \frac{V_0}{R} e^{-\frac{R}{L}t} \right) \quad t > 0$$
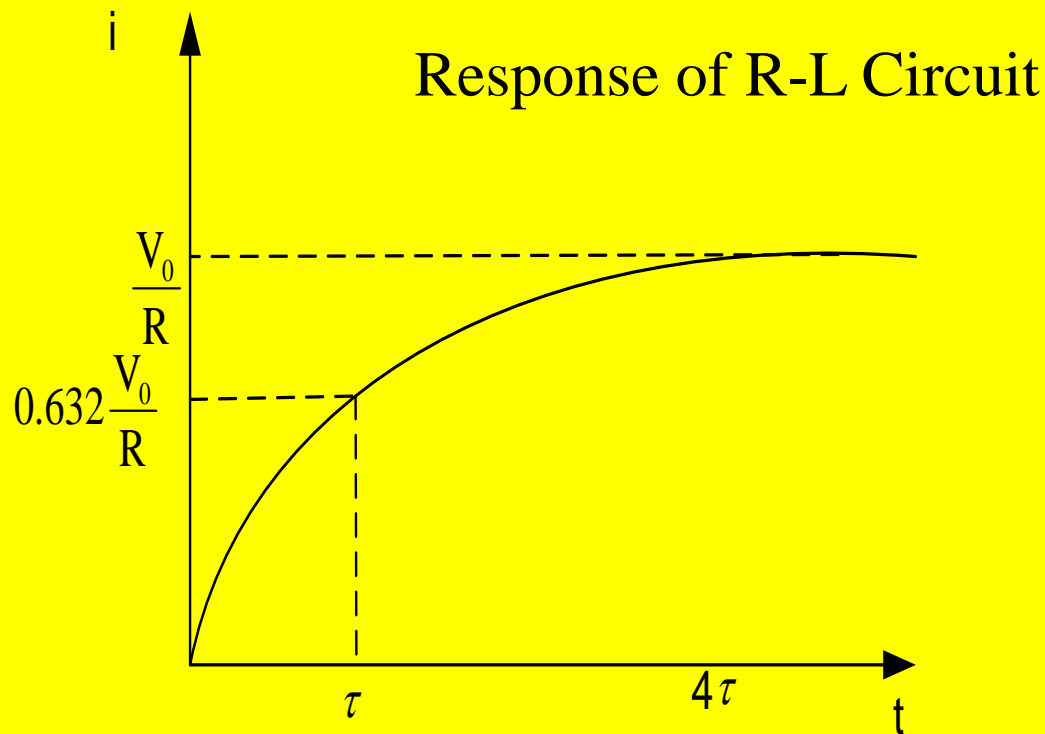
$$\text{or, } i(t) = \frac{V_0}{R} \left( 1 - e^{-\frac{t}{\tau}} \right) \quad t > 0 \quad \tau = \frac{L}{R} \quad \text{Time Constant}$$



At  $t=4\tau$   
98% of  
final  
response  
of  $i(t)$   
happens