

SOLUTIONS

Solution-1:

$$I_D = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right) \quad \text{with} \quad V_T = \frac{kT}{q}$$

$k = (1.38 \times 10^{-23})$ J/K (Boltzmann's constant), $q = 1.6 \times 10^{-19}$ C (electronic charge)

At 25°C , $T = 273 + 25 = 298\text{ K}$ and $V_T = 25.70\text{ mV}$

$$\frac{I_D}{I_S} = \frac{10 \times 10^{-3}}{0.01 \times 10^{-6}} = 10^6$$

$$\text{Therefore, } V_D = nV_T \ln \left(\frac{I_D}{I_S} + 1 \right) = 0.71\text{ V}$$

For Temperature $= 30^\circ\text{C}$

$$\text{We know, } I_{S2} = I_{S1} \times 2^{\left(\frac{T_2 - T_1}{10} \right)}$$


Here, $T_1 = 298\text{ K}$ and $T_2 = 273 + 30 = 303\text{ K}$ for $I_{S1} = I_S|_{T=298\text{ K}}$ and $I_{S2} = I_S|_{T=303\text{ K}}$

At 30°C (303 K), $I_{S2} = (0.01 \times 10^{-6}) \times \sqrt{2} = 1.414 \times 10^{-8}\text{ A} = I_S|_{T=303\text{ K}}$ and $V_T = 26.134\text{ mV}$


Using the new values for I_S and V_T , the required V_D for $I_D = 10\text{ mA}$ is - $V_D = 0.704\text{ V}$

Therefore, Percentage decrease in V_D required is $\frac{0.710 - 0.704}{0.710} \times 100 = 0.85\%$.

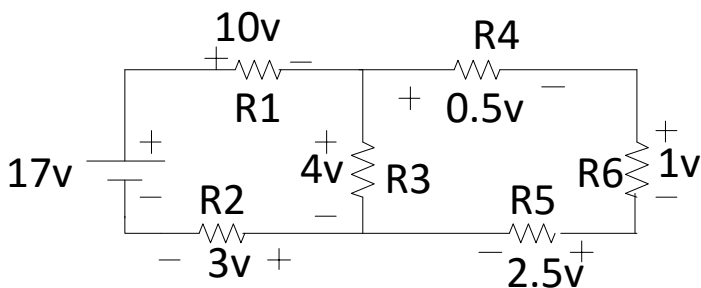
Solution-2 (a): Voltage across R_4 is 0.5 V .



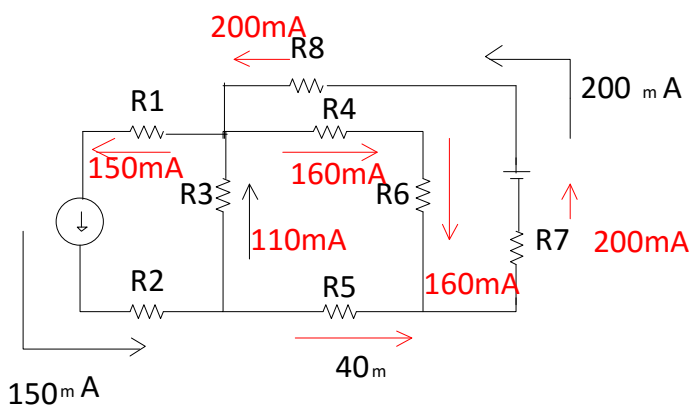Solution-2 (b): Currents are indicated in RED colour.



Solution-3:

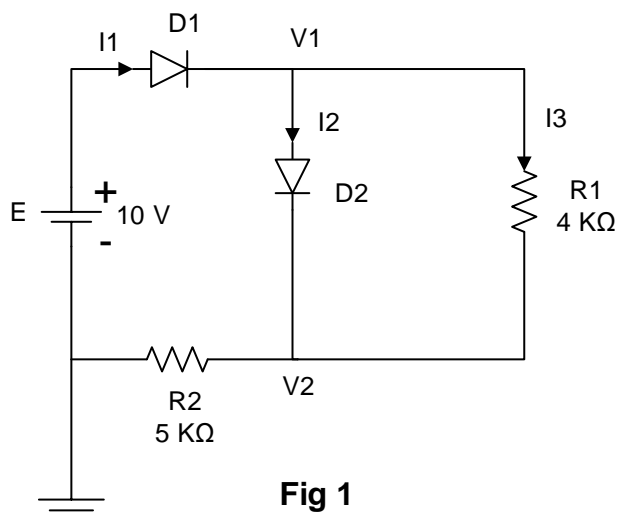


$$V1 = 10 - 0.7 = 9.3 \text{ V}, \quad V2 = 9.3 - 0.7 = 8.6 \text{ V}, \quad I_{R2} = \frac{8.6}{5} = 1.72 \text{ mA}$$

$$I3 = \frac{0.7}{4} = 0.175 \text{ mA}, \quad I2 = 1.72 - 0.175 = 1.545 \text{ mA}$$

$$I1 = I2 + I3 = I_{R2} = 1.72 \text{ mA}$$

Solution-4 (a):

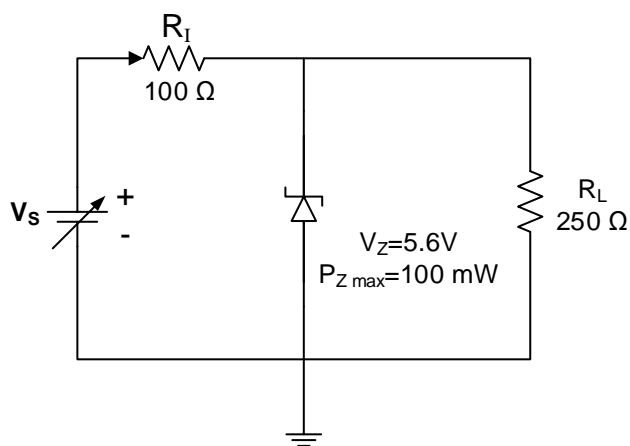

Since $P_Z = V_Z I_Z$ where I_Z is the current through the Zener diode, we have $I_{Z, \text{MAX}} = 100 / 5.6 = 17.86 \text{ mA}$

Since $I_{RL} = 5.6 / 0.250 = 22.4 \text{ mA}$, we have $I_{RI, \text{MAX}} = I_{Z, \text{MAX}} + I_{RL} = 17.86 + 22.4 = 40.26 \text{ mA}$

Therefore, $V_{S, \text{MAX}} = I_{RI, \text{MAX}} R_I + V_Z = 40.26 * 0.1 + 5.6 = 9.63 \text{ V}$

Solution-4 (b):


If the Zener diode is such that a minimum current of 1 mA is required for the Zener action to take place, what is the minimum source voltage V_S that can be used?

When the Zener diode is drawing minimum current, we have $I_{R1\text{ MIN}} = 1 + I_{RL} = 23.4 \text{ mA}$

Therefore, $V_{S\text{ MIN}} = I_{R1\text{ MIN}} R_1 + V_Z = 23.4 \times 0.1 + 5.6 = 7.94 \text{ V}$

Solution-5:

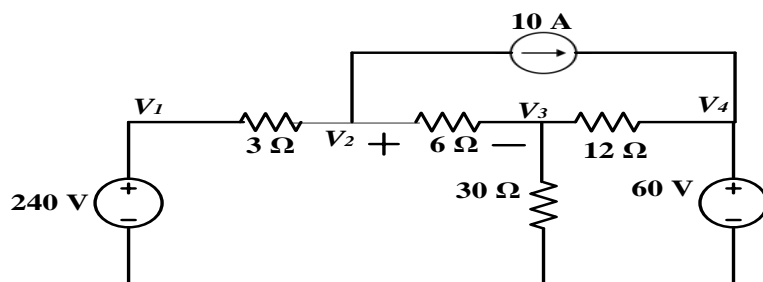The circuit has 4 nodes namely V_1, V_2, V_3 and V_4 apart from the reference node connected to negative terminal of the independent voltage sources.



Using Kirchoff's current law (KCL) at the node V_2 :

$$\frac{V_2 - 240}{3} + \frac{V_2 - V_3}{6} + 10 = 0 \text{ or } 2(V_2 - 240) + V_2 - V_3 + 60 = 0 \text{ giving}$$

$$3V_2 - V_3 - 420 = 0 \quad \dots\dots\dots(1)$$

Using KCL at the node V_3 :

$$\frac{V_3 - V_2}{6} + \frac{V_3}{30} + \frac{V_3 - 60}{12} = 0 \text{ or } 10(V_3 - V_2) + 2V_3 + 5(V_3 - 60) = 0 \text{ giving}$$

$$17V_3 - 10V_2 - 300 = 0 \quad \dots\dots\dots(2)$$

Now, (1) x10 becomes

$$30V_2 - 10V_3 - 4200 = 0 \quad \dots\dots\dots(3)$$

and, (2) x3 gives

$$-30V_2 + 51V_3 - 900 = 0 \quad \dots\dots\dots(4)$$


$$(3)+(4) \text{ becomes } 41V_3 - 5100 = 0 \Rightarrow V_3 = 124.39 \text{ V}$$

Substitution of V_3 in (2) gives $V_2 = 181.46 \text{ V}$

Voltage across the 6Ω resistor is $V_2 - V_3 = 181.46 - 124.39 = 57.07 \text{ V}$ (Ans)

Solution-6:

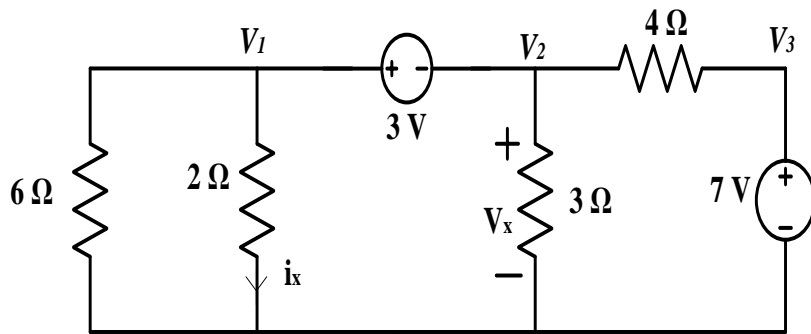V_1, V_2, V_3 are the three nodes apart from the reference node. As a source is connected in between V_1 and V_2 , it forms a **super node**.



Due to the super node V_1-V_2 : $V_1=3+ V_2$ (1)

Applying KCL due to super node $V_1 - V_2$:

$$\frac{V_2-7}{4} + \frac{V_2}{3} + \frac{V_1}{2} + \frac{V_1}{6} = 0$$

OR

$3(V_2 - 7) + 4V_2 + 6V_1 + 2V_1 = 0$ resulting in

$$8V_1 + 7V_2 = 21 \quad \text{.....(2)}$$

Substitution of (1) in (2) gives

$$24 + 8V_2 + 7V_2 = 21$$

$$\Rightarrow V_2 = -0.2$$

Now, (1) gives $V_1 = 2.8$

Therefore, $i_x = V_1/2 = (3+V_2) / 2 = \mathbf{1.4 \text{ A}}$ (Ans)

Lastly, $V_x = V_2 = \mathbf{-0.2 \text{ V}}$ (Ans)