

# Half adder:-

Adds two bits and produces sum and carry

Let the inputs are A and B

outputs are S and C


Half Adder Truth table

INPUTS		OUTPUTS	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\therefore S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = AB$$

Circuit

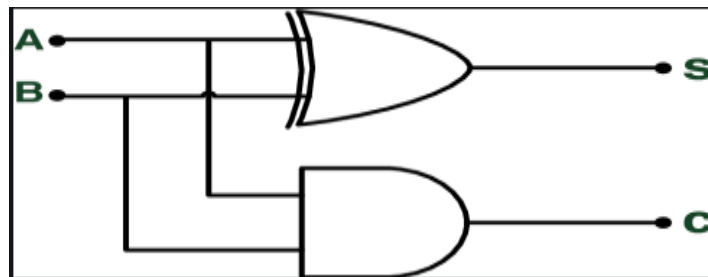

# Full adder


If performs the addition of 3 bits and produces two outputs sum and carry.

Let the inputs are A,B,C and output S and C.

## Truth table

A	B	C	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## Circuit diagram

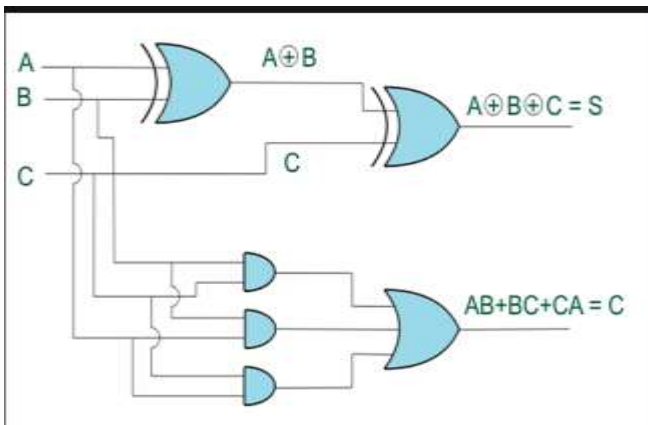

$$\therefore S = \sum m(1, 2, 4, 7)$$

		AB			
		00	01	11	10
C	0	0	①	0	①
	1	①	0	①	0

$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$$

$$= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + B\bar{C})$$

$$= A \oplus B \oplus C$$

$$C = \sum m(3, 5, 6, 7)$$

		AB			
		00	01	11	10
C	0	0	0	①	0
	1	0	①	①	①

$$C = AB + BC + AC$$


# Ripple carry adder

Let  $A = A_3A_2A_1A_0$   
 $B = B_3B_2B_1B_0$

To perform  $A+B$ , 4 full adders are required

$$\begin{array}{r}
 A+B \longrightarrow \quad A_3A_2A_1A_0 \\
 + B_3B_2B_1B_0 \\
 \hline
 C_2C_1C_0C_{in} \\
 \hline
 S_3S_2S_1S_0
 \end{array}$$

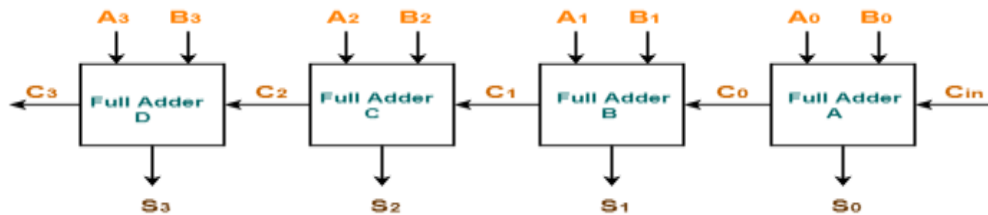The block diagram of 4-bit ripple carry adder is as follows:




## Half Subtractions

If performs subtraction of two bits and produces two outputs difference and borrow.

Let A,B are the inputs and *Difference*, *Borrow* are the outputs

Input		Output	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

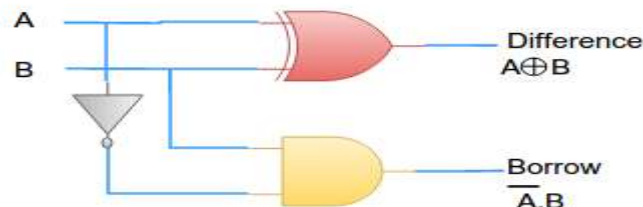
$$\text{Difference} = \bar{A}B + A\bar{B} = A \oplus B \quad \text{Borrow} = \bar{A}B$$



## Full subtractor

- It performs the subtraction of 3-bit and produces difference and borrow.
- Let the inputs are A,B,C and outputs are D and B.

A	B	C	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

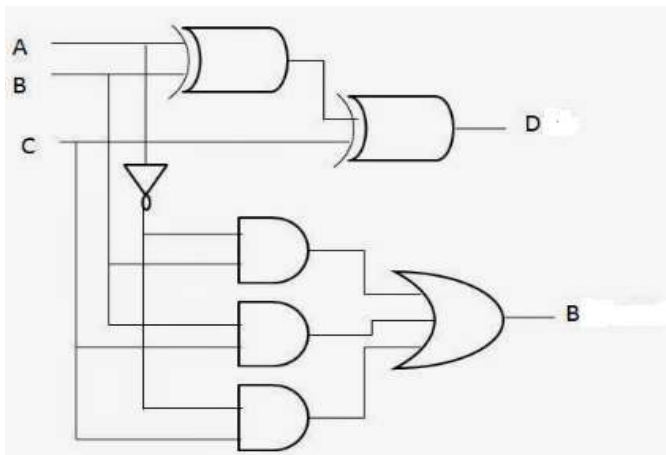

$$\therefore D = \sum m(1, 2, 4, 7)$$

$$= A \oplus B \oplus C$$

$$B = \sum m(1, 2, 3, 7)$$

		AB			
		00	01	11	10
C	0		1		
	1	1	1	1	

$$\therefore B = \bar{A}B + BC + \bar{A}C$$