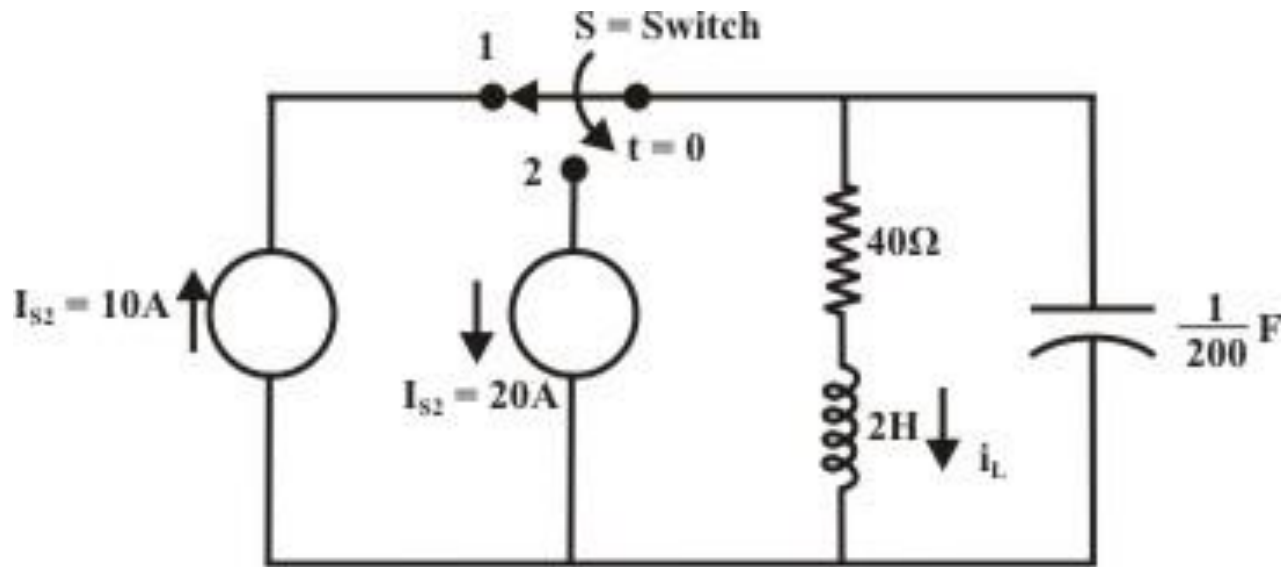


# Lecture 7

Initial Conditions

RLC Circuits

# Initial Conditions




Values for:

(a)  $i_L(0^-)$ ; (b)  $v_c(0^+)$ ; (c)  $v_R(0^+)$ ; (d)  $i_L(\infty)$

Values are 10 A, 400 V, 400 V, -20 A

Before closing the switch, the energy storage elements did not have any stored energy in them. If switch is closed at  $t=0$ , find

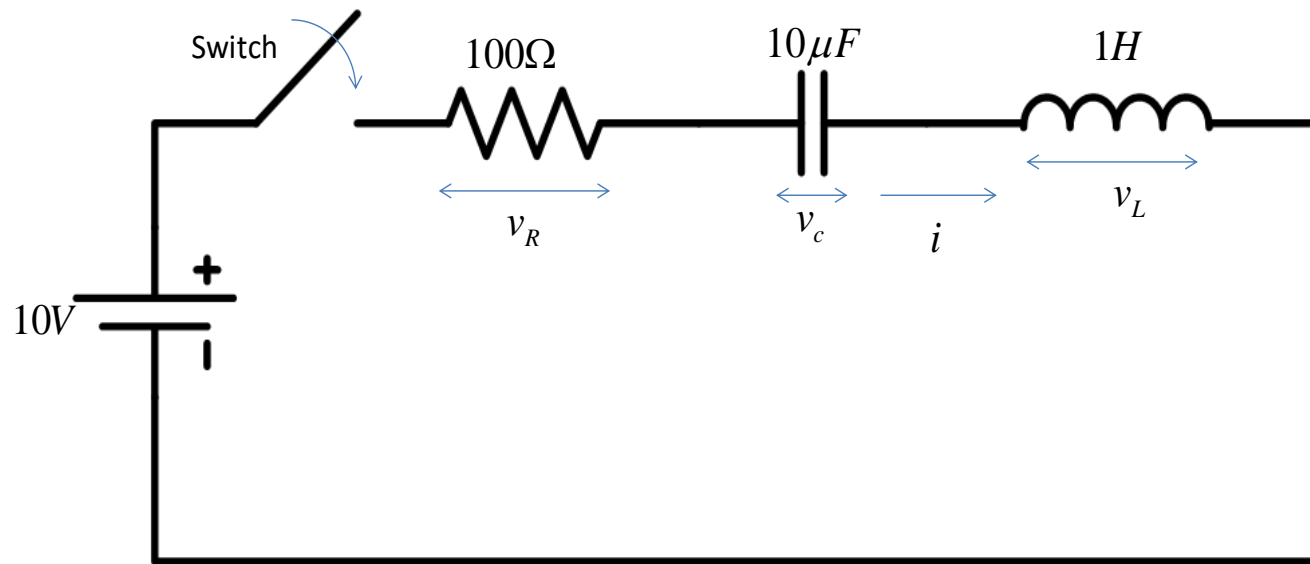
a)  $i(0^+)$  b)  $\frac{di}{dt}(0^+)$  c)  $\frac{d^2i}{dt^2}(0^+)$  d)  $V_L(0^+)$  and e)  $V_c(0^+)$ .



a) 0 A   b) 10 A/s   c) -1000 A/s<sup>2</sup>   d) 10 V   e) 0 V
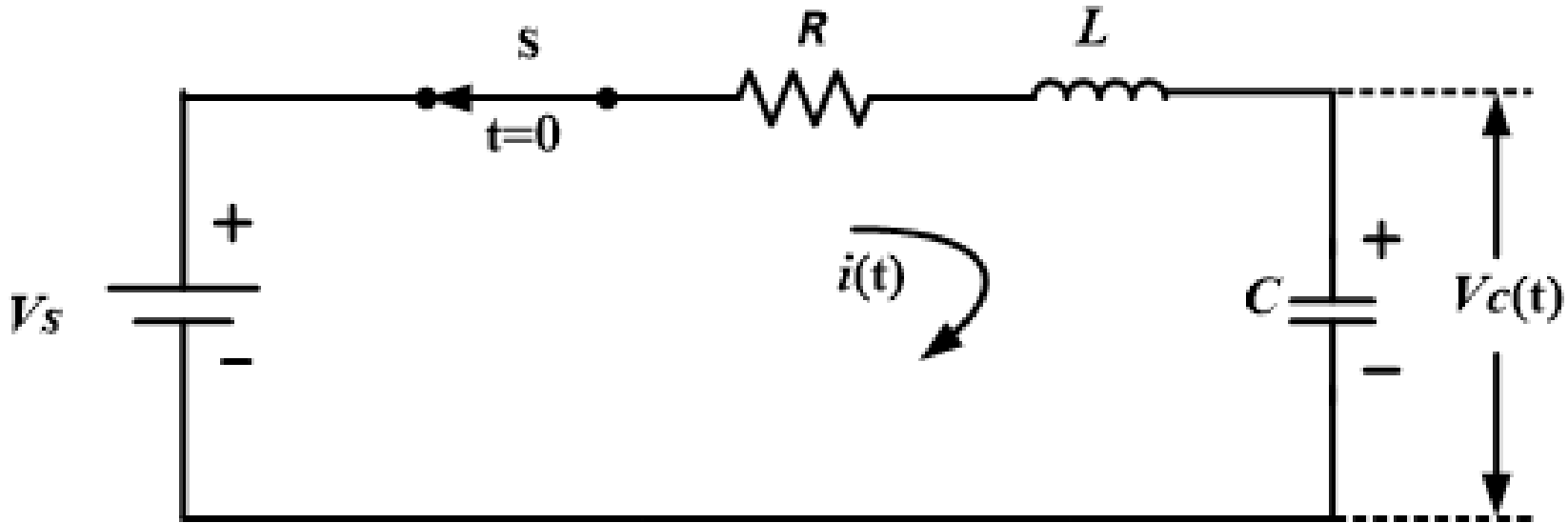
# RLC Circuits

Derive an expression for  $V_c(t)$  for  $t > 0$ .



$$\text{KVL} \Rightarrow L \frac{di(t)}{dt} + R i(t) + v_c(t) = V_s \quad \text{and} \quad i(t) = C \frac{dv_c(t)}{dt}$$

Substitution yields

$$LC \frac{d^2 v_c(t)}{dt^2} + RC \frac{dv_c(t)}{dt} + v_c(t) = V_s$$

Complete solution made of transient and steady state

$$v_c(t) = v_{cn}(t) + v_{cf}(t) = \left( A_1 e^{\alpha_1 t} + A_2 e^{\alpha_2 t} \right) + A$$

To find the natural response, consider the homogeneous diff eqn

$$LC \frac{d^2 v_c(t)}{dt^2} + RC \frac{dv_c(t)}{dt} + v_c(t) = 0$$

$$\Rightarrow \frac{d^2 v_c(t)}{dt^2} + \frac{R}{L} \frac{dv_c(t)}{dt} + \frac{1}{LC} v_c(t) = 0$$

Using  $\alpha = \frac{d}{dt}$ ,  $\alpha^2 = \frac{d^2}{dt^2}$

$$\alpha^2 + \frac{R}{L} \alpha + \frac{1}{LC} = 0 \quad < = \text{Quadratic Equation}$$

# Soln of quadratic equation

$$\alpha_1 = \left( -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \right)$$

$$\alpha_2 = \left( -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \right)$$

# Discriminant positive

$$\text{When } \left( \frac{R}{2L} \right)^2 - \frac{1}{LC} > 0$$

Roots are distinct with NEGATIVE real parts and giving the natural or transient response of the form

$$v_{cn}(t) = A_1 e^{\alpha_1 t} + A_2 e^{\alpha_2 t}$$

## Overdamped Response

# Critically damped Response

$$\text{When } \left( \frac{R}{2L} \right)^2 - \frac{1}{LC} = 0$$

Roots are EQUAL with NEGATIVE real parts and giving the natural or transient response of the form

$$v_{cn}(t) = \left( A_1 t + A_2 \right) e^{\alpha t}$$



# Underdamped Response

$$\text{When } \left(\frac{R}{2L}\right)^2 - \frac{1}{LC} < 0$$

Roots are complex conjugates:

$$\alpha_1 = \left( -\frac{R}{2L} + j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \right) = \beta + j\gamma$$

$$\alpha_2 = \left( -\frac{R}{2L} - j\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} \right) = \beta - j\gamma$$

$$\begin{aligned}
 v_{cn}(t) &= A_1 e^{\alpha_1 t} + A_2 e^{\alpha_2 t} = A_1 e^{(\beta + j\gamma)} + A_2 e^{(\beta - j\gamma)} \\
 &= e^{\beta t} \left[ (A_1 + A_2) \cos(\gamma t) + j(A_1 - A_2) \sin(\gamma t) \right] \\
 &= e^{\beta t} \left[ B_1 \cos(\gamma t) + B_2 \sin(\gamma t) \right] \text{ where } B_1 = A_1 + A_2 ; B_2 = j(A_1 - A_2)
 \end{aligned}$$

Further simplification gives expression for transient response

$$e^{\beta t} K \sin(\gamma t + \theta)$$

$$\text{with } K = \sqrt{B_1^2 + B_2^2} \text{ and } \theta = \tan^{-1} \left( \frac{B_1}{B_2} \right)$$

# Complete solution


$$v_c(t) = v_{cn}(t) + v_{cf}(t) = \left( A_1 e^{\alpha_1 t} + A_2 e^{\alpha_2 t} \right) + A$$

## Three types of Responses

# Initial Conditions

Before closing the switch, the energy storage elements did not have any stored energy in them. If switch is closed at  $t=0$ , find

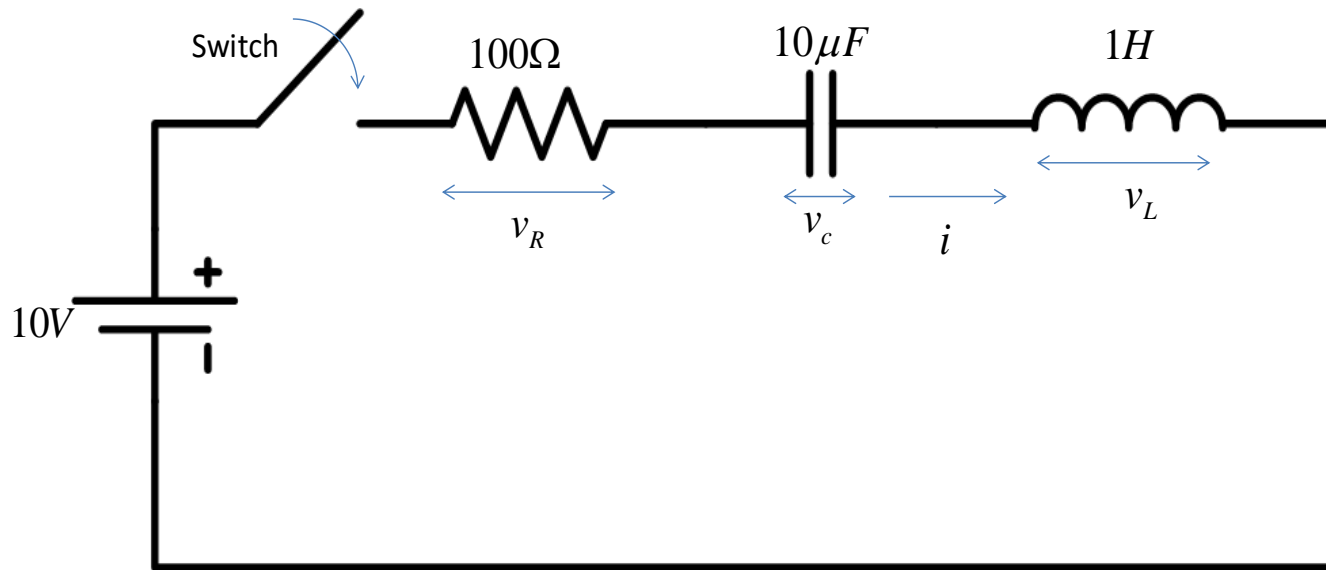
a)  $i(0^+)$  b)  $\frac{di}{dt}(0^+)$  c)  $\frac{d^2i}{dt^2}(0^+)$  d)  $V_L(0^+)$  and e)  $V_c(0^+)$ .



a) 0 A   b) 10 A/s   c) -1000 A/s<sup>2</sup>   d) 10 V   e) 0 V
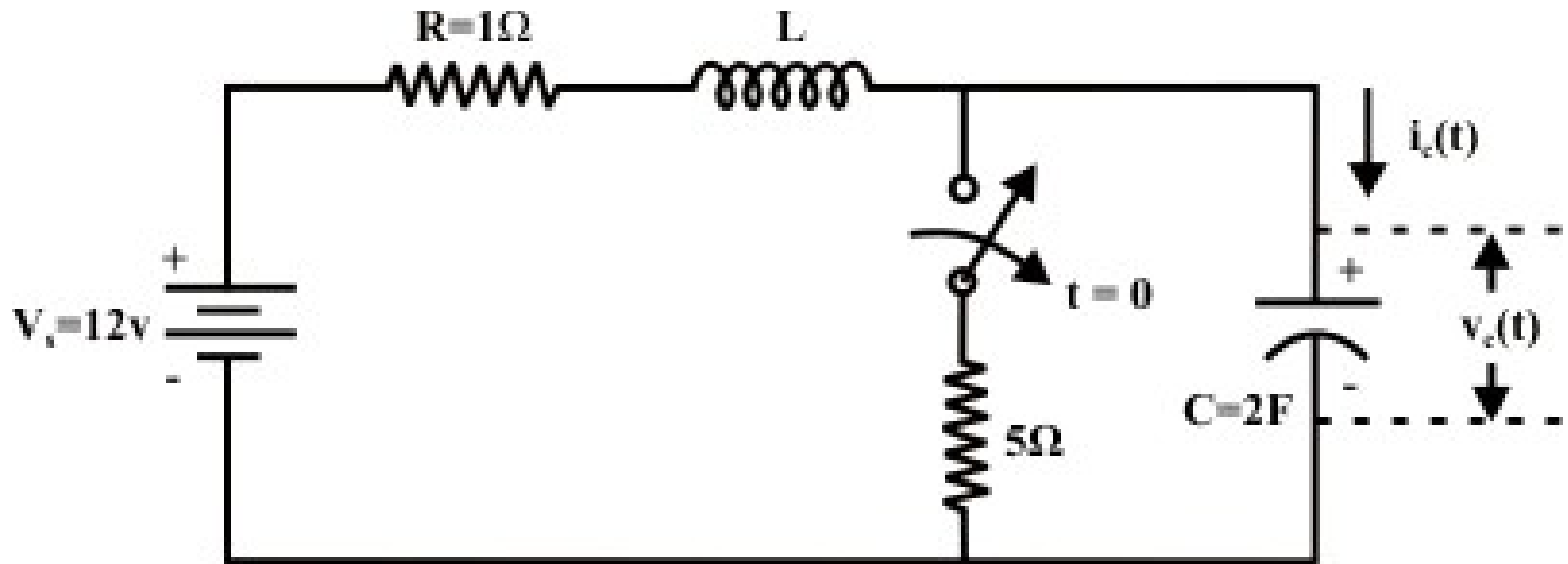
# Example

Switch is closed for a sufficiently long time before opening at  $t=0$ . Find the expression for  $v_c(t)$  and  $i_c(t)$ . Take  $L = 0.2$  H.



# Solution

Initial conditions for the capacitor voltage and inductor current:

$$v_c(0^+) = v_c(0^-) = 10 \text{ V}$$

$$i_L(0^+) = i_L(0^-) = \frac{12}{1+5} = 2 \text{ A}$$

Roots are:

$$\alpha_1 = -0.563; \quad \alpha_2 = -4.436$$

General expression for the capacitor voltage for  $t > 0$  is

$$v_c(t) = A_1 e^{\alpha_1 t} + A_2 e^{\alpha_2 t} + A = A_1 e^{-0.563t} + A_2 e^{-4.436t} + A$$

and

$$\frac{dv_c(t)}{dt} = \alpha_1 A_1 e^{\alpha_1 t} + \alpha_2 A_2 e^{\alpha_2 t} = -0.563 A_1 e^{\alpha_1 t} - 4.436 A_2 e^{\alpha_2 t}$$

Using initial conditions


$$A_1 = -2.032, A_2 = 0.032 \text{ and } A = 12$$

$$v_c(t) = -2.032 e^{-0.563t} + 0.032 e^{-4.436t} + 12$$

$$i_c(t) = C \frac{dv_c(t)}{dt} = 2(1.144e^{-0.563t} - 0.144e^{-4.436t})$$



Draw the plots for capacitor voltage for 20 sec

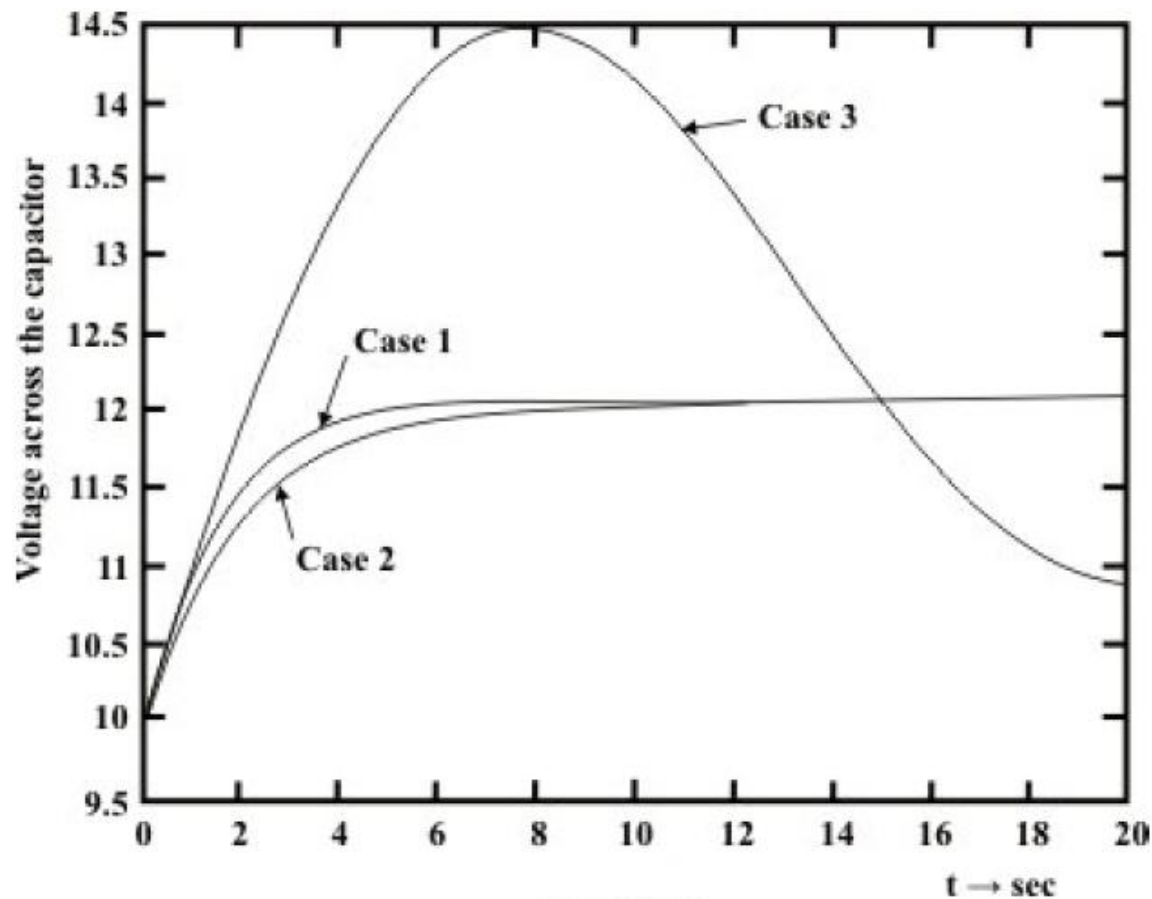


Case 1:  
 $L = 0.5 \text{ H}$

Case 2:  
 $L = 0.2 \text{ H}$

Case 3:  
 $L = 0.8 \text{ H}$

Draw the plots for capacitor current for 20 sec

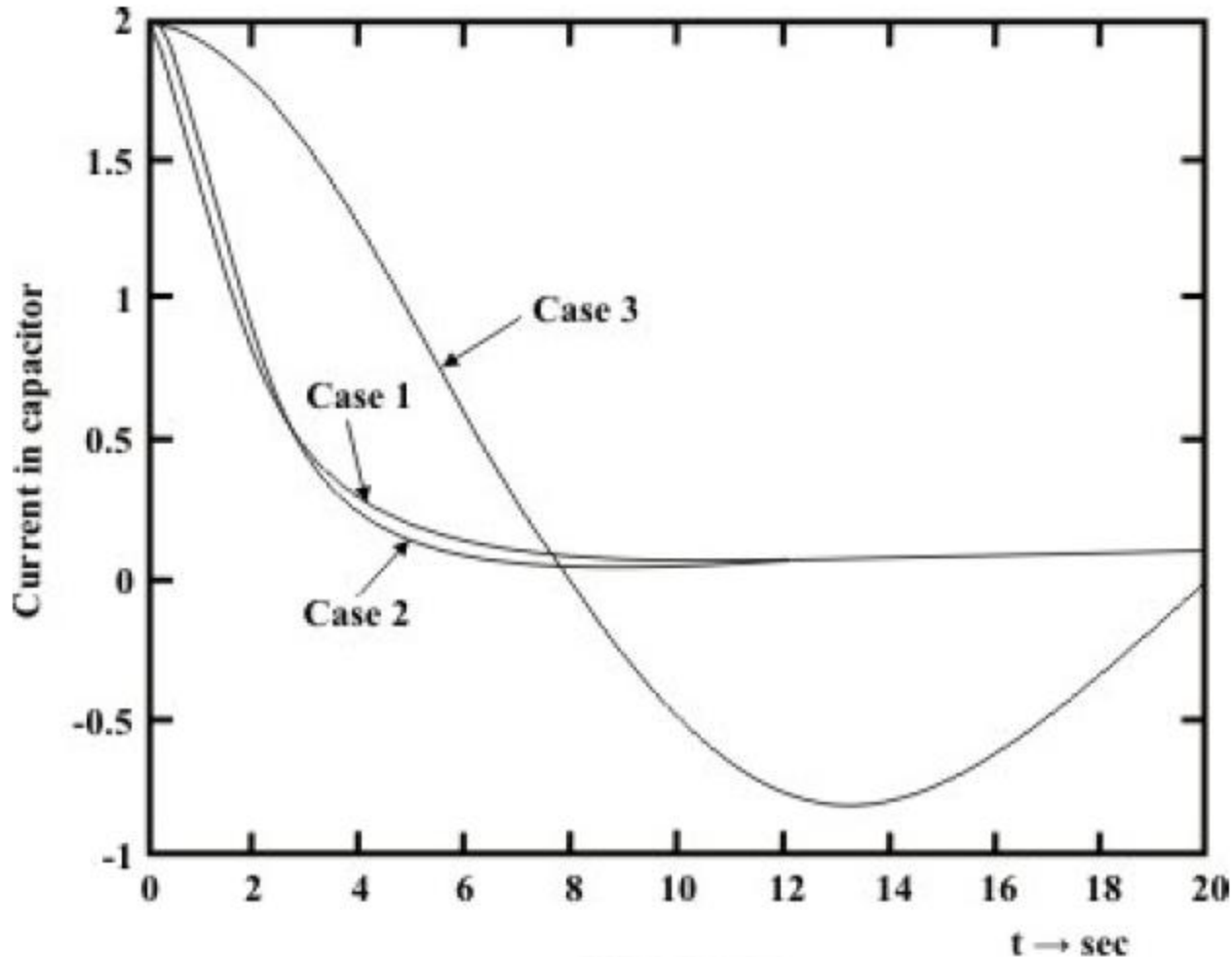

Case 1:  
 $L = 0.5 \text{ H}$

Case 2:  
 $L = 0.2 \text{ H}$

Case 3:  
 $L = 0.8 \text{ H}$