

Lecture 6


Quiz Question+Solution

and

RL and RC Circuits

Quiz Question

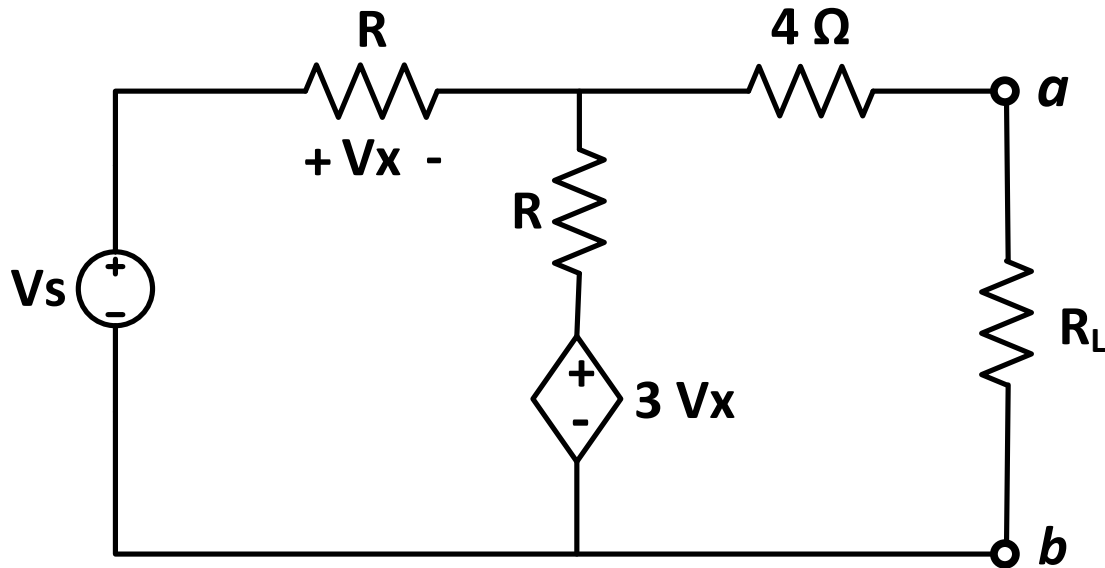Using Thevenin's voltage (V_{th}) and equivalent resistance (R_{th}) across a - b , find maximum power delivered to the load R_L .



Solution


After removing the load resistor R_L , let the mesh current be 'i' in clockwise direction.

Applying KVL in the mesh, one gets $V_s - 4V_x - Ri = 0$.

But, $V_x = Ri$, therefore $V_s - 5Ri = 0$ giving $i = V_s / (5R)$ (1)

$V_{th} = V_{ab} = 3 Ri + Ri = 4Ri = (4/5) V_s = 0.8 V_s$ Volt(2)

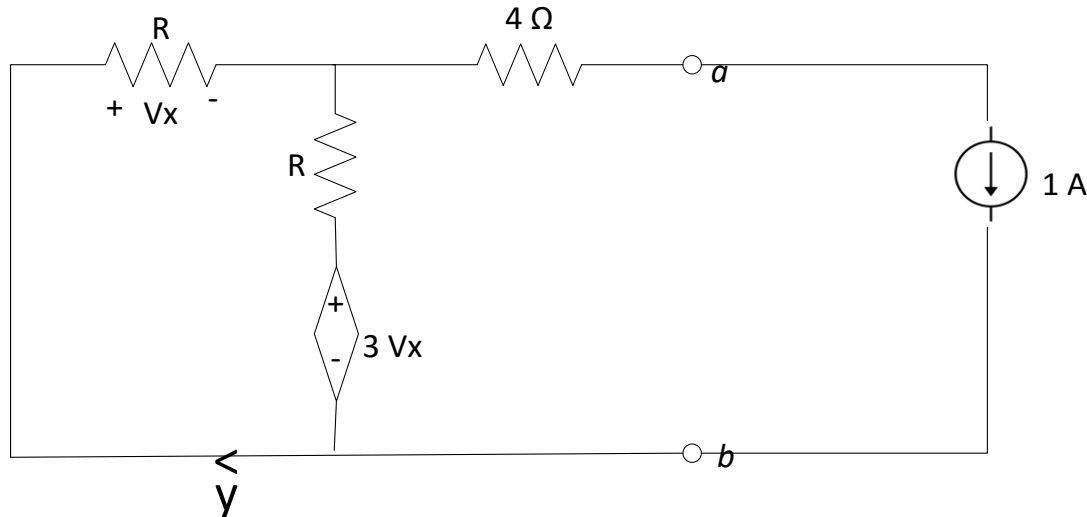The following figure is used to determine equivalent resistance.




Applying KVL in the LHS mesh yields $Ry - (1-y)R + 3 Ry = 0$ giving $y = 0.2$ (3)

Voltage across the externally connected $1A$ source is $V_e = Ry + 4$.


Therefore, from (3) **$R_{eq} = V_e/1 = (0.2R + 4)$ Ohm**(4)

Finally, maximum power delivered, **$P_m = (V_{th})^2/(4R_{eq})$ Watt**(5)

Response of RL Series Circuit

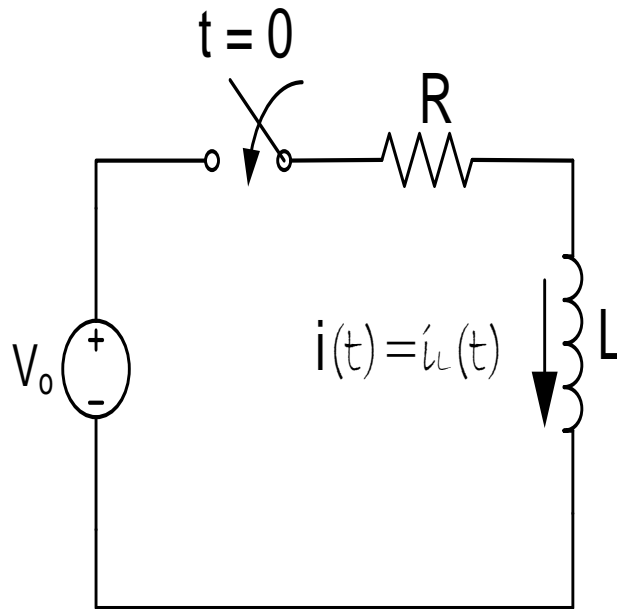

Find $i(t)$

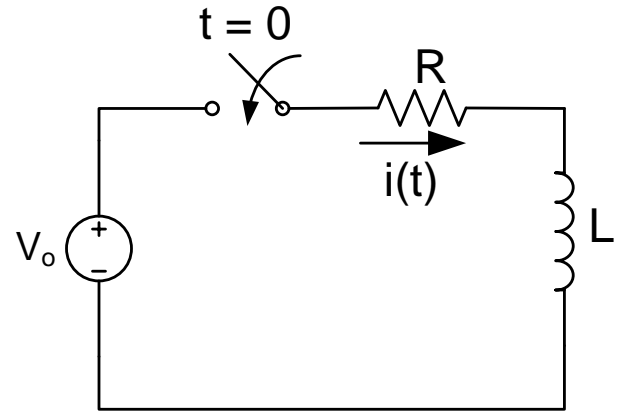

For $t < 0$, $i(t) = 0$

$$Ri + L \frac{di}{dt} = V_0 \quad \text{for } t > 0 \quad \text{and using KVL}$$

$$\text{or, } L \frac{di}{dt} = V_0 - Ri$$

$$\text{or, } \frac{L di}{V_0 - Ri} = dt$$

Integrating, we get

$$\int \frac{L di}{V_0 - Ri} = \int dt$$

$$-\frac{L}{R} \ln(V_0 - Ri) = t + K$$

Integrating, we get

$$\int \frac{L di}{V_0 - Ri} = \int dt$$

$$-\frac{L}{R} \ln(V_0 - Ri) = t + K$$

Setting $i = 0$ at $t = 0$, we have

$$-\frac{L}{R} \ln V_0 = K$$

Hence, we have

$$-\frac{L}{R} \ln(V_0 - Ri) = -\frac{L}{R} \ln V_0 + t$$

$$\text{or, } -\frac{L}{R} \ln\left(\frac{V_0 - Ri}{V_0}\right) = t$$

$$\text{or, } \ln\left(\frac{V_0 - Ri}{V_0}\right) = -\frac{Rt}{L}$$

$$\text{or, } \frac{V_0 - Ri}{V_0} = e^{-\frac{Rt}{L}}$$

$$V_0 - Ri = V_0 e^{-\frac{R}{L}t}$$

$$\text{or, } Ri = V_0 - V_0 e^{-\frac{R}{L}t}$$


$$\text{or, } i = \frac{V_0}{R} - \frac{V_0}{R} e^{-\frac{R}{L}t}$$

The expression for the response for all t is


$$i(t) = \left(\frac{V_0}{R} - \frac{V_0}{R} e^{-\frac{R}{L}t} \right)$$

$$\frac{L}{R} = \tau = \text{Time Constant}$$


Response of R-L Circuit

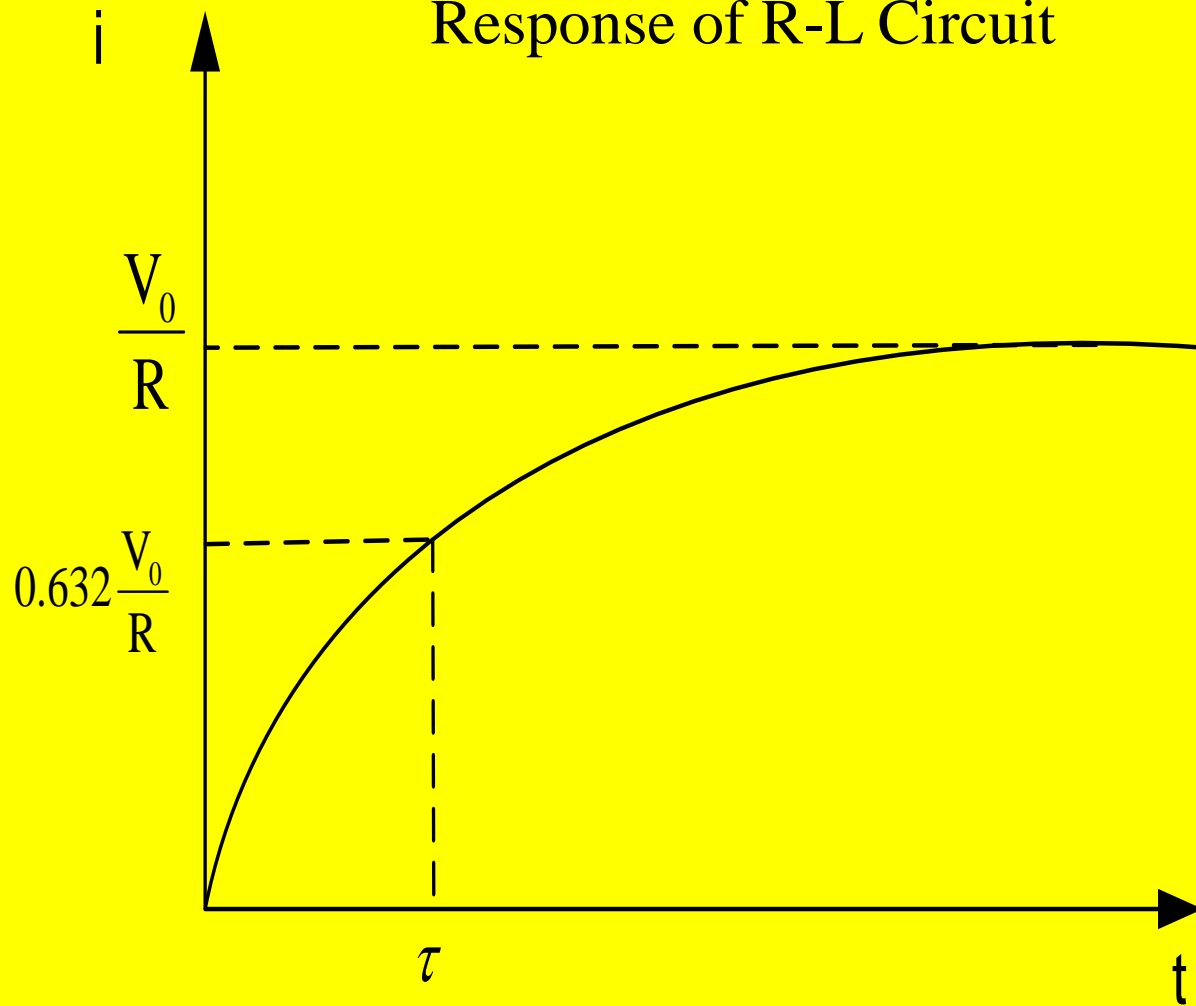

Response of RC Series Circuit

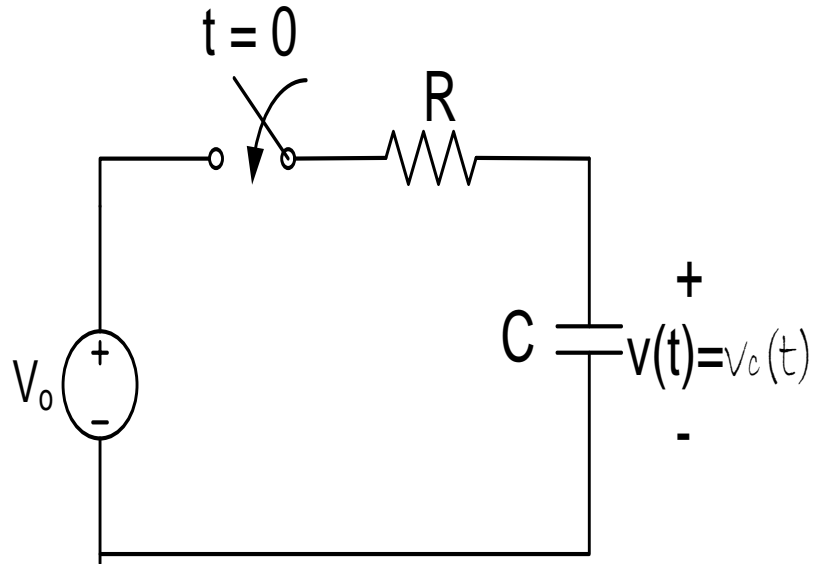

Find $v(t)$

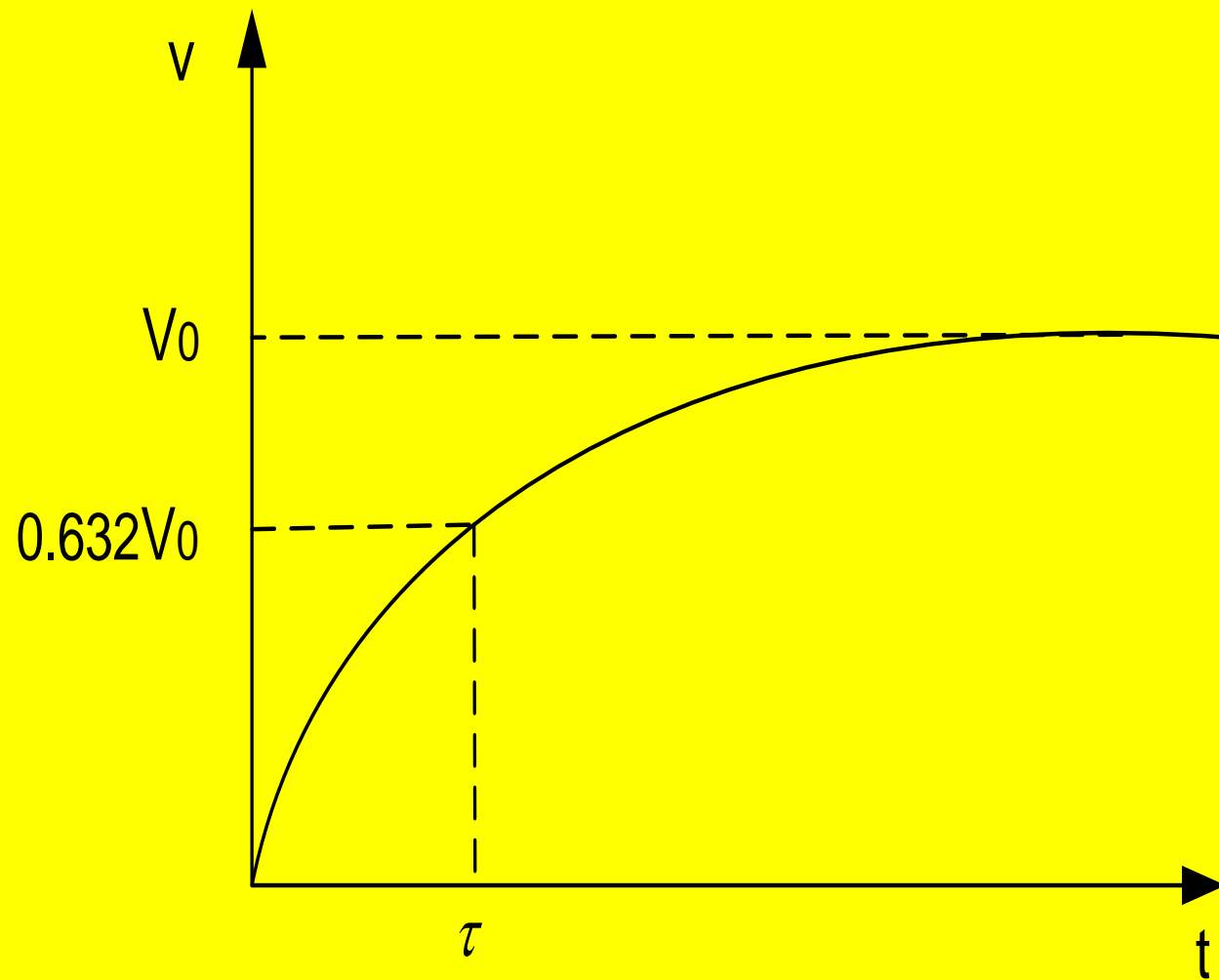

First order Differential Equation: $dx(t)/dt + ax(t) = b$

Can also be written as: $dx(p)/dp + ax(p) = b$

Multiplying both sides by e^{ap} gives:

$$e^{ap} dx(p)/dp + e^{ap} ax(p) = e^{ap} b$$

$$\Rightarrow d(e^{ap} x(p))/dp = e^{ap} b$$

$$\Rightarrow d(e^{ap} x(p)) = e^{ap} b dp$$

$$\Rightarrow \int_0^t d(e^{ap} x(p)) = \int_0^t e^{ap} b dp$$

$$\Rightarrow e^{ap} x(p) \big|_o^t = (b/a) e^{ap} \big|_o^t$$

Substitution of limits of integral $\Rightarrow e^{at} x(t) - x(0) = (b/a) (e^{at} - 1)$

$$\Rightarrow e^{at} x(t) = x(0) + (b/a) (e^{at} - 1)$$

Multiplying both sides of above equation by e^{-at}

$$\Rightarrow x(t) = e^{-at} x(0) + (b/a) (1 - e^{-at})$$

$$= (x(0) - b/a) e^{-at} + b/a$$

Solution of first order DE $\dot{x}(t) + ax(t) = b$ is

$$x(t) = [x(0) - (b/a)] e^{-at} + (b/a)$$


For series RL circuit : $x(t) = i(t)$, $a = R/L$ and $b = V_0/L$

$$\text{So, } i_L(t) = [i(0) - (V_0/R)] e^{-Rt/L} + (V_0/R)$$

For series RC circuit : $x(t) = v(t)$, $a = 1/(RC)$ and $b = V_0/(RC)$

$$\text{Then, } v_c(t) = [v_c(0) - V_0] e^{-t/(RC)} + V_0$$

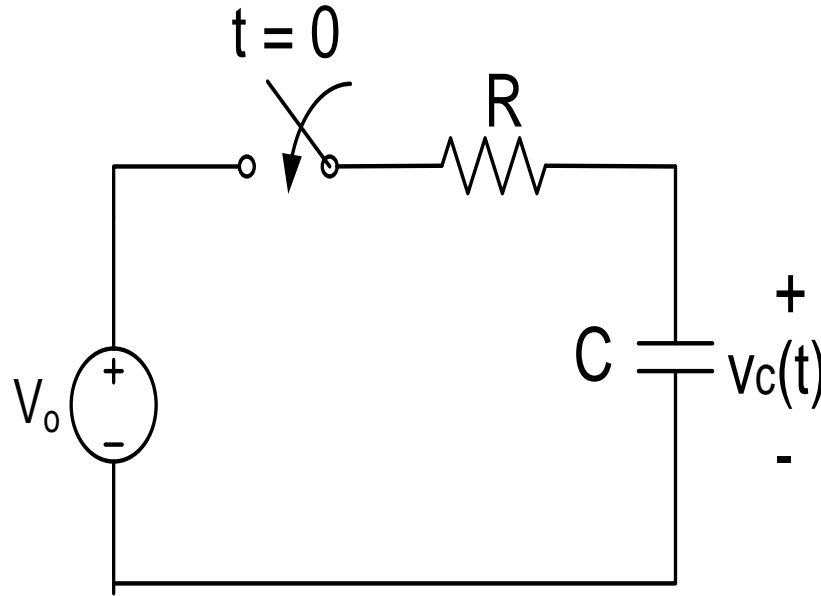
Determine and plot voltage $v_c(t)$ across the capacitor for $0 \leq t \leq 2$ sec.



$$V_0 = 12 \text{ V}, R = 1 \text{ k}\Omega, C = 470 \text{ }\mu\text{F}$$
$$\text{and } v_c(0) = 5 \text{ V}$$

$$v_c(t) = [v_c(0) - V_0] e^{-t/(RC)} + V_0 = (-7) e^{-t/0.47} + 12$$

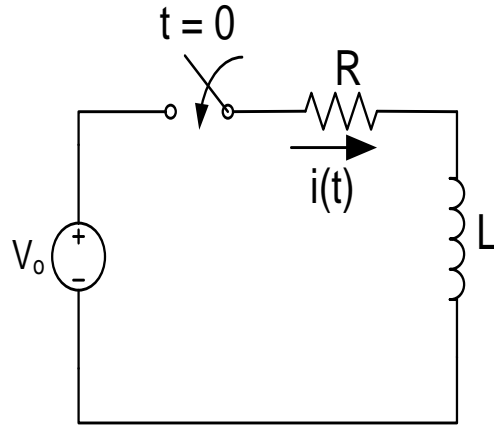
Determine and plot inductor current $i_L(t)$ for $t \leq 0.1$ sec.



$$V_0 = 100 \text{ V}, R = 8\Omega, L = 0.2 \text{ H}$$

$$i_L(t) = [0 - 12.5] e^{-40t} + 12.5 = 12.5(1 - e^{-40t})$$

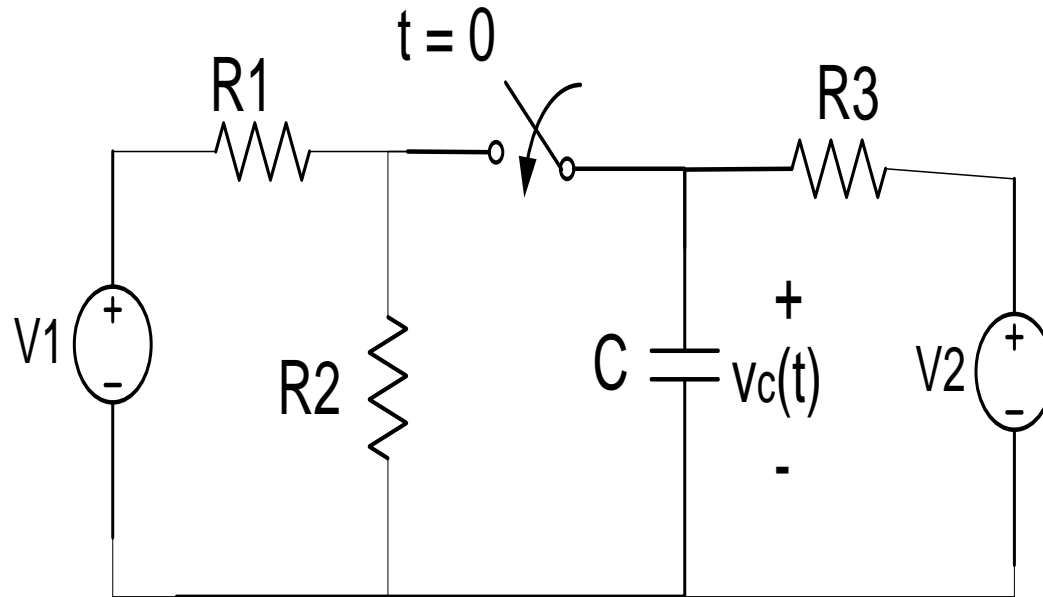Find expression for $V_c(t)$ for $t > 0$.



$$V_c(0) = V_2, R_{th} = R_1 || R_2 || R_3, V_0 = V_{th} = R_{th}(V_1/R_1 + V_2/R_3)$$

Feedback

- Go slow
- Move faster
- More examples
- Tutorial problems (easy/tough)