

SOLUTIONS

Solution of pre-tutorial:

1. Single phase motors are not able to start by themselves. This requires a polyphase source. 3-phase generators, motors and transformers are simpler, cheaper and more efficient. 3-phase transmission lines deliver more power for a given cost or for a given weight of conductor. Voltage regulation of a 3-phase system is inherently better. In case of star-connected source, the line voltage is $\sqrt{3}$ times the phase voltage. This helps in transmitting and distributing power with a higher voltage. The number of conductors required for transmission and distribution is reduced thus helps reducing the cost in case of a balanced three-phase system.

$$v_{ab} = v_{an} - v_{bn}$$

$$= V_p \angle 20^\circ - V_p \angle -100^\circ$$

$$= V_p \sin(\omega t + 20^\circ) - V_p \sin(\omega t - 100^\circ)$$

$$= V_p \times 2 \sin\left(\frac{\omega t + 20^\circ - \omega t + 100^\circ}{2}\right) \cos \frac{\omega t + 20^\circ + \omega t - 100^\circ}{2}$$

$$= V_p \times 2 \sin(60^\circ) \cos(\omega t - 40^\circ)$$

$$= \sqrt{3}V_p \cos(\omega t - 40^\circ)$$

$$= \sqrt{3}V_p \cos(90^\circ - (\omega t + 50^\circ))$$

$$= \sqrt{3}V_p \sin(\omega t + 50^\circ)$$

$$v_{ab} = \sqrt{3}V_p \sin(\omega t + 50^\circ) = V_L \angle 50^\circ$$

$$v_{bc} = \sqrt{3}V_p \sin(\omega t - 70^\circ) = V_L \angle -70^\circ$$

$$v_{ca} = \sqrt{3}V_p \sin(\omega t - 190^\circ) = V_L \angle -190^\circ$$

2.

(a) $Z_P = 12 + j5 \Omega$

$$I_{bB} = 20 \angle 0^\circ$$

P.F. angle = $\cos^{-1}(0.935) = 20.770^\circ$

$$\tan^{-1}\left(\frac{5}{12+R_w}\right) = 20.77^\circ \Rightarrow \frac{5}{12+R_w} = 0.38 \Rightarrow 13.18 = 12 + R_w$$

$$\Rightarrow R_w = 1.18 \Omega$$

(b) $V_{bn} = I_{bB}(Z_P + R_w) = 20 \angle 0^\circ (12 + j5 + 1.18) = 20 (13.18 + j5)$
 $= 263.6 + j100 = 282 \angle 20.77^\circ \text{ V}$

(c) $V_{BN} = I_{bB}(Z_P) = 20 \angle 0^\circ (12 + j5) = 260 \angle 22.62^\circ \text{ V}$
 $V_{BC} = \sqrt{3} V_{BN} \angle 30^\circ = 450.33 \angle 52.62^\circ$

$$V_{AB} = V_{BC} \angle 120^\circ = 450.33 \angle 172.62^\circ \text{ V}$$

(d) Line voltage at the source $V_L = \sqrt{3} |V_{bn}| = 488.44 \text{ V}$, $I_L = |I_{bB}| = 20$

Total apparent power supplied by the source = $\sqrt{3} V_L I_L = 16.92 \text{ KVA}$

3.

(a) V_{cn} , is the phase voltage.

$$\text{So, } V_{cn} = \frac{400}{\sqrt{3}} \angle -270^\circ = 230.94 \angle -270^\circ \text{ V}$$

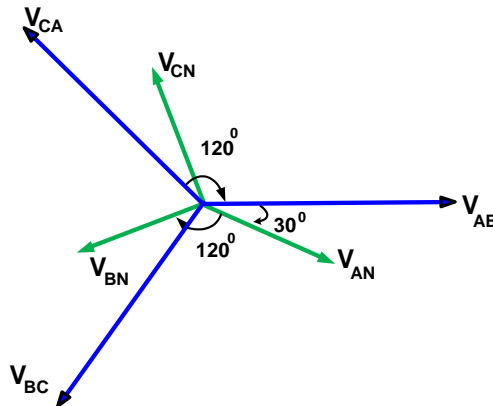


Fig. Q1



$$(b) Z_{AN} = (-j100) || (100) || (50 + j50)$$

$$= \frac{-j100 \times 100 \times (50 + j50)}{-j100 \times 100 + 100(50 + j50) - j100 \times (50 + j50)} = 50 \Omega$$

$$I_{aA} = \frac{230.94 \angle -30^\circ}{50} = 4.62 \angle -30^\circ \text{ A}$$

$$(c) \text{ Real power drawn by the load is } = 3 \times V_{ph} \times I_{ph} = 3.2 \text{ kW}$$


4.

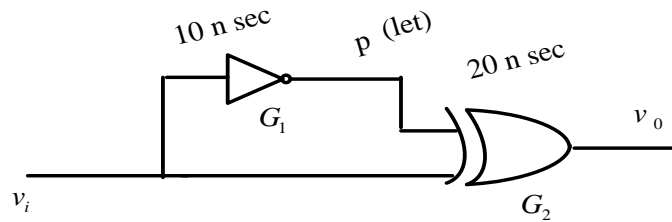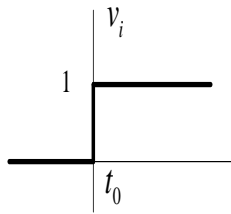


$$\text{Let } t_1 = t_0 + 10 \text{ nsec}$$

$$t_2 = t_0 + 20 \text{ nsec}$$


$$t_3 = t_0 + 30 \text{ nsec}$$

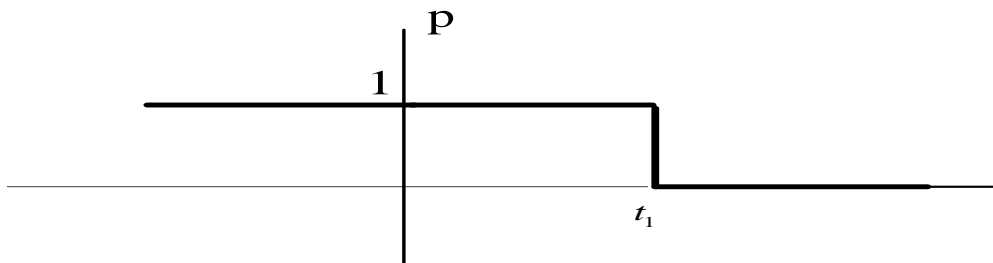

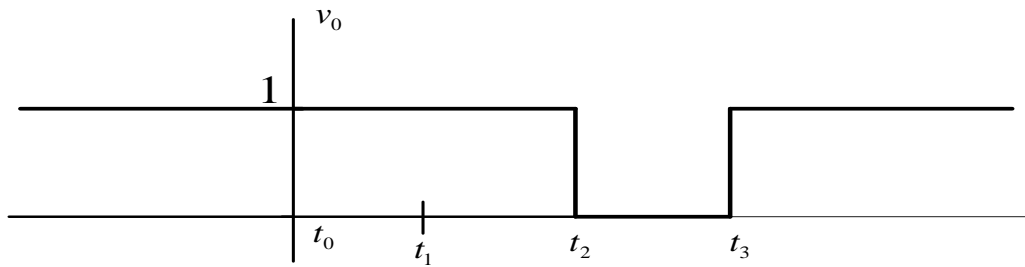v_o at $t = t_0$ depends on the inputs of G_2 at $t = t_0 - 20 \text{ nsec}$, at $t = t_1$ depends on inputs $t = t_1 - 20 \text{ nsec}$ and so on



5. NOT Gate Implementation :

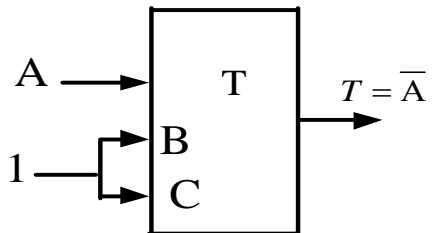


XOR gate:


$$T = ABC\overline{C} + A\overline{B}C + \overline{A}BC$$

$$= A[B \oplus C] + \overline{A}BC$$

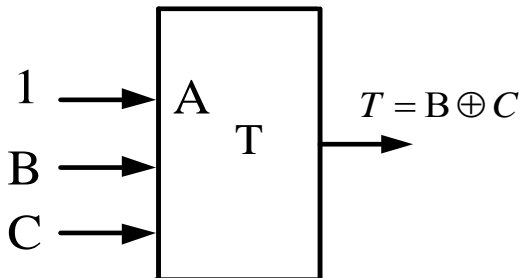
$$\text{if } A=1 \Rightarrow T = B \oplus C$$



AND Gate

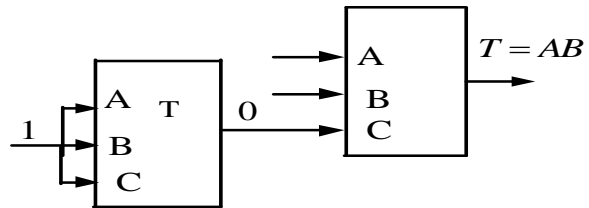

OR Gate:

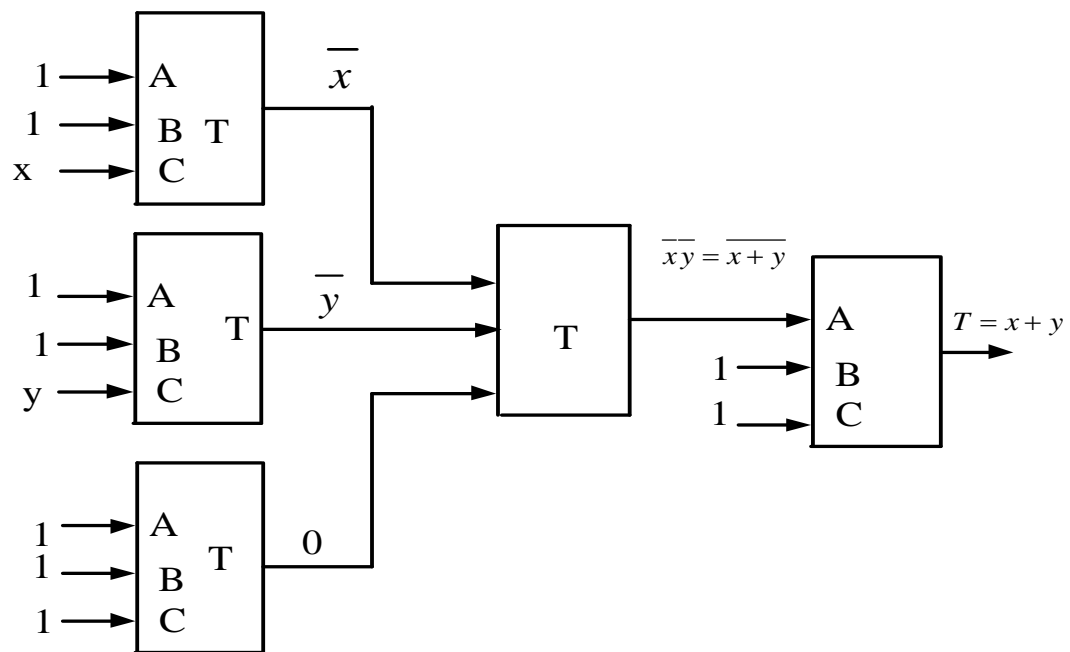

- T Gate plus the logical value 1 act as a universal gate.