

## SOLUTIONS

### Solution of pre-tutorial:

Let the output be 'P'

x	y	z	P
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned}\therefore P &= \bar{x}yz + x\bar{y}z + xy\bar{z} + xyz \\ &= \bar{x}yz + x\bar{y}z + xy(z + \bar{z}) \\ &= \bar{x}yz + x[y + \bar{y}z] \\ &= \bar{x}yz + xy + xz \\ &= z(x + \bar{x}y) + xy \\ &= xy + yz + zx\end{aligned}$$


### Solution of problem 2:

From the timing diagram, we obtain the truth table as follows.


A	B	C	f
0	0	0	1
1	1	1	0
0	1	1	0
1	0	1	1
0	1	0	0
0	0	1	1
1	0	0	0
1	1	0	0

$$\begin{aligned}\therefore f &= \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C \\ &= \bar{A}\bar{B}[C + \bar{C}] + A\bar{B}C \\ &= \bar{B}[\bar{A} + AC] \\ &= \bar{B}[(\bar{A} + A)(\bar{A} + C)] \\ &= \bar{A}\bar{B} + \bar{B}C\end{aligned}$$


### Implementation using basic gates

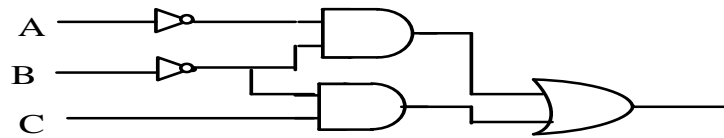
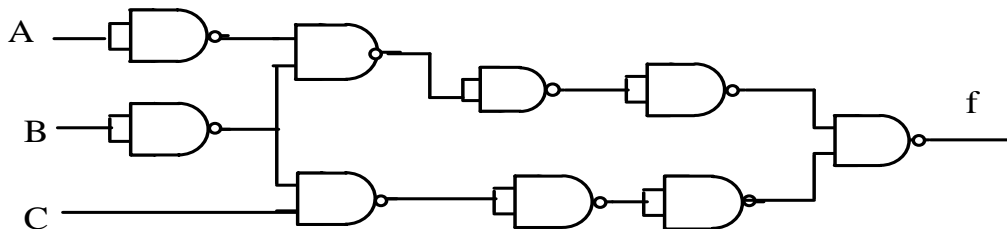
### Implementation using two input NAND gates



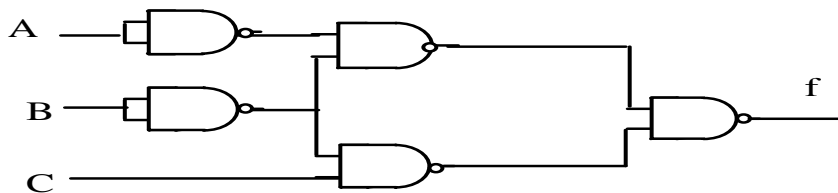By removing all the groups of two series NOT gates, we get



### **Solution of problem 3:**

$$(a) \quad v = A+B+E$$

$$w=C$$

$$x=A+D$$

$$y=B+C$$

$$z=D+E$$

For the safe to be opened  $f(A,B,C,D,E)=v w x y z=1$

$$f(A,B,C,D,E)=(A+B+E)C(A+D)(B+C)(D+E)$$

$$= (AC+BC+CE)(A+D)(BD+BE+CD+CE)$$

$$= (AC+ACD+ABC+BCD+ACE+CDE)(BD+BE+CD+CE)$$

$$= (AC+BCD+CDE)(BD+BE+CD+CE)$$

$$= ABCD+ABCE+ACD+ACE+BCD+BCDE+BCD+BCDE+BCDE+BCDE+CDE+CDE$$

$$= ACD+ACE+BCD+CDE$$

From the above Boolean expression, it is clear that a minimum of three executives are required to open the safe.

(b). The combinations of three executives required to open the safe are  $ACD$ ,  $ACE$ ,  $BCD$  and  $CDE$ .

(c). As all the combinations contain  $C$ , the “essential executive” is  $C$ .

#### Solution of problem 4:

The apparent power drawn by the load  $= \frac{1200 \text{ W}}{0.8} = 1500 \text{ VA}$

$$3 \times |V_{ph}| \times |I_{ph}| = 1500 \text{ VA}$$

$$\Rightarrow |I_{ph}| = \frac{1500}{3 \times \frac{300}{\sqrt{3}}} = 2.886 \text{ A}$$

$$\text{Magnitude of phase impedance} = \frac{|V_{ph}|}{|I_{ph}|} = \frac{\frac{300}{\sqrt{3}}}{2.886} = 60 \Omega$$

$$\begin{aligned} \text{Phase impedance} &= \mathbf{Z}_{ph} = 60 \angle \theta = 60 \times \cos \theta + j60 \times \sin \theta = 60 \times 0.8 + j60 \times 0.6 \\ &= 48 + j36 \Omega \end{aligned}$$

#### Solution of problem 5:

The wattmeter  $\mathbf{W}_1$  is connected between lines A and C, it will show

$$\mathbf{W}_1 = V_{AC} I_A \cos(30^\circ - \theta) = V_L I_L \cos(30^\circ - \theta)$$

The wattmeter  $\mathbf{W}_2$  is connected between lines B and C, it will show

$$\mathbf{W}_2 = V_{BC} I_B \cos(30^\circ + \theta) = V_L I_L \cos(30^\circ + \theta)$$

Hence,  $\mathbf{W}_1 > \mathbf{W}_2$ . So,  $\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = \tan(\theta)$ , where  $\theta$  is the p.f. angle.

$$\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = \tan(\cos^{-1}(0.8)) \Rightarrow \mathbf{W}_2 = 5.93 \text{ kW}$$

**(a)** Real power consumed by the load =  $W_1 + W_2 = \sqrt{3} |V_L| \times |I_L| \cos(\theta) = 20.93 \text{ kW}$

$$\Rightarrow |V_L| = 503.5 \text{ V}$$

**(b)** Load resistance per phase =  $R_{ph} = \frac{\text{real power consumed}}{|I_L|^2} = \frac{20.93 \text{ kW}}{30^2} = 23.25 \Omega$

**(c)** Load reactance per phase =  $X_{ph} = \frac{\text{reactive power consumed}}{|I_L|^2} = \frac{\sqrt{3}(W_1 - W_2)}{|I_L|^2} = \frac{15.71 \text{ kVA}}{30^2} =$   
 $= 17.455 \Omega$