


Lecture 10

AC Power

Power Factor Improvement

EXAMPLE

Estimate real, reactive powers and pf

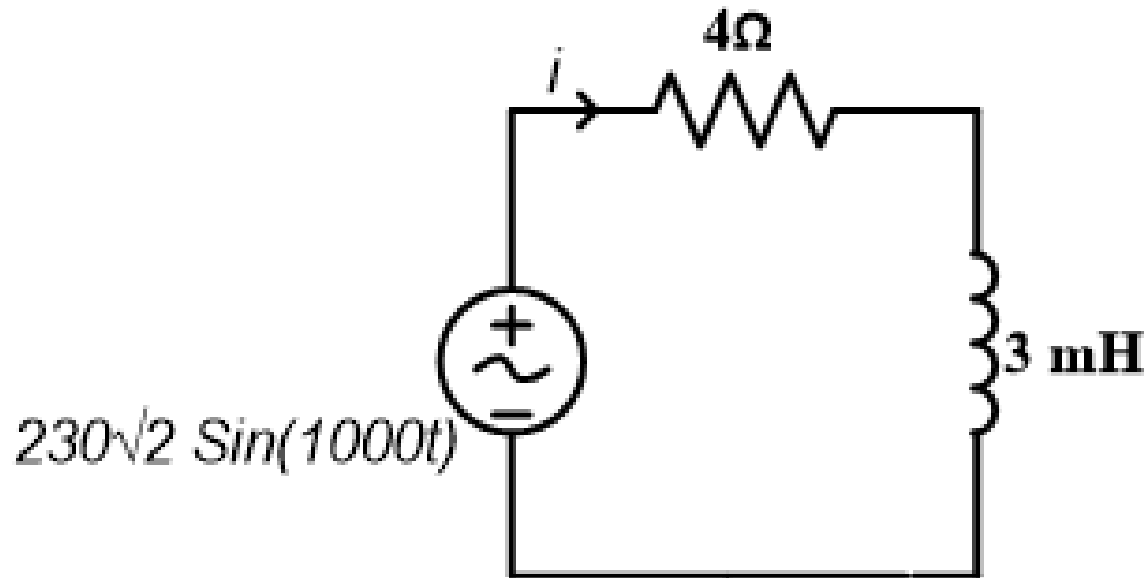

Given, $V_m \angle \theta = 230\sqrt{2} \angle 0^\circ$, $Z = 4 + j3 = 5 \angle \tan^{-1}(3/4) = 5 \angle 36.87^\circ$

Then, $I_m \angle \phi = 230\sqrt{2} \angle 0 / 5 \angle 36.87^\circ = 46\sqrt{2} \angle -36.87^\circ$

$$\theta = 0^\circ \text{ but } \phi = -36.87^\circ \Rightarrow \theta - \phi = 36.87^\circ$$

$$\text{Power Factor} = \cos(\theta - \phi) = \cos(36.87^\circ) = 0.8 \text{ lagging}$$

$$\begin{aligned} \text{Real Power, } P &= \frac{1}{2} \times 230 \sqrt{2} \times 46 \sqrt{2} \cos(36.87^\circ) \\ &= V \times I \times \cos(36.87^\circ) = 230 \times 46 \times 0.8 = 8464 \text{ W} \end{aligned}$$

$$\text{Real power} = P = I^2 R = 46 \times 46 \times 4 = 8464 \text{ W}$$



$$\begin{aligned} \text{Apparent Power } |S| &= V \times I = P / \cos(\theta - \phi) = 10580 \text{ VA} \\ \text{Also, } |S| &= V \times I = 230 \times 46 = 10580 \text{ VA} \end{aligned}$$

$$\begin{aligned} \text{Reactive Power } Q &= V \times I \times \sin(36.87^\circ) = 6348 \text{ VAR} \\ \text{Also, } P \times \tan(\theta - \phi) &= 8464 \times 0.75 = 6348 \text{ VAR} \end{aligned}$$



$$\text{Reactive power} = Q = I^2 X_L = 46 \times 46 \times 3 = 6348 \text{ W}$$

Power Factor Improvement

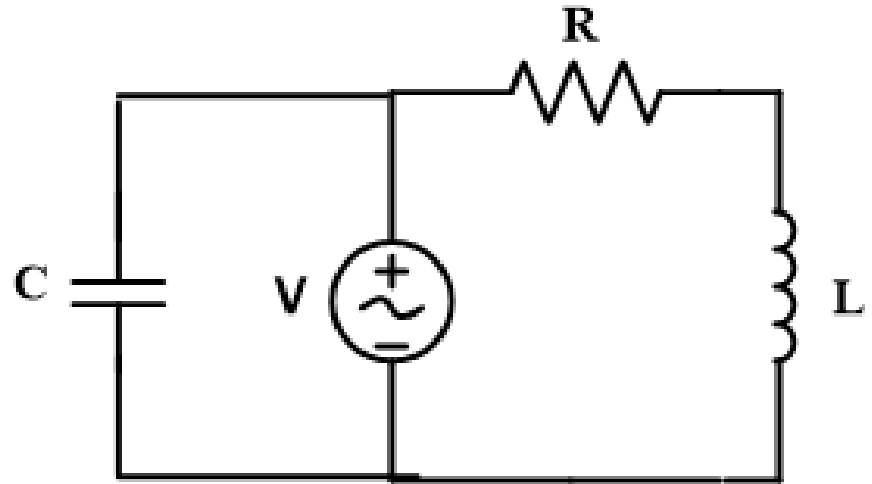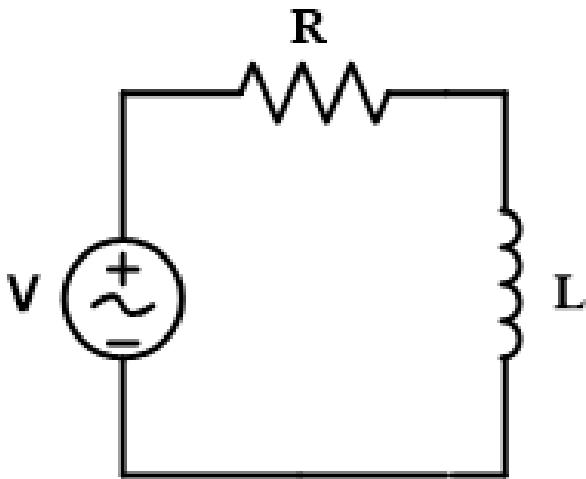Power Factor to be 0.9 lagging from 0.8 lagging




Power Factor Improvement

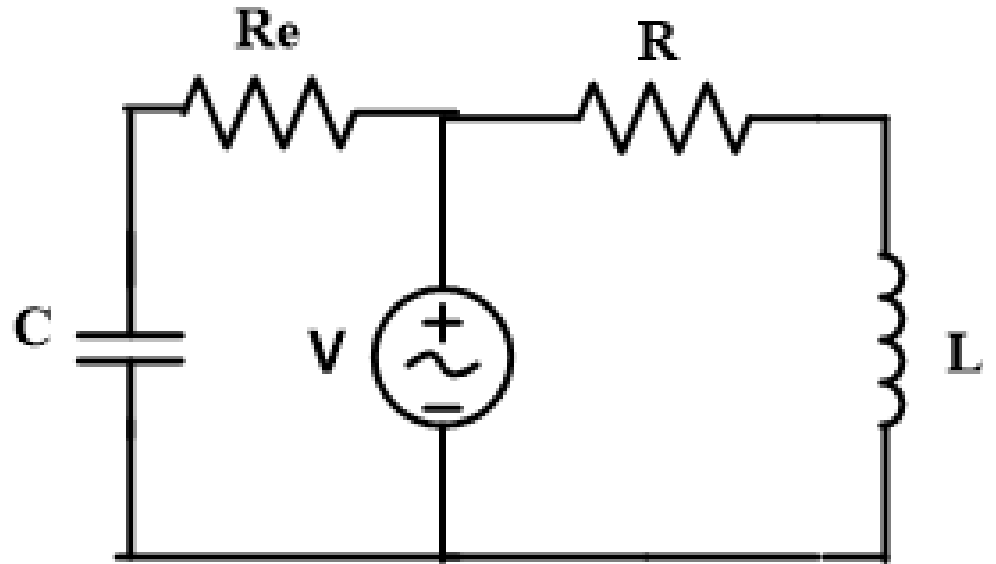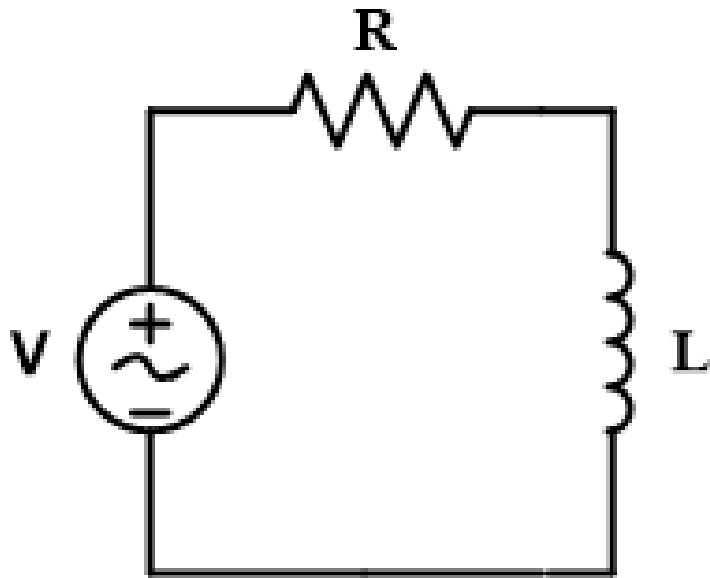

Power Factor Improvement
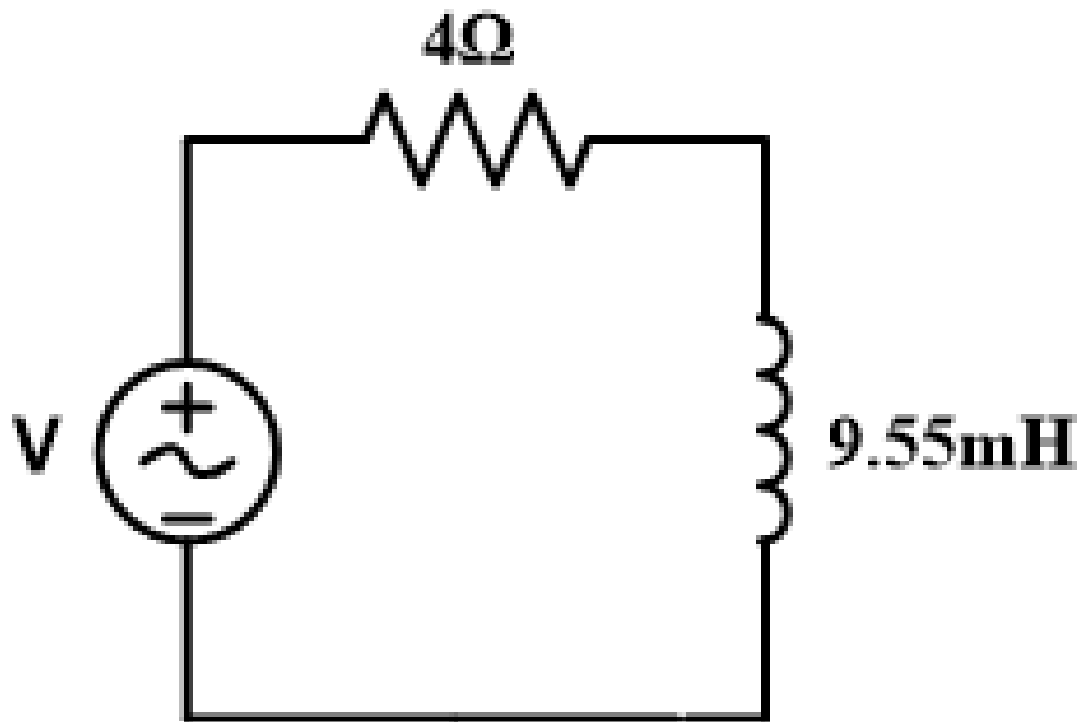
$$v = 20\sqrt{2} \sin(\omega t) \quad \text{where } f = 50 \text{ Hz}$$



Power
Factor to
be 0.9
lagging

Given values in rms:

$$V = 20 \angle 0^\circ \text{ and } Z = 4 + j3 = 5 \angle 36.87^\circ$$

$$\text{Then, } I = V/Z = 4 \angle -36.87^\circ$$

The power factor angle is: $\theta - \phi = 36.87^\circ$

PF is: $\cos(0 - (-36.87^\circ)) = \mathbf{0.8 \text{ lagging.}}$

$$\text{Real power} = P = I^2 R = VI \cos(36.87^\circ) = 20 \times 4 \times 0.8 = 64 \text{ W}$$

$$\text{Reactive power} = Q = I^2 X_L = VI \sin(36.87^\circ) = 48 \text{ VAR}$$


For Power Factor to be 0.9 lagging

Real power remains same $\Rightarrow VI = 64/0.9 = 71.11 \text{ VA}$

$$\cos(\phi_n) = 0.9 \Rightarrow \phi_n = 25.84^\circ$$

Reactive power has to be $\Rightarrow VI \sin(25.84^\circ) = 31 \text{ VAR}$

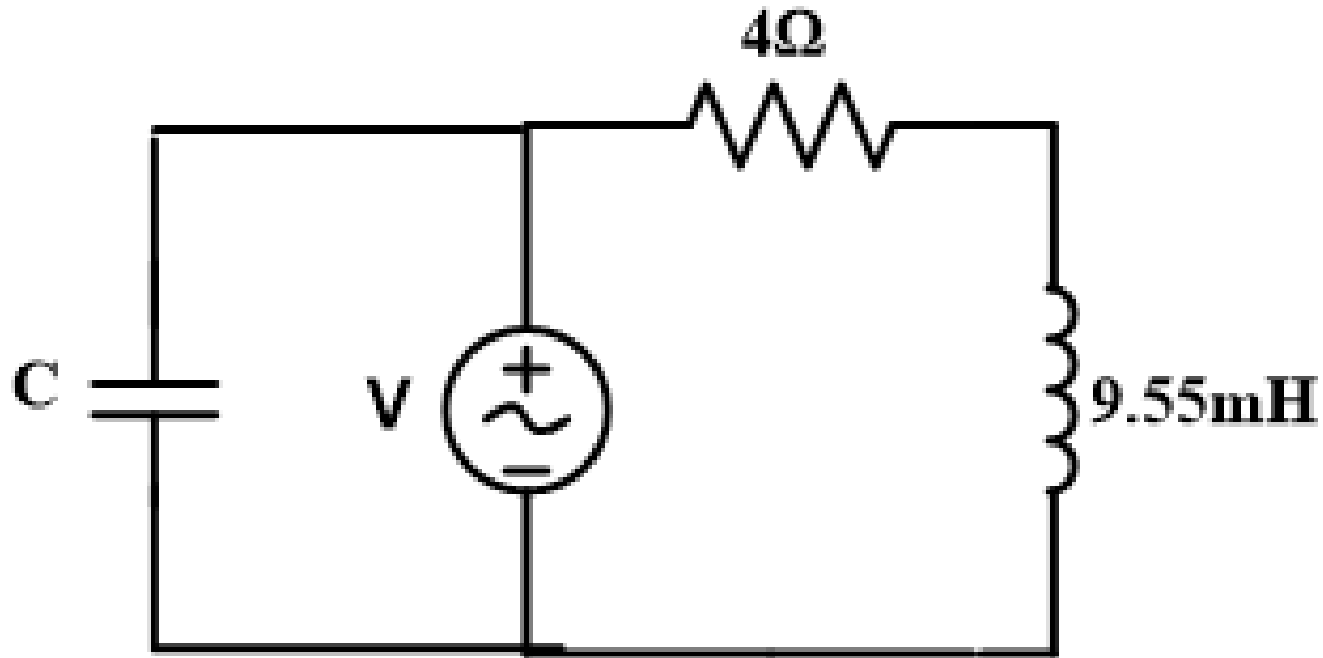For improving the power factor, following scheme is adopted.



The capacitor has to generate

$$Q_c = (48 - 31) = 17 \text{ VAR}$$

$$Q_c = V^2 / X_c = 17 \Rightarrow \omega C V^2 = 17$$

$$C = 17 / (2 \times \pi \times 50 \times 400) = 135.3 \text{ } \mu\text{F}$$