

TUTORIAL-3

EE 101: Basic Electronics

DEPARTMENT OF ELECTRONICS & ELECTRICAL ENGINEERING

INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI


(First question is the **Pre-Tutorial Assignment problem** to be solved in the space provided.)

Name:

Roll No.


Tutorial Group:

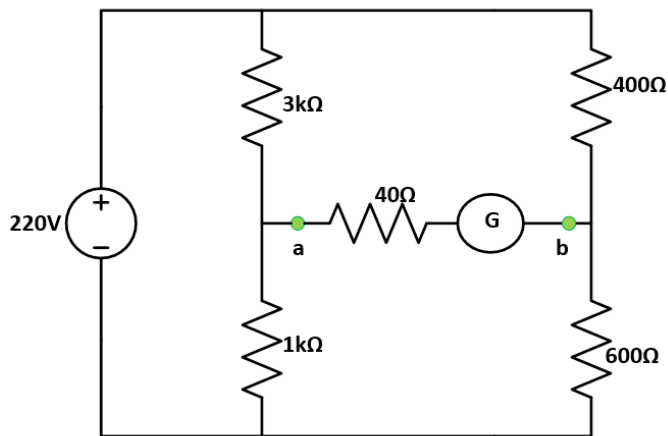1. Find current through the Galvanometer (G, from terminal a to terminal b) which has an internal resistance of $40\ \Omega$.




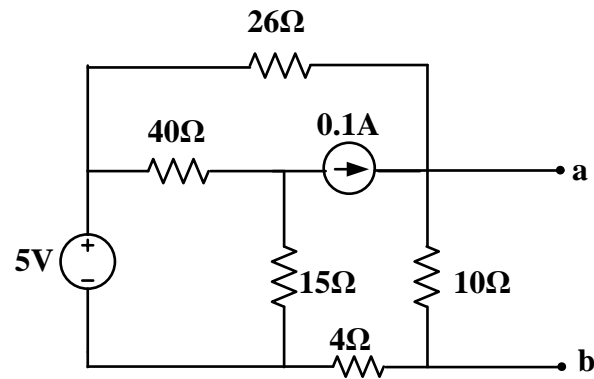2. Find Norton's equivalent resistance in the following circuit as seen by the terminal a-b by the
a). conventional method and
b). open-circuit voltage and short-circuit current method.

Give reasons, if any, for differences between the two estimated values.




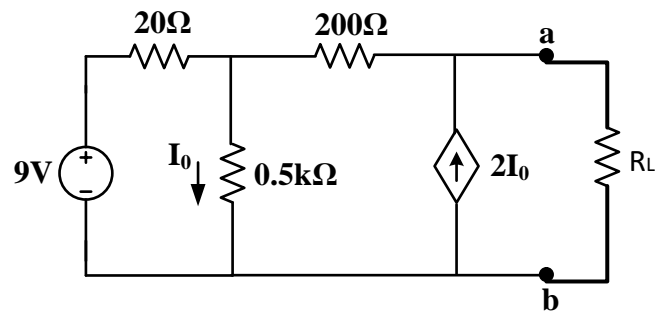3. Find the maximum power delivered to the load resistor R_L .




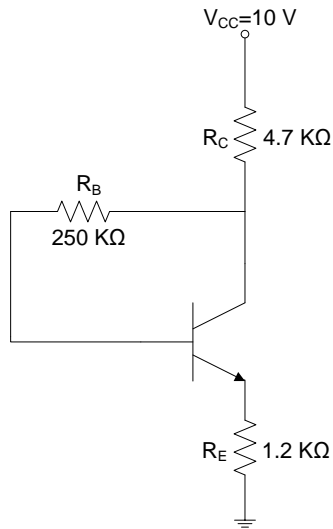4. In the two circuits shown below, the transistors have $\beta=100$. Assume $V_{BE}=0.7\text{ V}$ when the B-E junction is forward biased and $V_{CE}=0.1\text{ V}$ if the transistor is in saturation

Find the Q-point for the transistors in (i) and (ii), i.e. V_{CE} , I_C and I_B



(i)

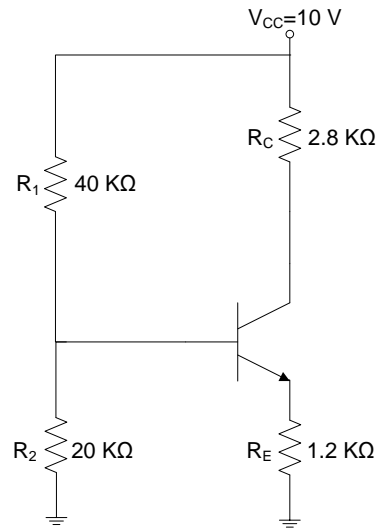

(ii)

5. In the circuit of (ii), R_1 is changed to be $20\text{ k}\Omega$ while everything else remains the same. What will be the state of the transistor in this case?