

EE-101: Basic Electronics, Quiz-1

Set Code: EE-101/2019/Q1-JH


Max. Time: 45 min

Max. Marks: 10

Tutorial Group: T- 18

Roll no.: 190123046

Name: Radhesh Pasad
Kalkar

Invigilator's Signature: 

Instructions

- Write answers neatly with **appropriate SI units** in the spaces provided
- All answers should be rounded upto **third decimal point**.
- **Exchange** of Calculators or any other material is not allowed.
- **Mobile phones** are not allowed inside the examination hall.

1. For the circuit shown in Fig. 1, find the voltages V_1 and V_2 and the currents I_1 , I_2 and I_3 . Assume the diodes to be ideal with a forward voltage drop of 0.7 V. [1 X 5]

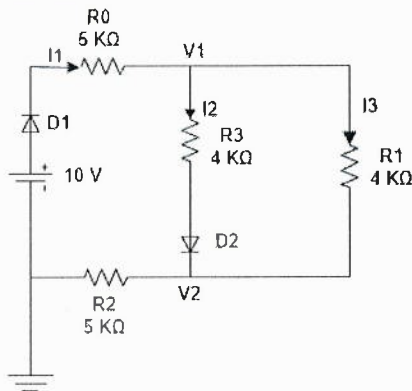


Fig. 1

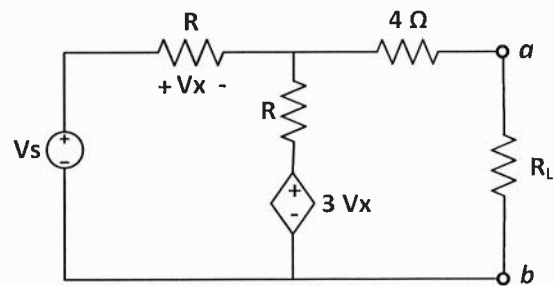


Fig. 2

Solution: (i) $V_1 = 5.571V$ (ii) $V_2 = 3.729V$ (iii) $I_1 = 0.746mA$
(iv) $I_2 = 0.286mA$ (v) $I_3 = 0.460mA$

2. For the circuit shown in Fig. 2, the value of the source voltage (V_s) is 5 V and the resistor (R) value is 5 Ω . Find the Thevenin voltage (V_{th}) and the Thevenin equivalent resistance (R_{th}) across the terminal $a-b$. Find the maximum power (P_m) delivered to the load resistor R_L .

[2+2+1]

Solution: (i) $V_{th} = 4.000V$

(ii) $R_{th} = 5.000\Omega$

(iii) $P_m = 0.800W$