

TUTORIAL-11

PRE-TUTORIAL ASSIGNMENT- SOLUTION

Solution:

(a)

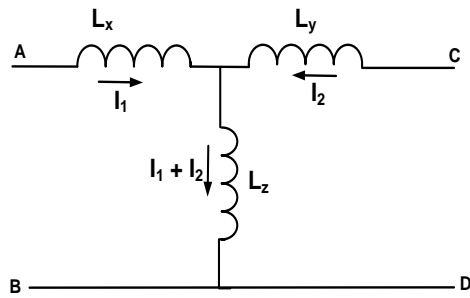


Fig. 1(a)

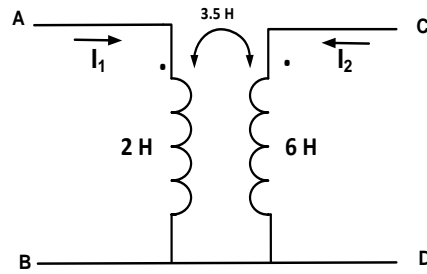


Fig. 1(b)

From Fig. 1(a) we can write,

$$\begin{aligned} V_{AB} &= L_x I_1 + L_z I_1 + L_z I_2 \\ V_{CD} &= L_y I_2 + L_z I_1 + L_z I_2 \end{aligned}$$

From Fig. 1(b) we can write,

$$\begin{aligned} V_{AB} &= 2I_1 + 3.5I_2 \\ V_{CD} &= 6I_2 + 3.5I_1 \end{aligned}$$

From the above equations we can write,

$$\begin{aligned} L_x + L_z &= 2 \\ L_z &= 3.5 H \\ \Rightarrow L_x &= -1.5 H \\ L_y + L_z &= 6 \\ \Rightarrow L_y &= 2.5 H \end{aligned}$$

(b) If the dot in the secondary of Fig. 1(b) is reversed than the equations will be,


$$\begin{aligned} V_{AB} &= 2I_1 - 3.5I_2 \\ V_{CD} &= 6I_2 - 3.5I_1 \end{aligned}$$

From the above equations we can write,

$$\begin{aligned} L_x + L_z &= 2 \\ L_z &= -3.5 H \\ \Rightarrow L_x &= 5.5 H \\ L_y + L_z &= 6 \\ \Rightarrow L_y &= 9.5 H \end{aligned}$$

TUTORIAL-11: SOLUTIONS

Solution-1:

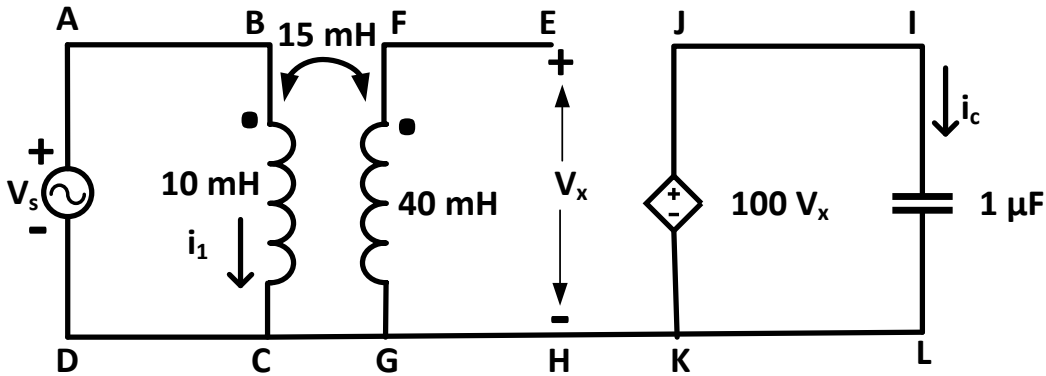

Applying KVL in the loop ABCDA

$$\frac{10t^2}{t^2 + 0.01} = 10 \times 10^{-3} \frac{di_1}{dt}$$

$$\Rightarrow \frac{di_1}{dt} = \frac{1000t^2}{t^2 + 0.01}$$

There will be an induced voltage in 40 mH coil due to the current i_1 in 10 mH coil. Applying KVL in the loop EFGHE

$$15 \times 10^{-3} \frac{di_1}{dt} = V_x$$

$$\Rightarrow V_x = \frac{15t^2}{t^2 + 0.01}$$

Applying KVL in the loop LKJIL

$$100V_x - \frac{\int i_c dt}{C} = 0$$

$$\Rightarrow i_c = 100C \times \frac{dV_x}{dt} = \frac{0.03t}{(t^2 + 0.01)^2} \text{ mA}$$

Solution-2: $Z_{in} = R_s + j\left(\omega L_s - \frac{1}{\omega C_s}\right)$ At $\omega = 45 \text{ krad/s}$, $Z_{in} = 65.4 \angle -40.2^\circ$

$$\frac{Z_c}{R} = \frac{1}{\omega CR} = \frac{1}{45 \times 10^{-4} \times 50} = 4.44$$

Maximum value of current will flow when the impedance is minimum. The impedance will be minimum when

$$\left(\omega L_s - \frac{1}{\omega C_s}\right) = 0, \text{ Hence}$$

$$\omega = \frac{1}{\sqrt{LC}} = 50 \text{ krad/s} \quad \text{and the corresponding } f = \frac{\omega}{2\pi} = 7.96 \text{ kHz}$$

Solution-3:

Decimal x	Binary I\P			$y_4 \ y_3 \ y_2 \ y_1 \ y_0$				
	x_2	x_1	x_0					
0	0	0	0	0	0	0	1	0
1	0	0	1	0	0	1	0	1
2	0	1	0	0	1	0	0	0
3	0	1	1	0	1	0	1	1
4	1	0	0	0	1	1	1	0
5	1	0	1	1	0	0	0	1
6	1	1	0	1	0	1	0	0
7	1	1	1	1	0	1	1	1

By observation


$$y_0 = x_0$$

$$y_1 = \sum m(0,3,4,7)$$


$$y_2 = \sum m(1,4,6,7)$$

$$y_3 = \sum m(2,3,4)$$

$$y_4 = \sum m(5,6,7)$$

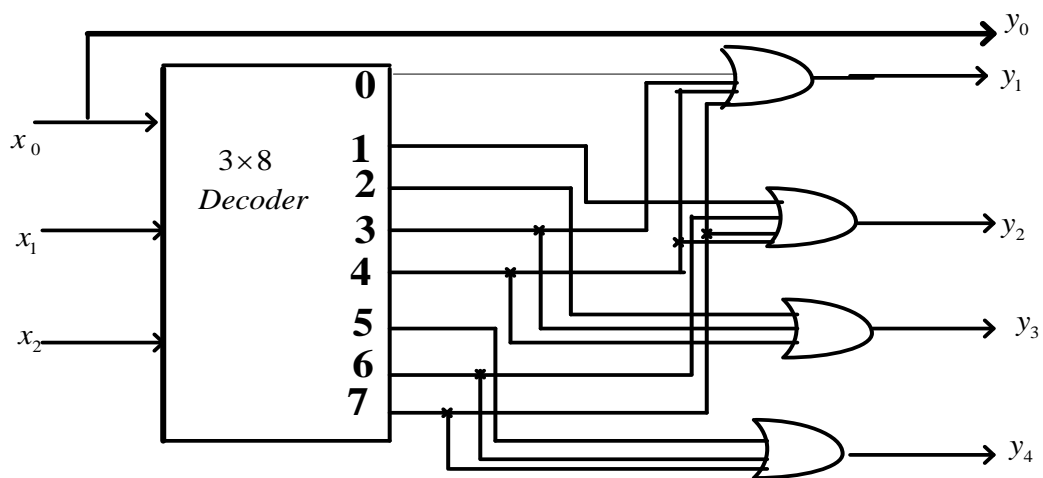

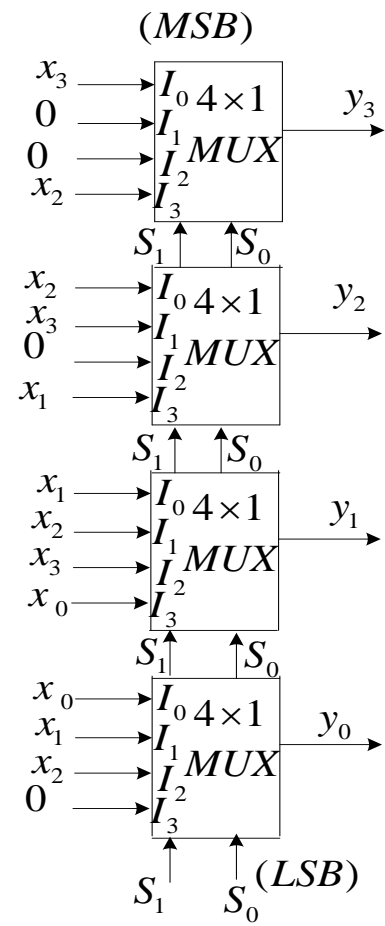Solution-4: Let input 4 bit string be MSB x_3, x_2, x_1, x_0 LSB



S_1	S_0	MUX
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

y_3	y_2	y_1	y_0
x_3	x_2	x_1	x_0
0	x_3	x_2	x_1
0	0	x_3	x_2
x_2	x_1	x_0	0