

10. Consider the two cascaded  $2 \times 1$  multiplexers as shown below in Fig. Q10. Determine the minimal sum of products expression for the output  $f(P, Q, R)$  if  $I_0$  of MUX<sub>1</sub> and MUX<sub>2</sub> are  $\bar{R}$  and 0 respectively. [2]

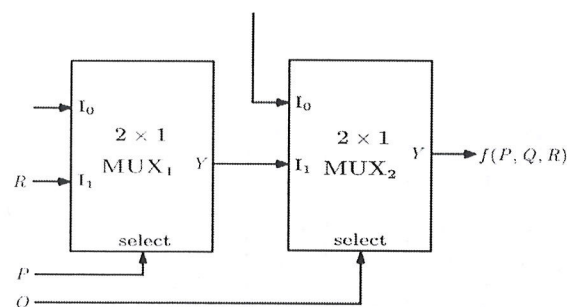


Fig. Q10

Solution:  $f(P, Q, R) = \sum m(2, 7) = \bar{P}QR + PQR$

11. A synchronous counter has three  $JK$  flip-flops with the input functions  $J_2 = \bar{Q}_1$ ;  $K_2 = Q_0$ ;  $J_1 = Q_2 + Q_0$ ;  $K_1 = \bar{Q}_2$ ;  $J_0 = Q_1$  and  $K_0 = 0$ . (a) Assuming that initially  $Q_2Q_1Q_0 = 000$ , determine the number of clock pulses are required before the counter begins as a modulo- $N$  counter? (b) What is  $N$ ? [1+2]

Solution: (a) 3

(b) 3

12. A three bit pseudo random number generator is shown in Fig. Q12. Initially the value of output  $Y_2Y_1Y_0$  is set to 111. What is the value of the outputs  $Y_2Y_1Y_0$  after 600 clock cycles? [2]

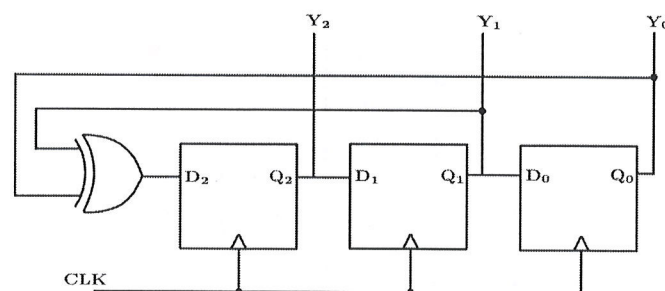


Fig. Q12

Solution: 101

## EE-101: Basic Electronics End semester Examination

Set Code: EE-101/2019/ES-SD

Max. Time: 180 min

Max. Marks: 30

Tutorial Group: T- 18

Roll no.: 190123046

Name: Radnesh P. Kalkar

Invigilator's Signature: *[Signature]*

### Instructions

- Write answers neatly with appropriate SI units in the spaces provided
- All answers should be rounded up to the third decimal point.
- Exchange of Calculators or any other material is not allowed.
- Mobile phones are not allowed inside the examination hall.
- Write answers neatly in the space below the question marked as Solution

1. A balanced three-phase system has star connected loads, star connected sources and nonzero line impedances. At the source end, the nomenclature of the three lines are with small letters **a, b, c** and at the load end, the nomenclatures are with capital letters **A, B, C**. The line voltage  $V_{AB}$  has a value of  $500 \angle 0^\circ$  V (rms). Voltage coil of one wattmeter (**W**) is connected between the lines **A** & **B** and the current coil is in series with the line **aA**. If the line and the load impedances per phase are  $Z_L = 1 + j0$  and  $Z_P = 12 + j5$ . Find, (a)  $V_{bn}$ (rms) (answer in phasor form) and (b) the reading of the wattmeter in kW. [1+2]

Solution: (a)  $V_{bn} = 309.285 \angle -151.582^\circ$  V (b)  $W = 6.741$  kW

2. A 400 V rms (line voltage) balanced three-phase system supplies 1500 W to a balanced Y-connected load at a lagging PF of 0.9. What are the values of (a) the per phase load resistance ( $R_P$ ) and (b) the per phase load reactance ( $X_P$ )? [1+1]

Solution: (a)  $R_P = 28.800 \Omega$  (b)  $X_P = 13.939 \Omega$

3. Find the equivalent inductances seen at terminals 1 and 2 in the network of Fig. Q3 if the following terminals are connected together: (a) none and (b) A to B. [1+1]

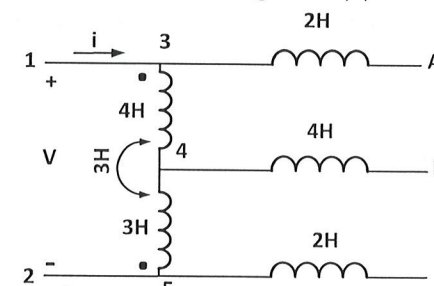


Fig.Q3

Solution: (a) 1.000 H

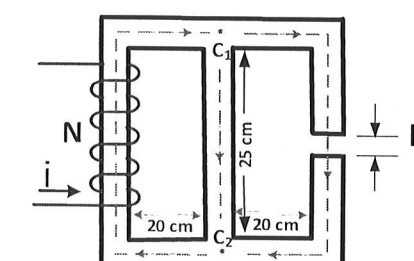


Fig.Q4

(b) 0.900 H

2

4. Fig. Q4 shows a parallel magnetic circuit. The core material has a relative permeability of 4000. The number of turns is given as  $N = 800$  and the cross-sectional area of the core is  $A_c = 3 \times 3 \text{ cm}^2$ . The length of the air gap is  $l_g = 0.02 \text{ cm}$  and the flux in the central limb is  $0.01 \text{ Wb}$ . Find (a) the flux in the right limb and (b) the required exciting current. [1+2]

Solution: (a)  $0.002 \text{ Wb}$  (b)  $3.186 \text{ A}$

2

5. Let  $i_s = 3 \cos(10t) \text{ A}$  in the circuit shown in Fig. Q5. Find the total energy stored when the current  $i_s$  is maximum if (a) a-b is open-circuited, (b) a-b is short-circuited. [1+1]

Solution: (a)  $49.500 \text{ J}$  (b)  $41.401 \text{ J}$

3

6. Determine (a) the value of the resonant frequency ( $f_0$ ) in Hz and (b) the magnitude of the impedance seen from the source at half power frequencies for the network shown in Fig. Q6. [2+1]

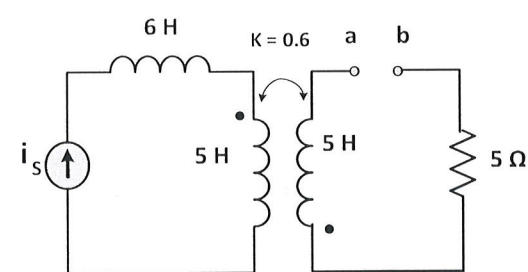


Fig. Q5

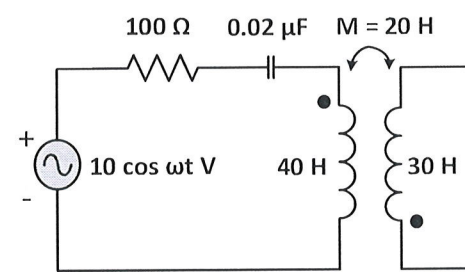


Fig. Q6

Solution: (a)  $217.392 \text{ Hz}$  (b)  $141.421 \text{ ohm}$

2

7. Given the network of figure shown in Fig. Q7, express the functions  $f_2(w, x, y, z)$  and  $f_3(w, x, y, z)$  using minimum possible number of minterms if  $f_1 = w\bar{y} + \bar{w}y$  and the overall transmission function is to be  $f(w, x, y, z) = \sum m(0, 4, 9, 10, 11)$ . Given that  $f_2(w, x, y, z) \neq 0$ . [1+1]

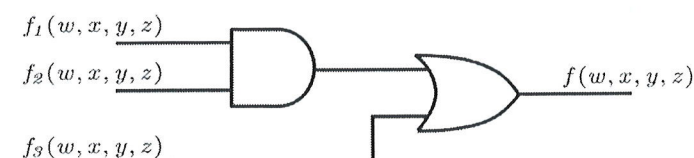


Fig. Q7

Solution:  $f_2(w, x, y, z) = \sum m(9)$ ;  $f_3(w, x, y, z) = \sum m(0, 4, 10, 11)$

1.5

8. The literal count of a Boolean expression is the sum of the number of times each literal appears in the expression. For example, the literal count of  $(xy + x\bar{z})$  is 4. What are the minimum possible literal counts of the (a) product-of-sum and (b) sum-of-product representations respectively of the function given by the following K-map (Fig. Q8)? Here, X denotes "don't-care". [1.5+1.5]

yz \ wx	00	01	11	10
00	X	1	0	1
01	0	1	X	0
11	1	1	X	0
10	X	0	0	X

Fig. Q8

Solution: (a) 9 (b) 10

3

9. The borrow obtained from the operation  $x - y - z$  of a full subtractor can be realized using two  $2 \times 4$  decoders as shown in Fig. Q9. For feasible realization, the input and enable signals of the decoders can be connected to one of the six signals  $\{x, \bar{x}, y, \bar{y}, z, \bar{z}\}$ . The appropriate choice for  $A_0, A_1, E_0, B_0, B_1$  and  $E_1$  are respectively. [3]

Solution:  $A_0 = z$ ;  $A_1 = y$ ;  $E_0 = x$ ;  $B_0 = z$ ;  $B_1 = y$ ;  $E_1 = \bar{x}$

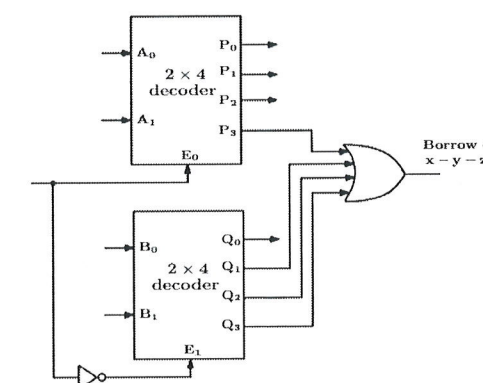


Fig. Q9