

Lecture 8

Sinusoidal Forcing Function,
Phasor Relationship for R, L and C,
Impedance and Admittance,
Phasor Diagram

Why not only ac?

Storage, transmission loss, waste of power

Why not only dc?

Generation, dc/ac/dc conversion

Hybrid systems using ac+dc

Projector, audio system

- Why RMS of ac?

Average captures no information


Peak captures limited information

Sinusoidal Response of a Resistor

$$v(t) = V_m \sin \omega_0 t$$

$$i(t) = I_m \sin \omega_0 t$$

$$I_m = \frac{V_m}{R}$$

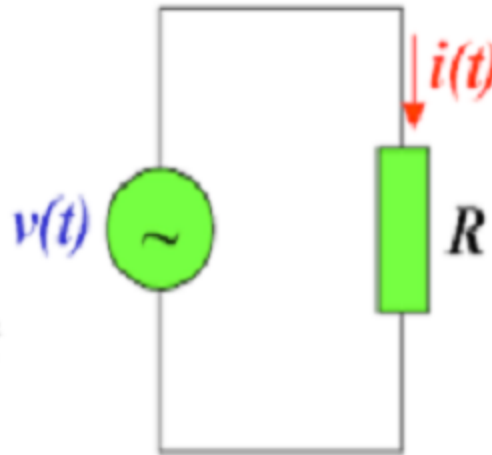


Current is also sinusoidal.

Has the same angular frequency, ω_0

Current and voltage of a resistor is in phase $\rightarrow \phi = 0$

Current magnitude is related to voltage magnitude by $I_m = \frac{V_m}{R}$

Sinusoidal Response of a Capacitor

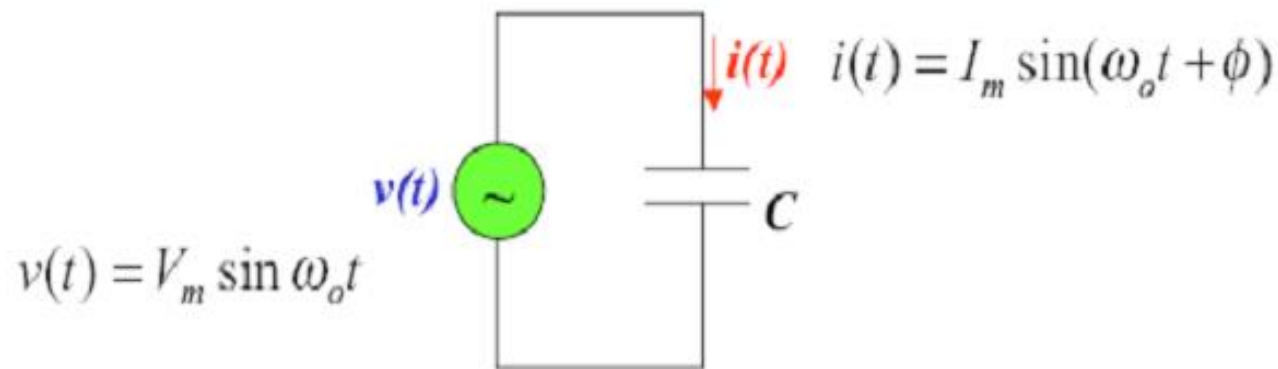


$$i(t) = C \frac{dv(t)}{dt}$$

$$i(t) = \omega_o C V_m \cos \omega_o t$$

$$i(t) = \omega_o C V_m \sin(\omega_o t + 90)$$

$$I_m = \omega_o C V_m$$

Sinusoidal Response of an Inductor

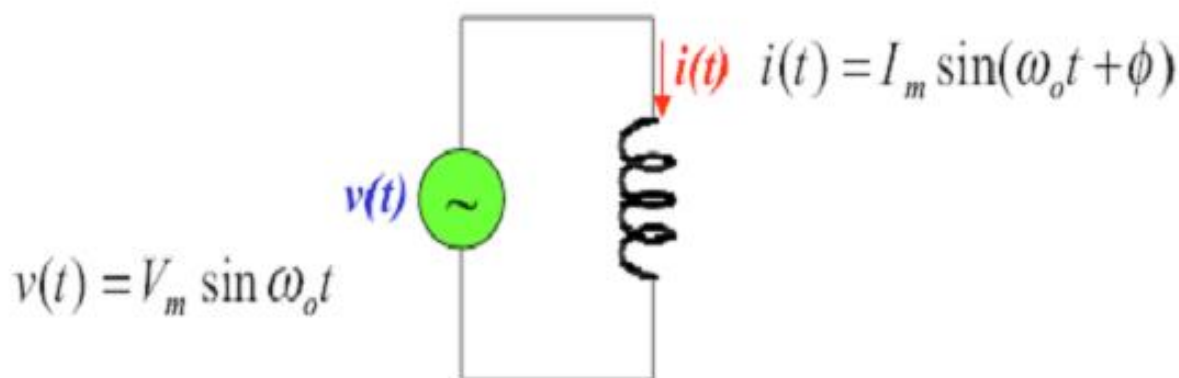

$$i(t) = \frac{1}{L} \int v(t) dt = -\frac{1}{\omega_o L} V_m \cos \omega_o t$$


$$i(t) = -\frac{1}{\omega_o L} V_m \sin(\omega_o t + 90)$$

$$i(t) = \frac{1}{\omega_o L} V_m \sin(\omega_o t - 90)$$


Phasor Plot

$$v(t) = V_m \cos(\omega t + \phi) = \operatorname{Re}\{V_m e^{j(\omega t + \phi)}\} = \operatorname{Re}\{V e^{j\omega t}\}$$

$$V = V_m e^{j\phi} = V_m \angle \phi$$

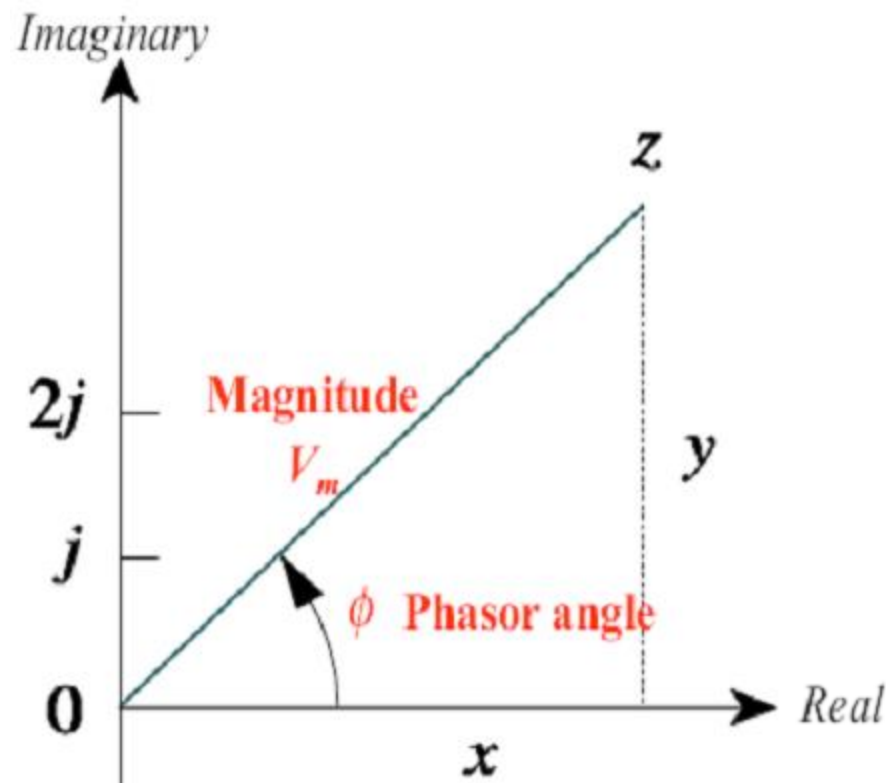

Phasor Response of a Capacitor

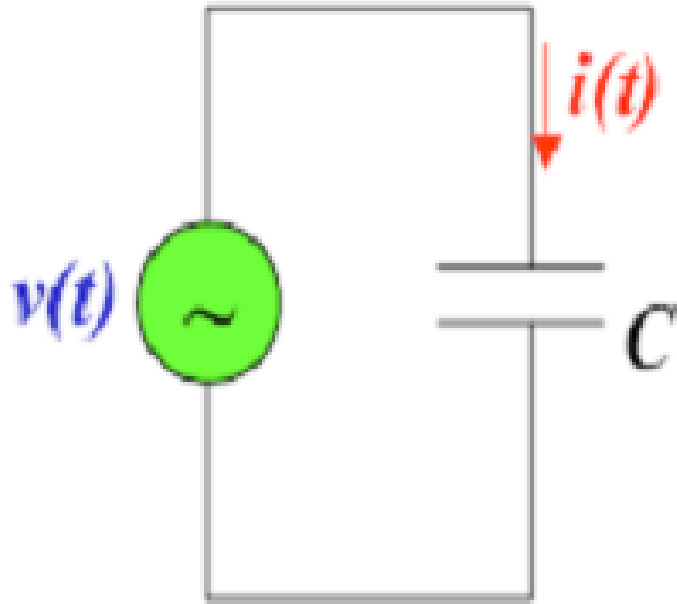

If $v(t) = V_m e^{j\omega_o t}$

$$v(t) = V_m \angle 0$$


then $i(t) = C \frac{dv(t)}{dt}$

$$i(t) = j\omega_o C V_m e^{j\omega_o t}$$

$$= I_m \angle 90^\circ$$

$$I_m = \omega_o C V_m$$

Phasor Response of an Inductor

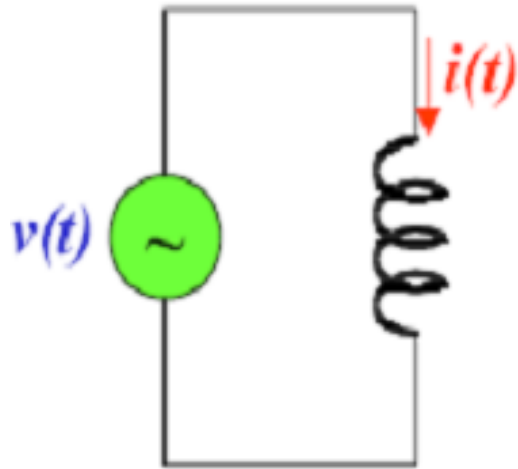

If $v(t) = V_m e^{j\omega_o t}$

$$v(t) = V_m \angle 0$$


then

$$i(t) = \frac{1}{L} \int v(t) dt$$

$$I_m = \frac{V_m}{\omega_o L}$$

$$i(t) = \frac{1}{j\omega_o L} V_m e^{j\omega_o t} = I_m \angle -90^\circ$$

Time domain

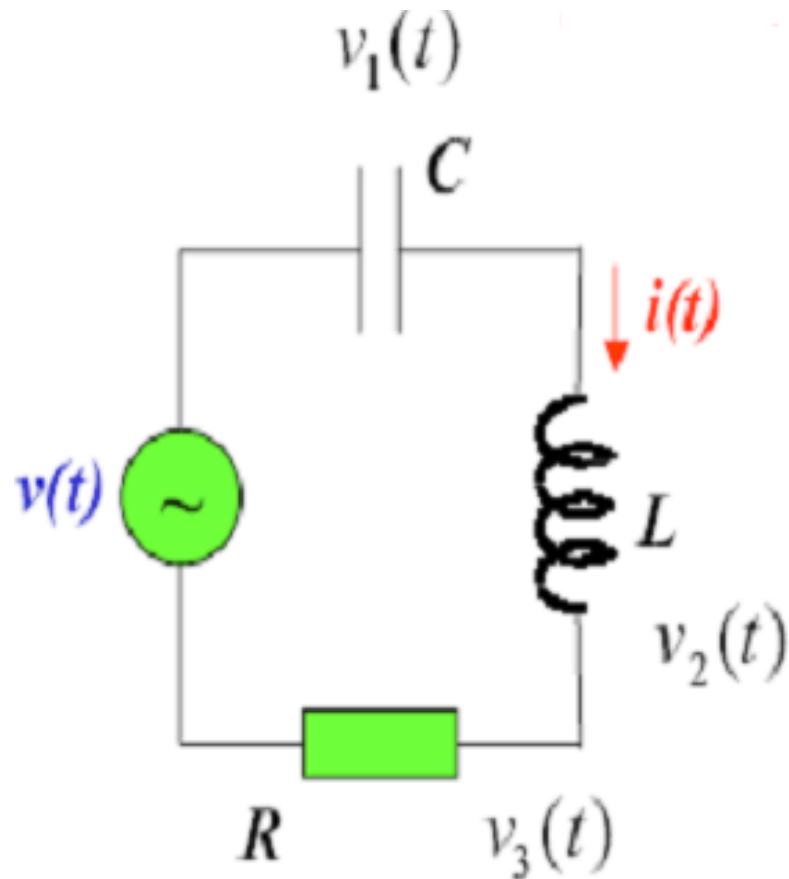

$$v(t) = V_m \cos \omega_o t$$


$$i(t) = I_m \cos(\omega_o t + \phi)$$

$$v_1(t) = V_1 \cos(\omega_o t + \phi_1)$$


$$v_2(t) = V_2 \cos(\omega_o t + \phi_2)$$

Phasor Transformation

Phasor domain

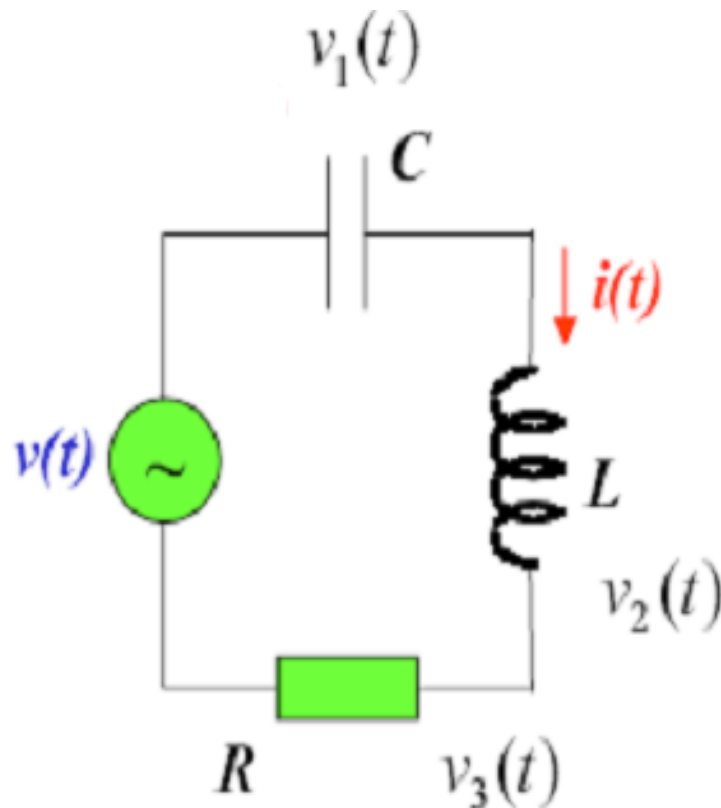

$$v(t) = V_m e^{j\omega_o t}$$

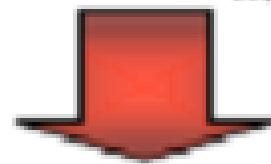


$$i(t) = I_m e^{j(\omega_o t + \phi)}$$

$$v_1(t) = V_1 e^{j(\omega_o t + \phi_1)}$$

$$v_2(t) = V_2 e^{j(\omega_o t + \phi_2)}$$

Example

- Consider the AC circuit

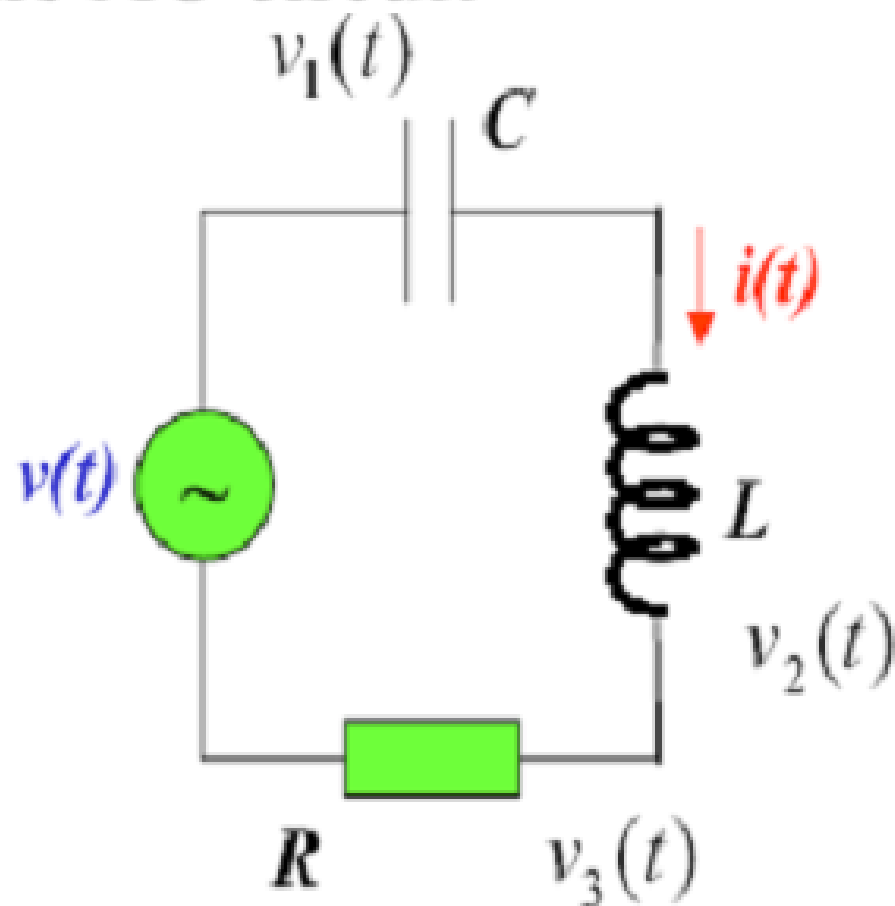

- Let $i(t) \longleftrightarrow I$

- Then $I = I_m e^{j\omega_o t}$

$$V = V_m e^{j(\omega_o t + \phi)}$$

- Then

$$V_1 = \frac{1}{j\omega_o C} I$$

$$V_2 = j\omega_o L I$$


$$V_3 = R I$$

$$V = (R + j\omega_o L + \frac{1}{j\omega_o C})I$$

$$V = [R + j(\omega_o L - \frac{1}{\omega_o C})]I$$

- So given V_m , we can determine I_m
 - Or given I_m , we can determine V_m
- and we can determine the phase angle between I and V**

Impedance of a Resistor

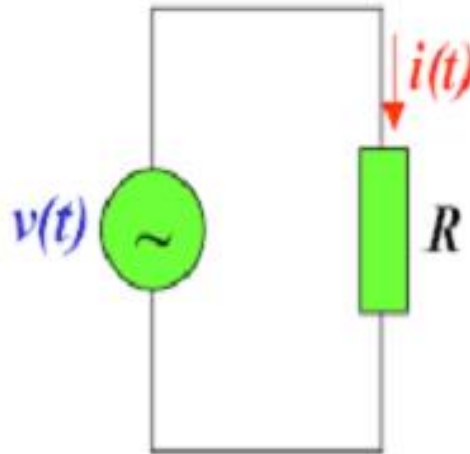


$$\begin{aligned} v(t) &= V_m e^{j(\omega_o t + \phi)} \\ i(t) &= \frac{V_m}{R} e^{j(\omega_o t + \phi)} \end{aligned}$$

Impedance $= \mathbf{Z}$

$$\frac{v(t)}{i(t)} = R$$

The diagram shows the word "Impedance" in red, followed by " $= \mathbf{Z}$ ". A dashed green arrow points from the \mathbf{Z} to a green dashed circle containing the expression $\frac{v(t)}{i(t)}$. To the right of the circle is an equals sign followed by the letter R .

Impedance of a Capacitor

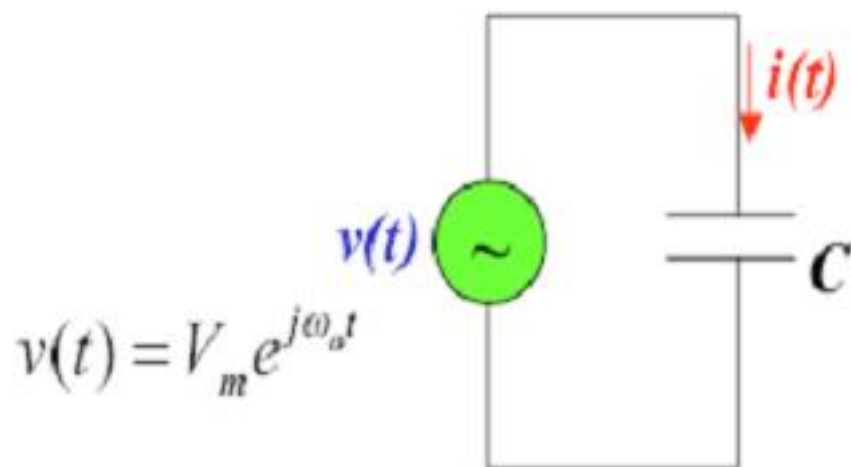

$$v(t) = V_m e^{j\omega_o t}$$


$$i(t) = C \frac{dv(t)}{dt}$$

$$i(t) = j\omega_o C V_m e^{j\omega_o t}$$

$$\text{Impedance of a capacitor} = \mathbf{Z} = \frac{v(t)}{i(t)} = \frac{1}{j\omega_o C}$$

$$\text{Impedance of an inductor} = \mathbf{Z} = \frac{v(t)}{i(t)} = j\omega_o L$$

Impedance of an inductor

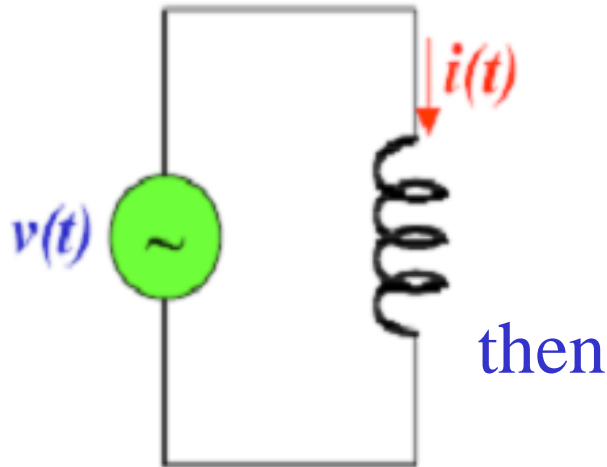

$$\text{If } v(t) = V_m e^{j\omega_o t}$$

$$i(t) = \frac{1}{L} \int v(t) dt$$

$$i(t) = \frac{1}{j\omega_o L} V_m e^{j\omega_o t}$$

$$\text{Impedance of an inductor} = \mathbf{Z} = \frac{v(t)}{i(t)} = j\omega_o L$$

• $R = 15\Omega; C = 800\mu F; L = 0.2H$ *Example*


• $\omega_o = 50\text{rad/s}$ Find $i(t)$ if $v(t) = 15 \cos \omega_o t$

• Then $Z_R = 15\Omega$

$$Z_C = \frac{1}{j\omega_o C} = -j25\Omega$$

$$Z_L = j\omega_o L = j10\Omega$$

$$Z = 15 - j15$$

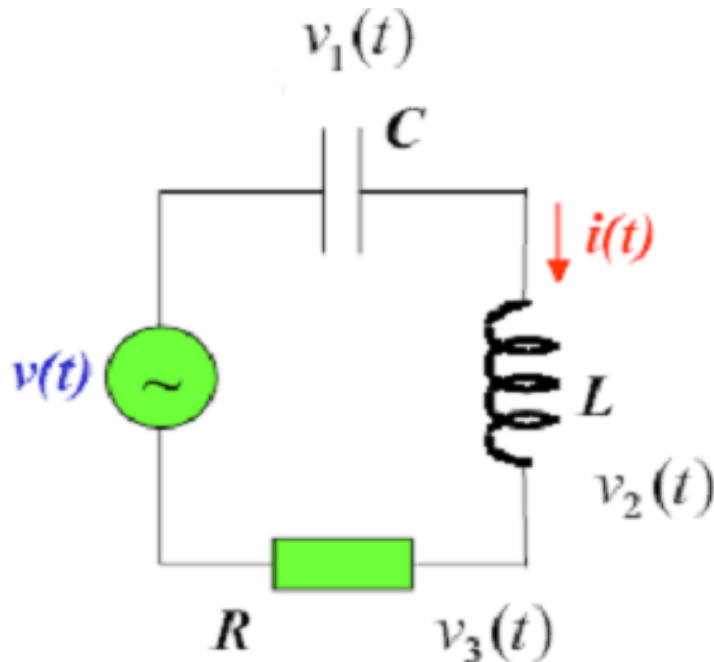

• If $v(t) = 15 \cos \omega_o t$

• Then $i(t) = \frac{1}{\sqrt{2}} \cos(\omega_o t + \frac{\pi}{4})$