

TUTORIAL-4

EE 101: Basic Electronics

DEPARTMENT OF ELECTRONICS & ELECTRICAL ENGINEERING

INDIAN INSTITUTE OF TECHNOLOGY GUWAHATI

(First question is the Pre-Tutorial Assignment problem to be solved in the space provided.)


Name:

Roll No.


Tutorial Group:

Q.1 If the switch in the following circuit is closed at time $t = 0$, then find

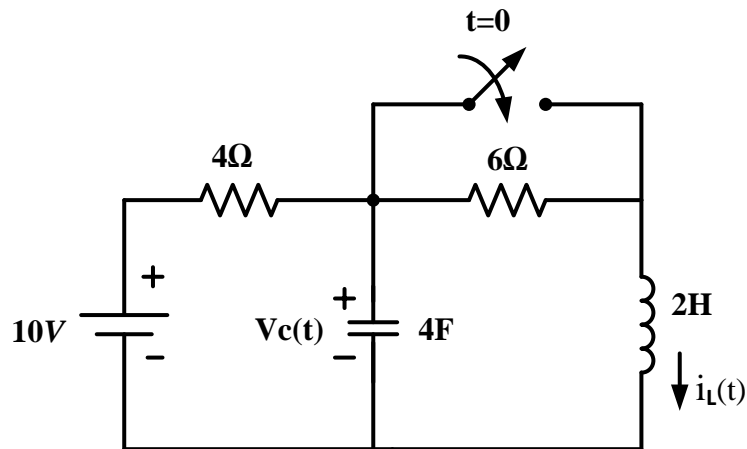- a) $V_c(0^-)$ b) $V_c(0^+)$ c) $dV_c(0^-)/dt$ d) $dV_c(0^+)/dt$ e) $di_L(0^-)/dt$ and f) $di_L(0^+)/dt$




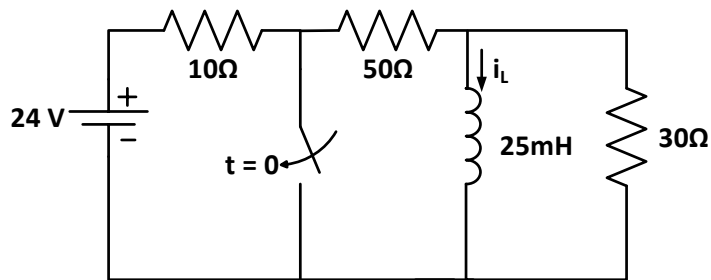Q.2 For the circuit shown below, the switch were open for a long time before it closes at time $t = 0$. Find $i_L(t)$ for $t > 0$.




Q.3 In the following circuit, the switch was closed for a long time before opening at $t = 0$.

Find $V_C(t)$ for $t > 0$.

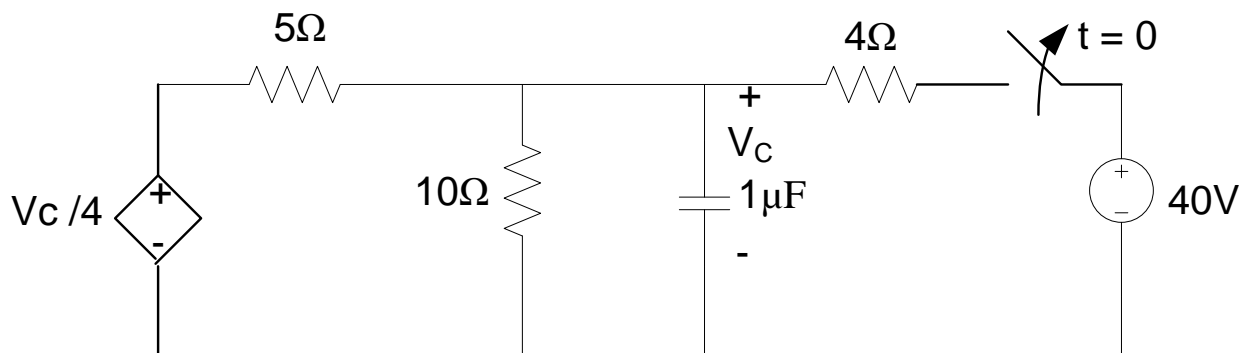

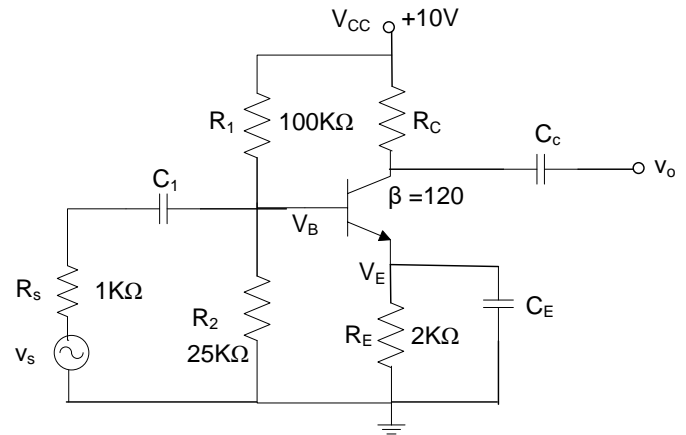Q.4 Consider the transistor amplifier shown below assuming that the capacitors are large enough to be ignored (short-circuited) for AC analysis. The transistor is assumed to have $\beta=120$ and the output resistance r_o of the transistor can be ignored. Assume $V_T=26\text{ mV}$



- (a) For this amplifier, choose R_C such that a voltage gain of $A_v=v_o/v_s=-160$ can be provided.
- (b) For this choice of R_C , what is the Q-point of the transistor?

Q.5

(a) Your friend assembled the circuit shown in the figure in the lab and he measured the DC voltages at A, C and E (with respect to ground) to be $V_A=3.45\text{ V}$, $V_C=9.39\text{ V}$ and $V_E=2.63\text{ V}$. Using these measurements, calculate the r_e and β of the transistor.

(b) Consider the same circuit once again but assume that $r_e=0.05\text{ k}\Omega$ and $\beta=20$. Do the small signal analysis of this circuit and find its voltage gain, input impedance and output impedance

