

TUTORIAL-2

EE 101: Basic Electronics


DEPARTMENT OF ELECTRONICS & ELECTRICAL ENGINEERING

INDIAN INSTITUTE OF TECHNOLOGY, GUWAHATI

PRE-TUTORIAL ASSIGNMENT- PROBLEM

(To be solved in the space provided.)

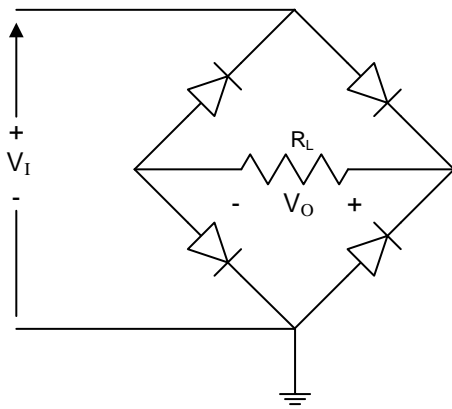
1. The bridge rectifier shown in the figure uses ideal diodes with a diode drop of 0.7 V.
 - (a) If the voltage V_I is sinusoidal with 25 V (RMS) and the load resistance R_L is $100\ \Omega$, what is the DC load current?
 - (b) What would be the required PIV of the diodes in the circuit?




TUTORIAL-2: PROBLEMS

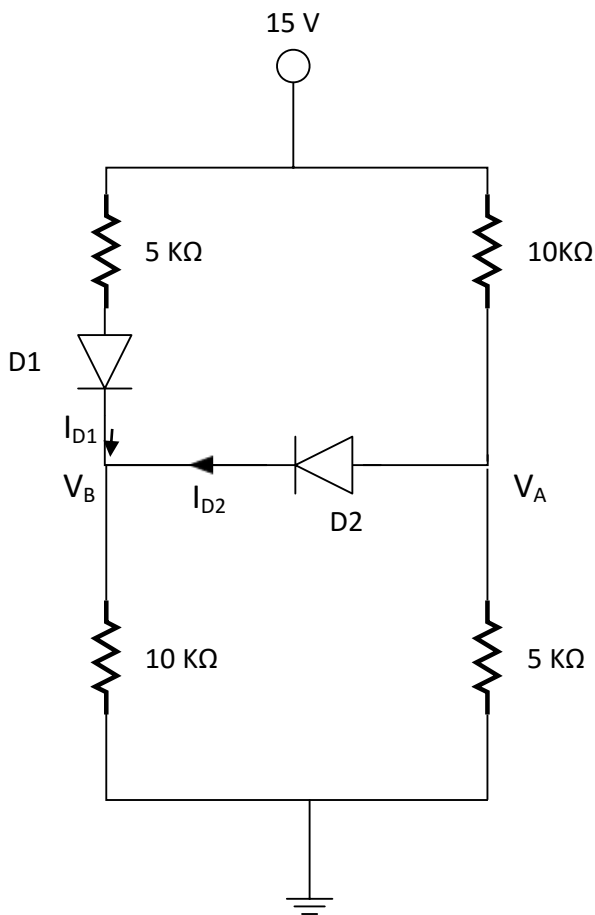1. For the circuit shown in the figure, what will be the state of the two diodes, D1 and D2? What will be the voltages V_A , V_B and the currents I_{D1} and I_{D2} ? Assume that a diode has a forward bias voltage of 0.7 V when it is conducting (i.e. when it is ON).


(Hint: There are four possibilities for the diode states of which only one will actually happen. Find this out and use it to find the required voltages and currents.)



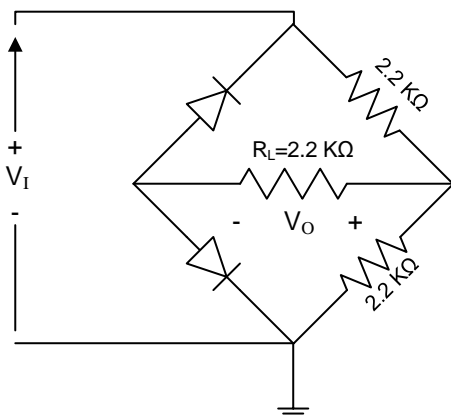2. Assume that ideal diodes with a diode voltage drop of 0.7 V are used in the circuit given below. Derive the V_O vs. V_I characteristic of this circuit and draw it.



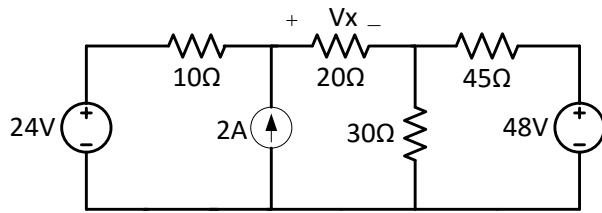3. Use superposition and source transformation to find the value of V_x for the circuit shown below.



4. Find the voltage across terminal pair xx' for the network shown using Thevenin's Equivalent circuit.

