

DIGITAL CIRCUITS


- ❖ Basic building blocks of digital computer .
- ❖ Broadly classified as combinational & sequential.
 - ❖ In combinational circuits, output depends only on the present inputs .
 - ❖ In sequential circuits, output not only depends on present inputs but also on the previous outputs.
- ❖ Boolean algebra plays important role in the design and analysis of digital circuits .
- ❖ Boolean algebra is a branch of algebra in which values of the variable either 0 or 1.

logic 1=HIGH (or) TRUE=5V

logic 0=LOW (or) FALSE=0V
- ❖ The logical functions involved in Boolean expressions are NOT,OR and AND


NOT Gate

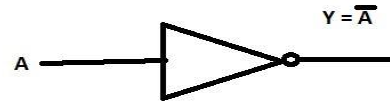❖ It has one input and one output signal. The output is complement of the input.




❖ Truth table is a table that describes output values for all the combinations of input values.

A	Y
0	1
1	0

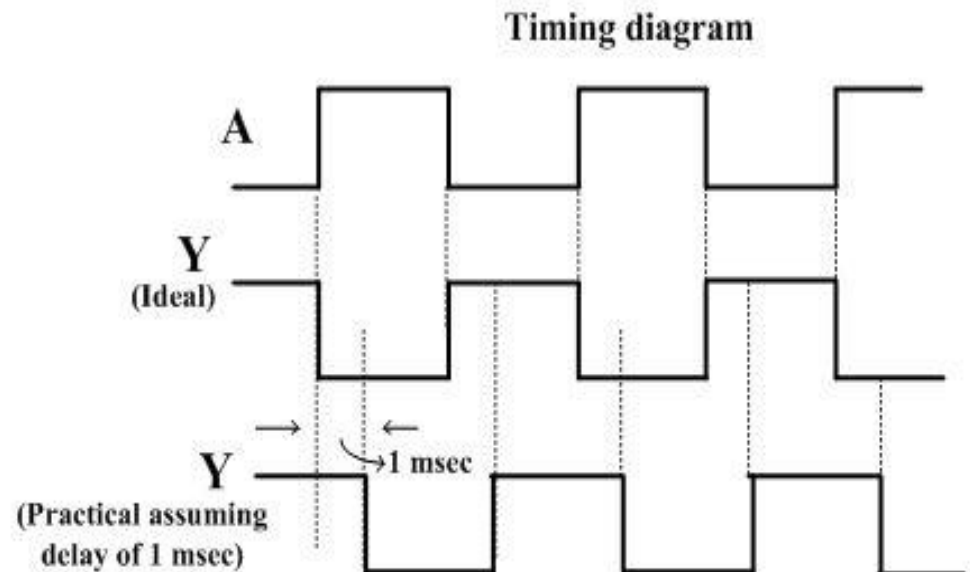


OR Gate

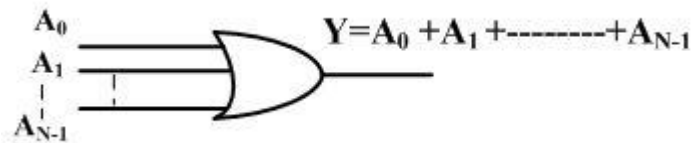- ❖ It has two or more input signals but only one output signal.
- ❖ The output is HIGH, if any or all the inputs are HIGH.



Truth table of two input OR gate

A_1	A_0	Y
0	0	0
0	1	1
1	0	1
1	1	1

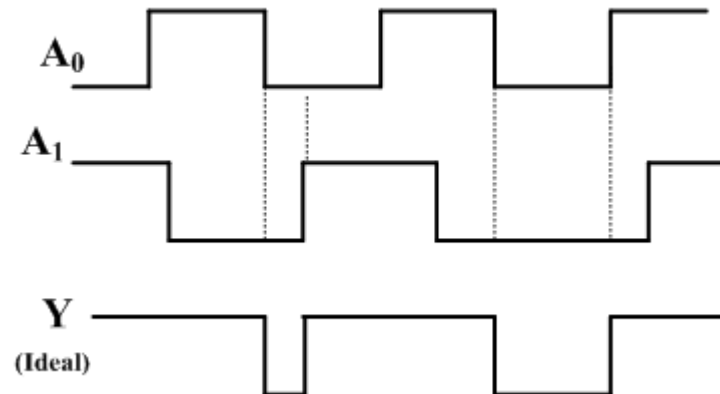

AND Gate

- ❖ AND gate has two or more inputs but only one output.
- ❖ Output is HIGH if all the inputs are HIGH.

Boolean laws and theorems

Laws of complementation

- (1) $\overline{\overline{A}} = A$
- (2) $\overline{\overline{1}} = 0$
- (3) $\overline{\overline{0}} = 1$

OR laws

- (1) $A+0=A$
- (2) $A+1=1$
- (3) $A+\overline{A}=1$
- (4) $A+\overline{A}=1$

AND laws

- (1) $A.0=0$
- (2) $A.1=A$
- (3) $A.\overline{A}=0$
- (4) $A.\overline{A}=0$

Commutative

$$A+B=B+A$$

$$AB=BA$$

Associative

$$(A+B)+C=A+(B+C)$$

$$=A+B+C$$

$$(AB)C=A(BC)=ABC$$

Distributive

$$A(B+C)=AB+AC$$

$$A+BC=(A+B)(A+C)$$

De Morgan's Theorem

$$\overline{A+B+C+\dots\dots\dots} = \overline{A} \overline{B} \overline{C} \dots\dots\dots$$

$$\overline{ABC\dots\dots\dots} = \overline{A} + \overline{B} + \overline{C} \dots\dots\dots$$

Conversion of English statements to Boolean expression.

Ex:- Seat Belt warning system .


$S=1 \rightarrow$ Seat belt fastened

$K=1 \rightarrow$ key inserted


$P=1 \rightarrow$ Person is seated

Let W = Output seat belt warning system.

$$\therefore W = P\bar{S}K$$

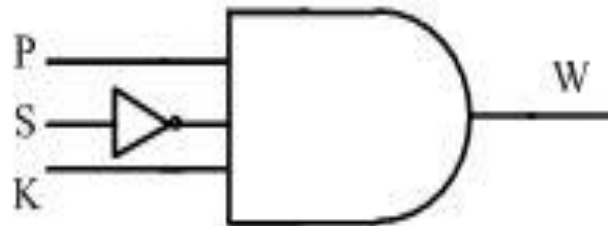


Ex-OR Gate

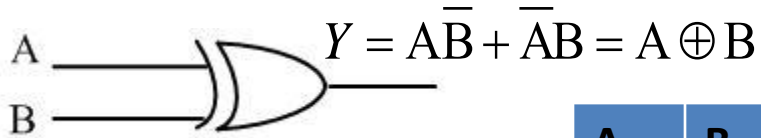

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

if inputs are same output is zero
if inputs are different output is 1

Ex-NOR Gate

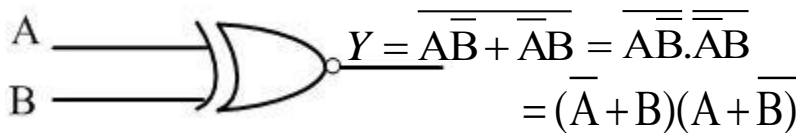


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

if inputs are same output is 1
otherwise output is zero.
Hence act as equality detector.


Universal Gates (NAND and NOR)

NAND Gate

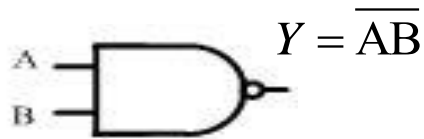


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


NOT using NAND

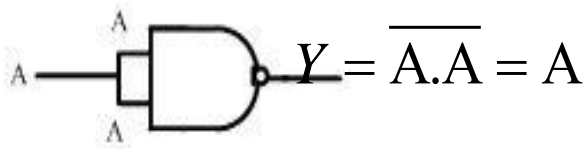


AND using NAND

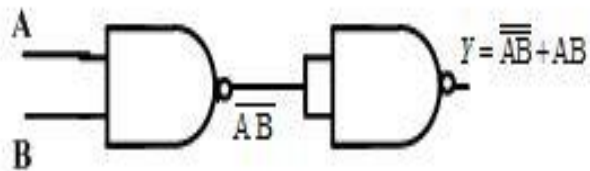

OR using NAND

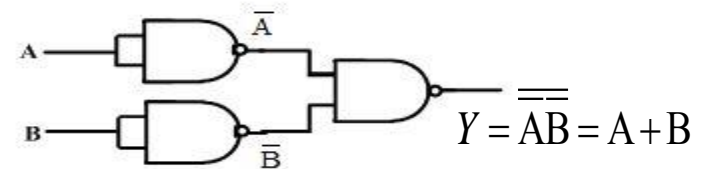

Ex-OR using NAND

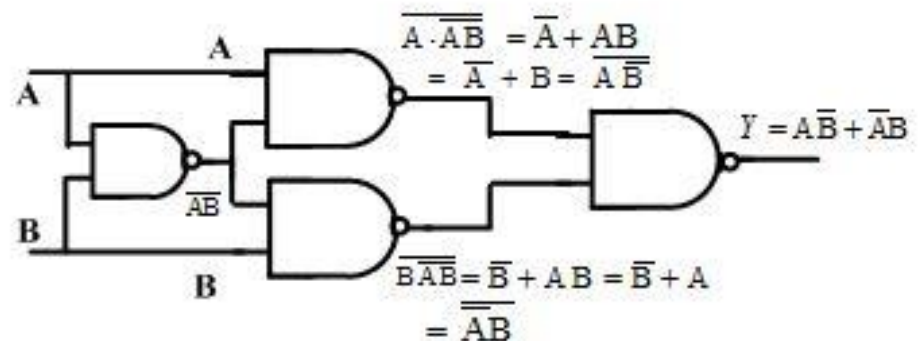


NOR Gate




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


NOT using NOR

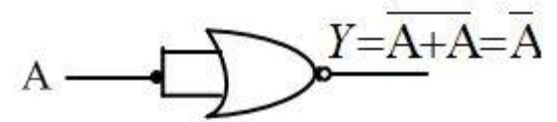

OR using NOR

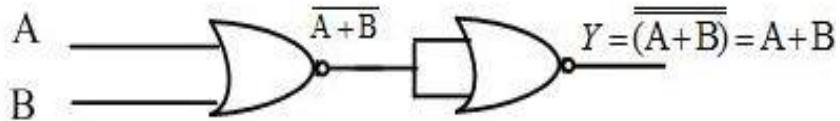

AND using NOR

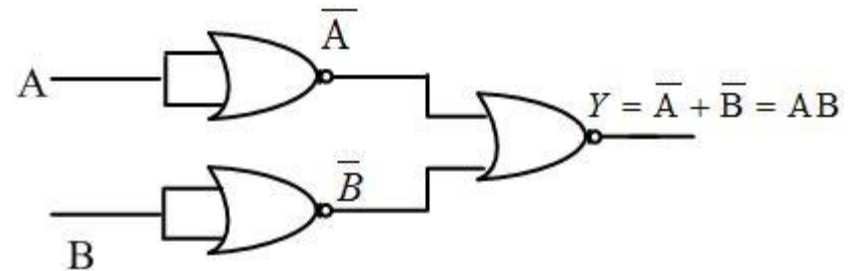

Ex-OR using NOR

